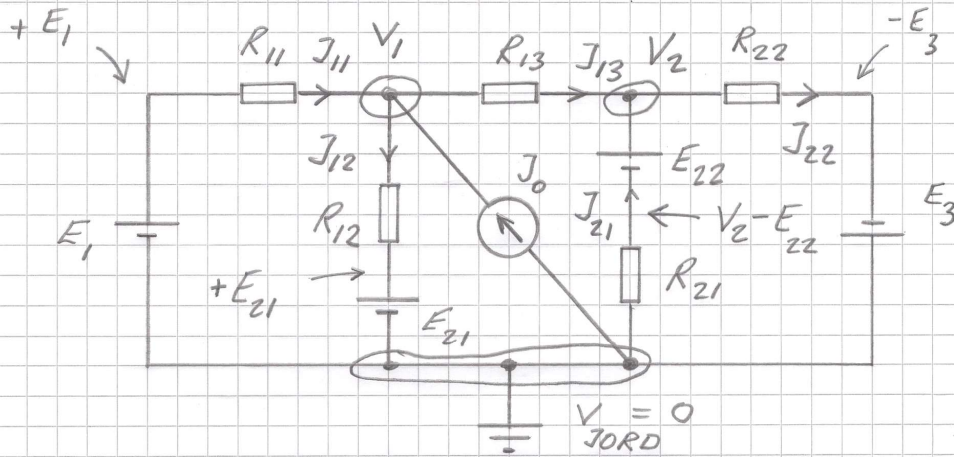


A1.17

NOD ANALYSIS



$$\text{NOD 1: } J_{11} - J_{12} + J_0 - J_{13} = 0 \dots (1)$$

$$\text{NOD 2: } J_{13} + J_{21} - J_{22} = 0 \dots (2)$$


$$\text{NOD 1: } \frac{E_1 - V_1}{R_{11}} - \frac{V_1 - E_{21}}{R_{12}} + J_0 - \frac{V_1 - V_2}{R_{13}} = 0 \dots (1)$$

$$\text{NOD 2: } \frac{V_1 - V_2}{R_{13}} + \frac{V_{\text{JORD}} - (V_2 - E_{22})}{R_{21}} - \frac{V_2 - (-E_3)}{R_{22}} = 0 \dots (2)$$

$$V_1 = +2,0 \text{ V} \quad V_2 = 0$$

$$J_{13} = \frac{V_1 - V_2}{R_{13}} \rightarrow J_{13} = 2,0 \text{ A}$$

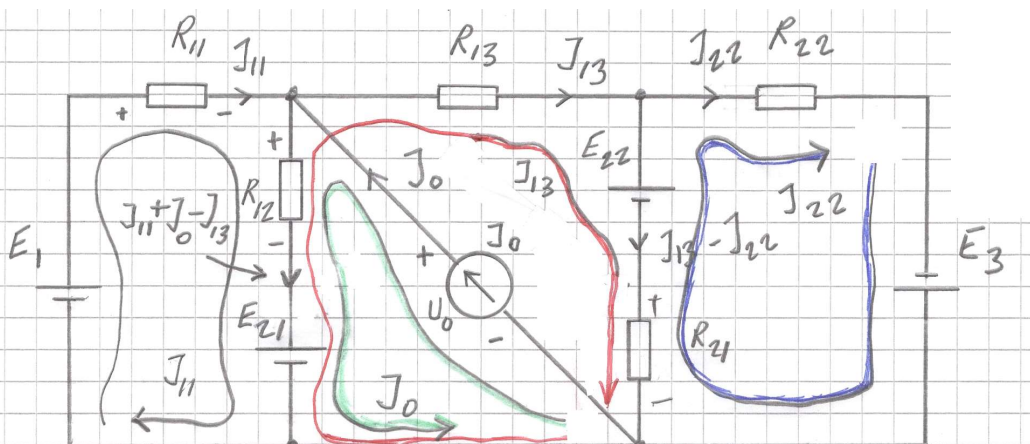Alternativ lösning med användande av slinganalys.



$$+E_1 - R_{11} J_{11} - R_{12} (J_{11} + J_0 - J_{13}) - E_{21} = 0$$

$$+E_{21} + R_{12} (J_{11} + J_0 - J_{13}) - R_{13} J_{13} - E_{22} - R_{24} (J_{13} - J_{22}) = 0$$

$$+U_0 - R_{12} (J_{11} + J_0 - J_{13}) - E_{21} = 0$$

$$+E_3 + R_{24} (J_{13} - J_{22}) + E_{22} - R_{22} J_{22} = 0$$

4 EKVATIONER OCH 4 OBEKANTA :

$$J_{11}, J_{13}, J_{22} \text{ och } U_0$$

(OBS! SPÄNNINGEN U_0 GENERERAS AV STRÖMGENERATORN J_0)

$$J_{11} = \dots \quad J_{13} = 2,0 \text{ A} \quad J_{22} = \dots \quad U_0 = \dots$$