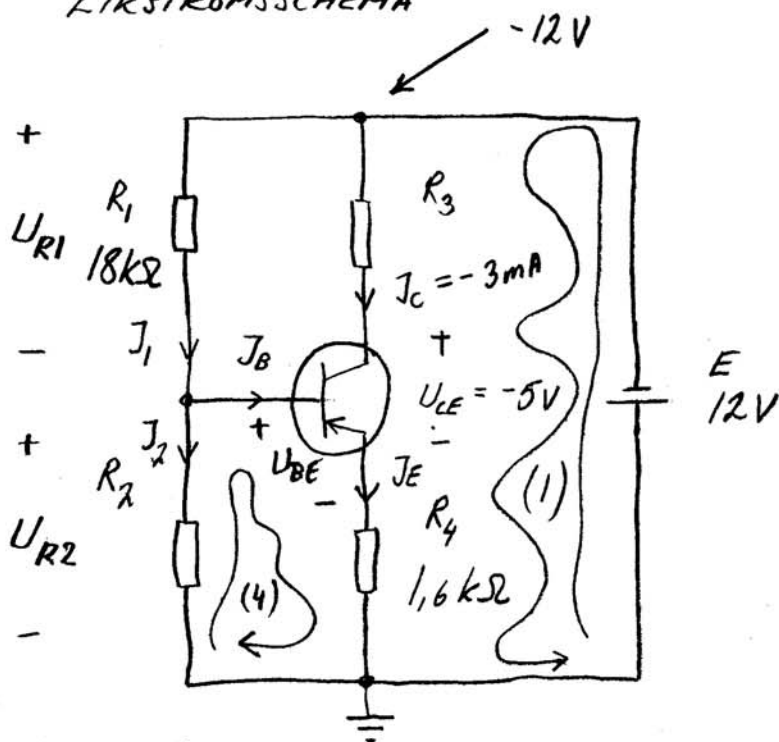


E4

LIKSTRÖMSSCHEMA



$$-E - R_3 J_C - U_{CE} - R_4 J_E \dots (1)$$

$$J_E = J_B + J_C \dots (2)$$

$$J_B = \frac{J_C}{h_{FE}}$$

$h_{FE} = 140$  ENLIGT  
 DATABLAD FÖR  
 BC177 SID 110.  
 (ALT. GRAFER SID 112)

$$\Rightarrow J_B = -22 \mu A$$

$$\text{INS 1 (2)} \Rightarrow J_E \approx -3 \text{ mA } (= J_C)$$

$$\text{INS 1 (1)} \Rightarrow \underline{R_3 = 733 \Omega}$$

$$R_2 = \frac{U_{R2}}{J_2} \dots (3)$$

$$+ U_{R2} - U_{BE} - R_4 J_E = 0 \dots (4)$$

$$\text{BILAGA SID 122} \Rightarrow U_{BE} = -0,67 \text{ V}$$

$$\text{INS 1 (4)} \Rightarrow U_{R2} = -5,47 \text{ V}$$

$$\left. \begin{aligned} J_2 &= J_1 - J_B = \frac{U_{R1}}{R_1} - J_B \\ -E &= U_{R1} + U_{R2} \Rightarrow U_{R1} = -6,53 \text{ V} \end{aligned} \right\} \rightarrow J_2 = -34 \mu\text{A}$$

$\underbrace{-E}_{-12\text{V}}$

$$\text{INS 1 (3)} \Rightarrow \underline{R_2 = 16,1 \text{ k}\Omega}$$