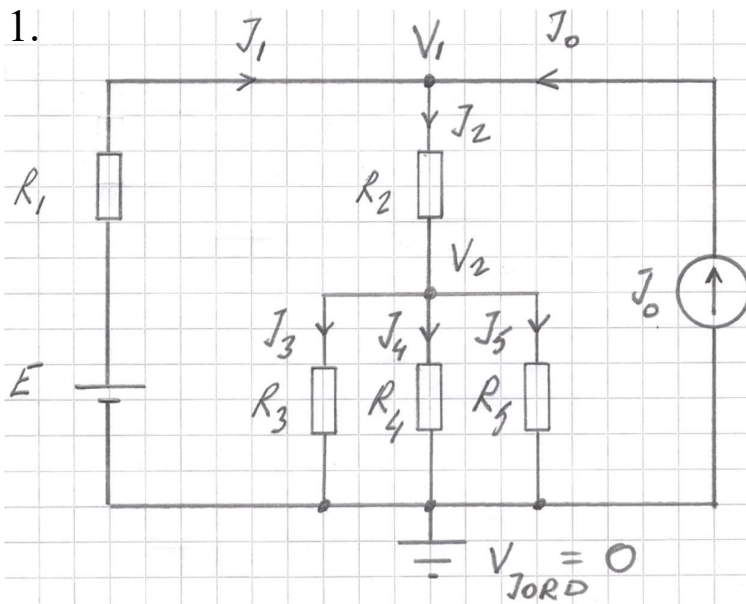


Lösningsförslag till tentamen TMEL08 Eltekniska system 2023-01-13

1.



$$\text{NOD 1 : } J_0 + J_1 - J_2 = 0$$

$$\text{NOD 2 : } J_2 - J_3 - J_4 - J_5 = 0$$


$$\text{NOD 1 : } J_0 + \frac{E - V_1}{R_1} - \frac{V_1 - V_2}{R_2} = 0$$

$$\text{NOD 2 : } \frac{V_1 - V_2}{R_2} - \frac{V_2 - 0}{R_3} - \frac{V_2 - 0}{R_4} - \frac{V_2 - 0}{R_5} = 0$$

$$\Rightarrow V_1 = +18 \text{ V} \quad V_2 = +12 \text{ V}$$

$$J_4 = \frac{V_2 - 0}{R_4} \Rightarrow \underline{J_4 = 3,0 \text{ mA}}$$

2a)

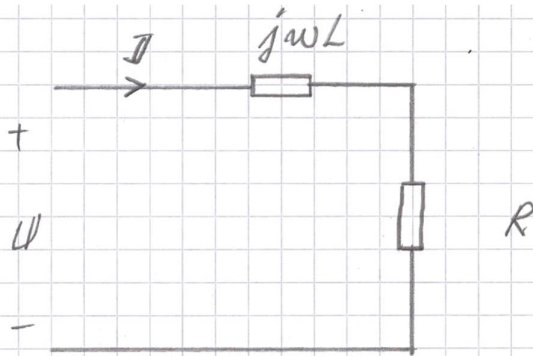

$$u(t) = 230\sqrt{2} \sin(100\pi t + 0^\circ) \text{ V} \rightarrow U = 230\sqrt{2} e^{j0^\circ} \text{ V}$$

$$I = \frac{U}{R + j\omega L} \Rightarrow$$

$$I = \frac{230\sqrt{2} e^{j0^\circ}}{24,0 + j100\pi \cdot 0,0573} =$$

$$= \frac{230\sqrt{2} e^{j0^\circ}}{\sqrt{24^2 + 18^2} \cdot e^{j \arctan \frac{18}{24}}} = 7,67\sqrt{2} e^{-j37^\circ} \text{ A}$$

$$\rightarrow i(t) = 7,67\sqrt{2} \sin(100\pi t - 37^\circ) \text{ A}$$

2b)

$$I = \frac{\hat{I}}{\sqrt{2}} = 7,67 \text{ A}$$

$$P = R I^2 \Rightarrow \underline{P = 1,41 \text{ kW}}$$

(Q<sub>L</sub>)

$$Q = X_L I^2 = |X_L = \omega L| = \underline{1,06 \text{ kVAR}}$$

$$S = \sqrt{P^2 + Q^2} \Rightarrow \underline{S = 1,76 \text{ kVA}}$$

ALTERNATIVT SÄTT ATT RÄKNA :

$$P = U \cdot I \cdot \cos \varphi$$

$$(Q_L) Q = U \cdot I \cdot \sin \varphi$$

$$S = U \cdot I$$

$$\varphi = \arg U - \arg I = 37^\circ$$

↑            ↑  
0°        -37°

$$U = \frac{\hat{U}}{\sqrt{2}} = 230 \text{ V}$$

2c)  $Q = Q_L - Q_C$

$$Q = 0 \Rightarrow Q_C = Q_L$$

$$Q_C = \frac{U^2}{X_C} = |X_C| = \frac{1}{\omega C} \Rightarrow U^2 \omega C$$

$$1,06 \cdot 10^3 = 230^2 \cdot 100\pi \cdot C \Rightarrow \underline{C = 63,7 \mu\text{F}}$$

2d)  $Q = 0 \Rightarrow S = P$  och  $\cos \varphi = 1 \Rightarrow \varphi = 0^\circ$

$$S = U \cdot I \Rightarrow 1,41 \cdot 10^3 = 230 \cdot I$$

$$\Rightarrow I = 6,13 \text{ A} \quad \hat{I} = 6,13 \sqrt{2} \text{ A}$$

$$\Rightarrow \underline{i(t) = 6,13 \sqrt{2} \sin(100\pi t) \text{ A}}$$


( $\varphi = 0^\circ$  INNEBÄR ATT  $\arg I = \arg U$ )

3a)

$$\frac{N_1}{N_2} = \frac{\hat{U}_1}{\hat{U}_2} \Rightarrow \frac{1500}{N_2} = \frac{230\sqrt{2}}{20}$$

$$\Rightarrow \underline{\underline{N_2 = 92}}$$

3b)

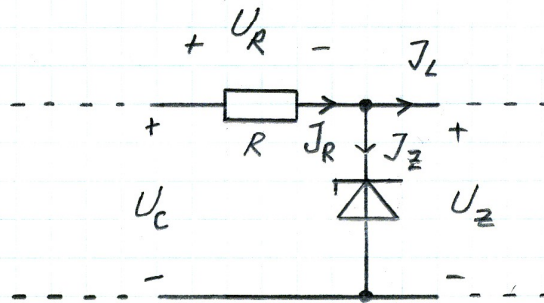

$$R = \frac{U_R}{J_R} = \frac{U_C - U_Z}{J_Z + J_L} \dots (1)$$

$$U_C \approx \hat{U}_Z - 2 \cdot 0,70 \Rightarrow U_C \approx 18,6 \text{ V}$$


$$(1) \Rightarrow R_{\text{MAX}} = \frac{18,6 - 12}{0,100 + 0,500} = 11 \Omega$$

$$P_{Z_{\text{max}}} = U_Z \cdot J_{Z_{\text{max}}} \Rightarrow J_{Z_{\text{max}}} = 833 \text{ mA}$$

$$(1) \Rightarrow R_{\text{MIN}} = \frac{18,6 - 12}{0,833 + 0} \approx 7,9 \Omega$$

ALLTSA VÄLJ 7,9 \Omega < R < 11 \Omega

3c)

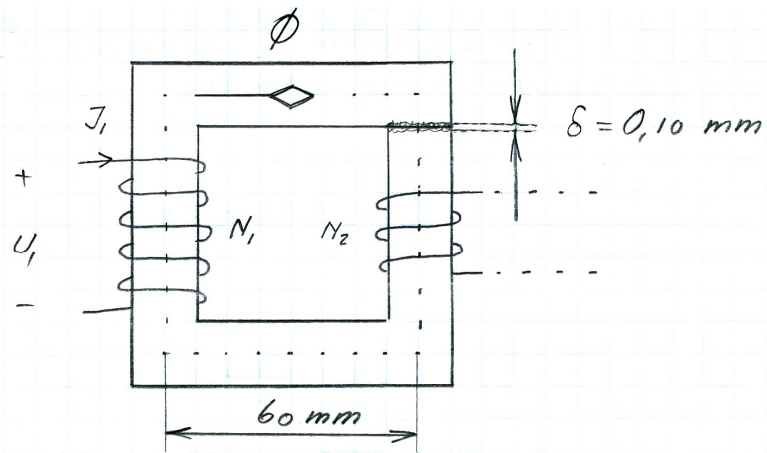

$$N_1 J_1 = R_m \cdot \Phi \dots (2)$$

JÄRNKÄRNANS MEDELLÄNGD  $l_{Fe} = 4 \cdot 60 = 240 \text{ mm}$

TVÄRSNITTSAREAN  $A_{Fe} = 15 \cdot 15 \text{ mm}^2 = 225 \text{ mm}^2$

$$R_{m_{Fe}} = \frac{l_{Fe}}{\mu_r \mu_0 A_{Fe}} \Rightarrow R_{m_{Fe}} \approx 169765 \frac{\text{A}}{\text{Vs}}$$

FÖRSUMMA LUFTGAPSSPRIDNINGEN  $\Rightarrow A_g \approx A_{Fe}$

$$R_{m_g} = \frac{\delta}{\mu_0 A_g} \Rightarrow R_{m_g} \approx 353678 \frac{\text{A}}{\text{Vs}}$$

FALL 1: INGET LUFTGAP  $\Rightarrow R_m = R_{m_{Fe}}$

FALL 2: LUFTGAP  $\Rightarrow R_m = R_{m_{Fe}} + R_{m_g}$

OM  $J_1$  ÄR KONSTANT  $\Rightarrow$

$$N_1 J_1 = R_{m_{Fe}} \cdot \Phi_1$$


$$N_1 J_1 = (R_{m_{Fe}} + R_{m_g}) \cdot \Phi_2 \Rightarrow$$

$$R_{mFe} \cdot \Phi_1 = (R_{mFe} + R_{mS}) \cdot \Phi_2 \quad \Rightarrow$$

$$\frac{\Phi_2}{\Phi_1} = \frac{R_{mFe}}{R_{mFe} + R_{mS}} \quad \Rightarrow \quad \frac{\Phi_2}{\Phi_1} \approx 0,32$$

{ ALLTSA,  $\Phi$  MINSKAR MED 68%  
{ (32% AV  $\Phi$  ÅTERSTÄR)

4a)

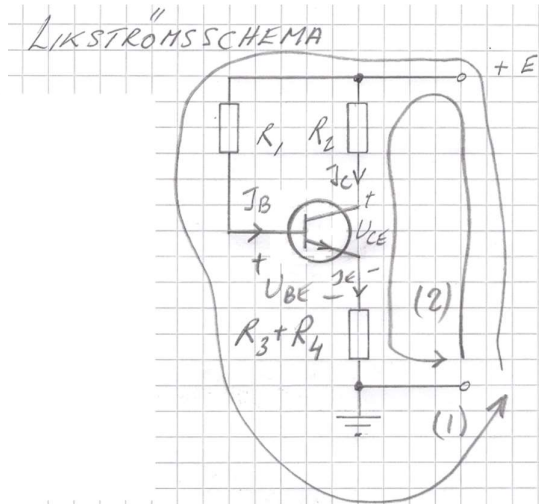

$$h_{FE} = \frac{I_C}{I_B} \Rightarrow I_B = 20 \mu A$$

$$I_E = I_B + I_C \rightarrow I_E = 4020 \mu A$$

$$+E - R_1 I_B - U_{BE} - (R_3 + R_4) I_E = 0 \dots (1)$$

$$(1) \rightarrow R_1 \approx 0,49 \text{ M}\Omega$$


4b)

$$+E - R_2 I_C - U_{CE} - (R_3 + R_4) I_E = 0 \dots (2)$$

$$(2) \rightarrow U_{CE} = 6,4 \text{ V}$$

4c)


EKVIVALENT SIGNALSCHEMA

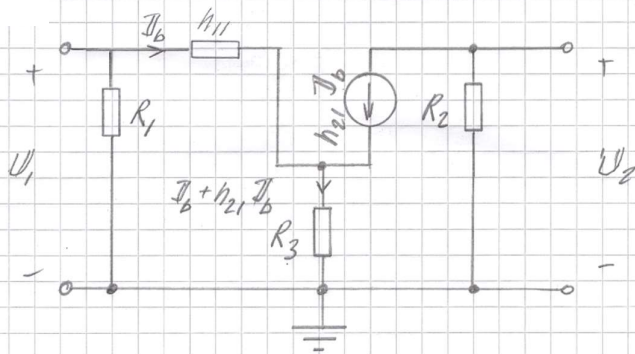

$$F = \frac{U_2}{U_1} = \frac{-h_{21} I_B R_2}{R_3 (I_B + h_{21} I_B) + h_{11} I_B}$$

$$|F| = 50 \Rightarrow \underline{R_3 = 10 \Omega} \Rightarrow \underline{R_4 = 380 \Omega}$$

5a)

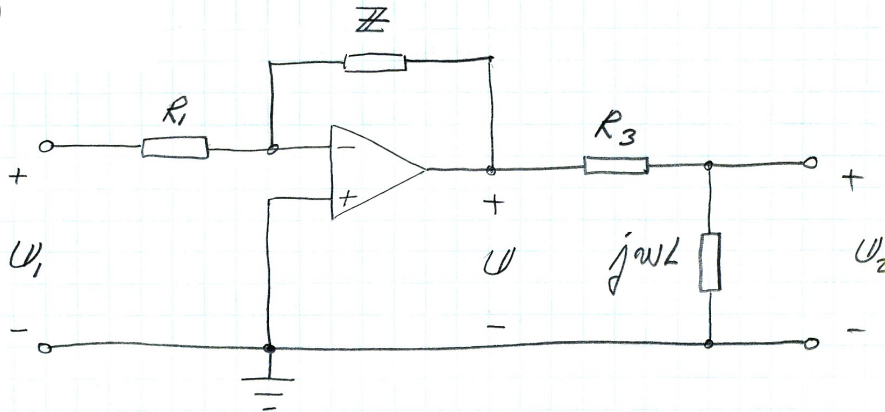

$$\frac{U_2}{U_1} = \frac{U_2}{U} \cdot \frac{U}{U_1} \dots (1)$$

$$U_2 = U \cdot \frac{j\omega L}{R_3 + j\omega L} \Rightarrow \frac{U_2}{U} = \frac{j\omega \cdot \frac{L}{R_3}}{1 + j\omega \cdot \frac{L}{R_3}}$$

$$\Rightarrow \frac{U_2}{U} = \frac{j \frac{\omega}{1587}}{1 + j \frac{\omega}{1587}}$$

$$\frac{U}{U_1} = - \frac{Z}{R_1} \quad \text{denn} \quad Z = \frac{\frac{1}{j\omega C} \cdot R_2}{\frac{1}{j\omega C} + R_2} =$$

$$= \frac{R_2}{1 + j\omega C R_2} \Rightarrow \frac{U}{U_1} = - \frac{R_2}{R_1} \cdot \frac{1}{1 + j\omega C R_2}$$

$$\Rightarrow \frac{U}{U_1} = -10 \cdot \frac{1}{1 + j \frac{\omega}{62500}}$$

$$(1) \Rightarrow \frac{U_2}{U_1} = -10 \cdot \frac{1}{1 + j \frac{\omega}{62500}} \cdot \frac{j \frac{\omega}{1587}}{1 + j \frac{\omega}{1587}}$$



5b)


$$\left| \frac{U_2}{U_1} \right| = 10 \cdot \frac{1}{\sqrt{1 + \left(\frac{\omega}{62500}\right)^2}} \cdot \frac{\omega}{1587 \sqrt{1 + \left(\frac{\omega}{1587}\right)^2}}$$

$$\text{OM } \omega \ll 1587 \frac{\text{RAD}}{\text{s}} \Rightarrow \left| \frac{U_2}{U_1} \right| \approx \frac{10}{1587} \cdot \omega$$

$$\text{OM } 1587 \frac{\text{RAD}}{\text{s}} < \omega < 62500 \frac{\text{RAD}}{\text{s}} \Rightarrow \left| \frac{U_2}{U_1} \right| = 10$$

$$\text{OM } \omega \gg 62500 \frac{\text{RAD}}{\text{s}} \Rightarrow \left| \frac{U_2}{U_1} \right| = \frac{625000}{\omega}$$


BODEDIAGRAM (AMPLITUDKURVA)

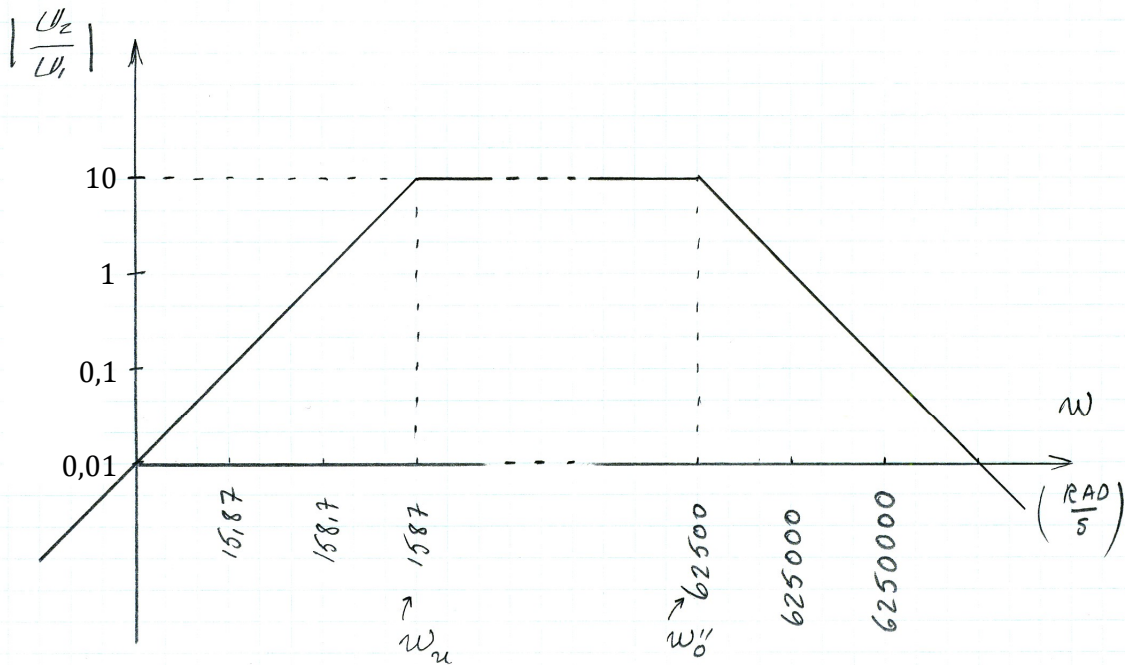

$$\omega_u = 2\pi f_u \Rightarrow \underline{f_u \approx 0,25 \text{ KHz}}$$


$$\omega'_0 = 2\pi f'_0 \Rightarrow \underline{f'_0 \approx 9,9 \text{ KHz}}$$

6. BEGYNNELSEVILLKOR DÅ  $t < 0$

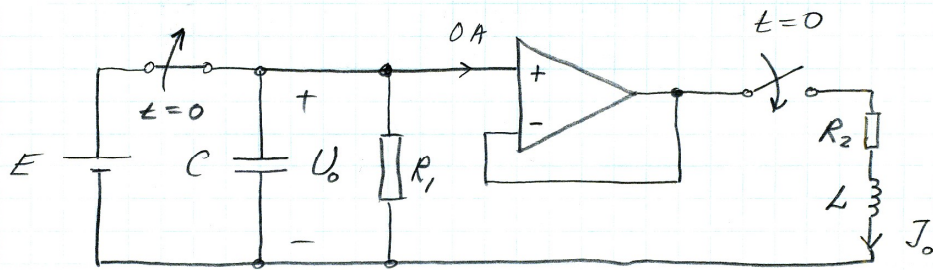

$$J_0 = 0 \text{ OCH } U_0 = E = 9,0 \text{ V}$$

OPERATORSHEMA ( $t \geq 0$ )

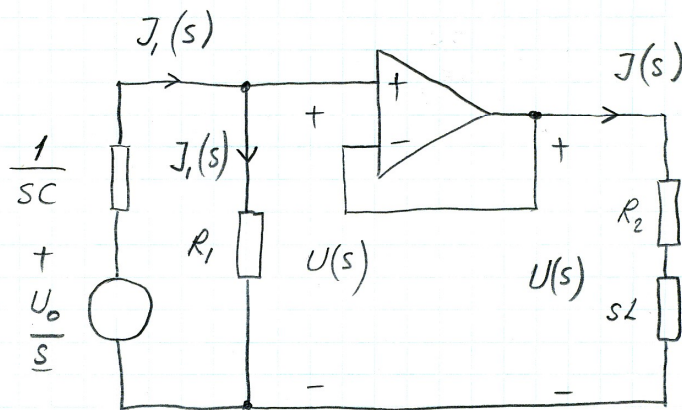

$$\frac{U_0}{s} - \frac{1}{sC} \cdot J_1(s) - R_1 J_1(s) = 0$$

$$J_1(s) = \frac{\frac{U_0}{s}}{\frac{1}{sC} + R_1} = \frac{U_0}{R_1} \cdot \frac{1}{s + \frac{1}{CR_1}}$$

$$U(s) = R_1 J_1(s) \Rightarrow U(s) = U_0 \cdot \frac{1}{s + \frac{1}{CR_1}}$$

$$\Rightarrow U(s) = 9,0 \cdot \frac{1}{s + 100} \rightsquigarrow \underline{\underline{u(t) = 9,0 \cdot e^{-100t} \text{ V}}}$$

$$J(s) = \frac{U(s)}{R_2 + sL} \Rightarrow$$

$$J(s) = \frac{9,0 \cdot \frac{1}{s+100}}{10 + s \cdot 0,200} = 45 \cdot \frac{1}{s+100} \cdot \frac{1}{s+50}$$

PARTIALBRÅKSUPPDELNING

$$\frac{45}{(s+100)(s+50)} = \frac{A}{s+100} + \frac{B}{s+50} =$$

$$= \frac{A(s+50) + B(s+100)}{(s+100)(s+50)}$$

$$A + B = 0$$

$$A = -0,90$$

$$50A + 100B = 45$$

$$B = 0,90$$

$$\Rightarrow J(s) = -0,90 \cdot \frac{1}{s+100} + 0,90 \cdot \frac{1}{s+50}$$

$$\rightsquigarrow \underline{\underline{\dot{i}(t) = 0,90 e^{-50t} - 0,90 e^{-100t} \quad A}}$$

ELLER ALTERNATIVT

$$J(s) = -0,90 \cdot \frac{1}{(s+75)+25} + 0,90 \cdot \frac{1}{(s+75)-25} =$$

$$= 1,8 \cdot \frac{25}{(s+75)^2 - 25^2} \rightsquigarrow$$

$$\underline{\underline{\dot{i}(t) = 1,8 \cdot e^{-75t} \cdot \sinh(25t) \quad A}}$$