

Digital IC Lecture

Adders

Deyu Tu, PhD

deyu.tu@liu.se


013-285851

Laboratory of Organic Electronics, Campus Norrköping

Outline

- Introduction
- The Binary Adder
- Single-bit Adder Design
- N-bit Adder Design


A Generic Digital Processor

 

Building Blocks

- **Arithmetic unit**
 - Bit-sliced datapath (adder, multiplier, shifter, comparator, etc.)
- **Memory**
 - RAM, ROM, Buffer, Shift registers
- **Control**
 - Finite state machine (PLA, random logic), Counters
- **Interconnect**
 - Switches, Arbiters, Bus


Bit-sliced Design

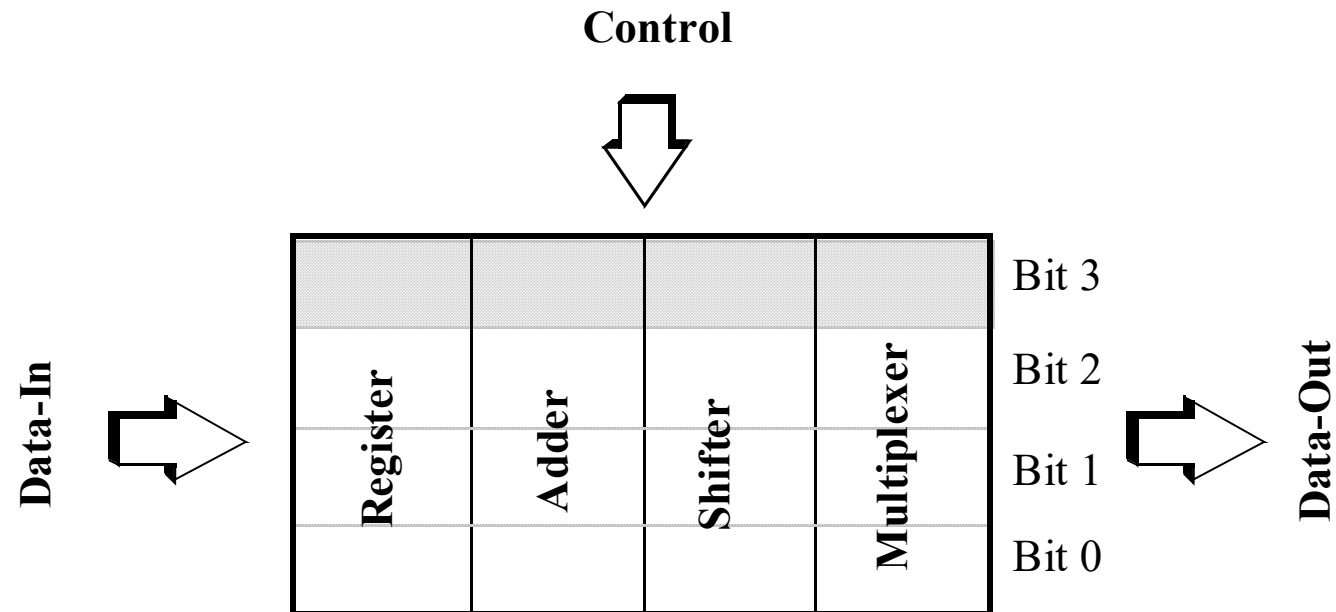

Tile identical processing elements

Bit-sliced Datapath

From register files / Cache / Bypass

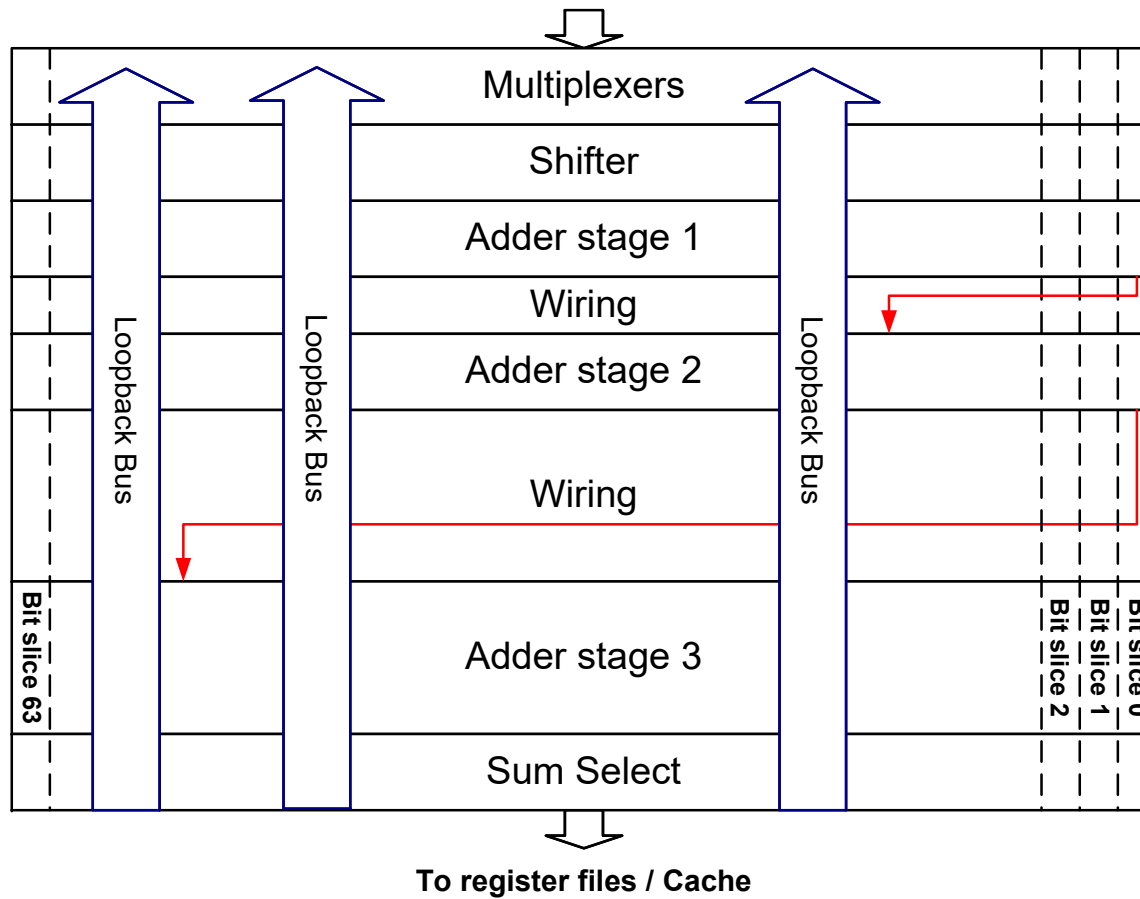

Half Adder


 


TABLE 11.1 Truth table for half adder


A	B	C_{out}	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

$$S = A \oplus B$$

$$C_{out} = A \cdot B$$

 


Full Adder

 

A	B	C_i	S	C_o	<i>Carry status</i>
0	0	0	0	0	delete
0	0	1	1	0	delete
0	1	0	1	0	propagate
0	1	1	0	1	propagate
1	0	0	1	0	propagate
1	0	1	0	1	propagate
1	1	0	0	1	generate
1	1	1	1	1	generate

The Binary Adder

 

$$\begin{aligned} S &= A \oplus B \oplus C_i \\ &= \bar{A}\bar{B}\bar{C}_i + \bar{A}B\bar{C}_i + \bar{A}B C_i + A\bar{B}C_i \\ C_o &= AB + BC_i + AC_i \end{aligned}$$

Express S and C_0 as a function of G, D, P

Three new variables which ONLY depend on A, B

$$\text{Generate (G)} = AB$$

$$\text{Delete (D)} = \bar{A} \bar{B}$$

$$\text{Propagate (P)} = A \oplus B$$

$$C_0(G, P) = G + PC_i$$


$$S(G, P) = P \oplus C_i$$

Can also derive expressions for S and C_0 based on D and P


Full Adder Design I

$$S = A \oplus B \oplus C$$


$$C_{out} = MAJ(A, B, C)$$

 


Full Adder Design II

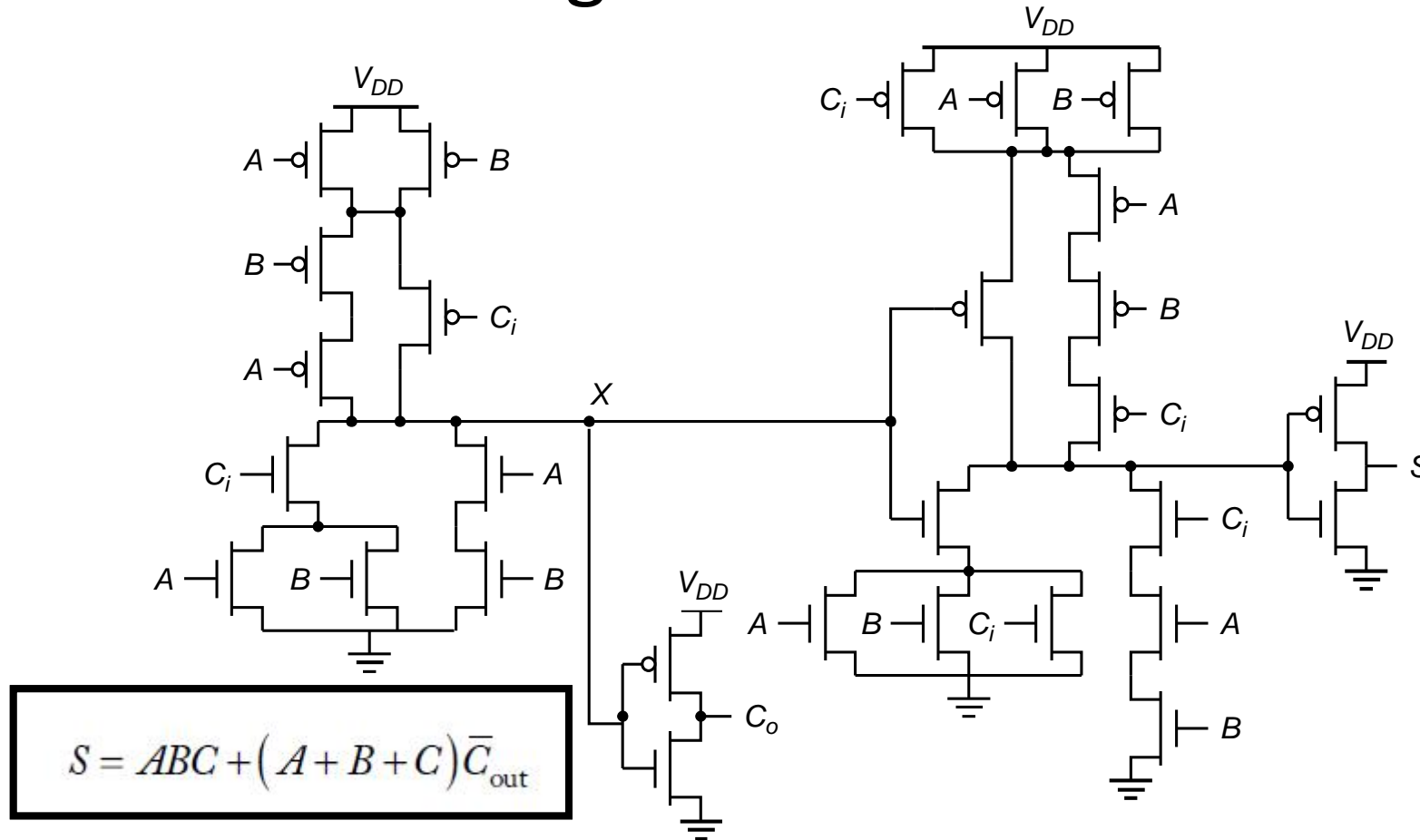


Full Adder Design III

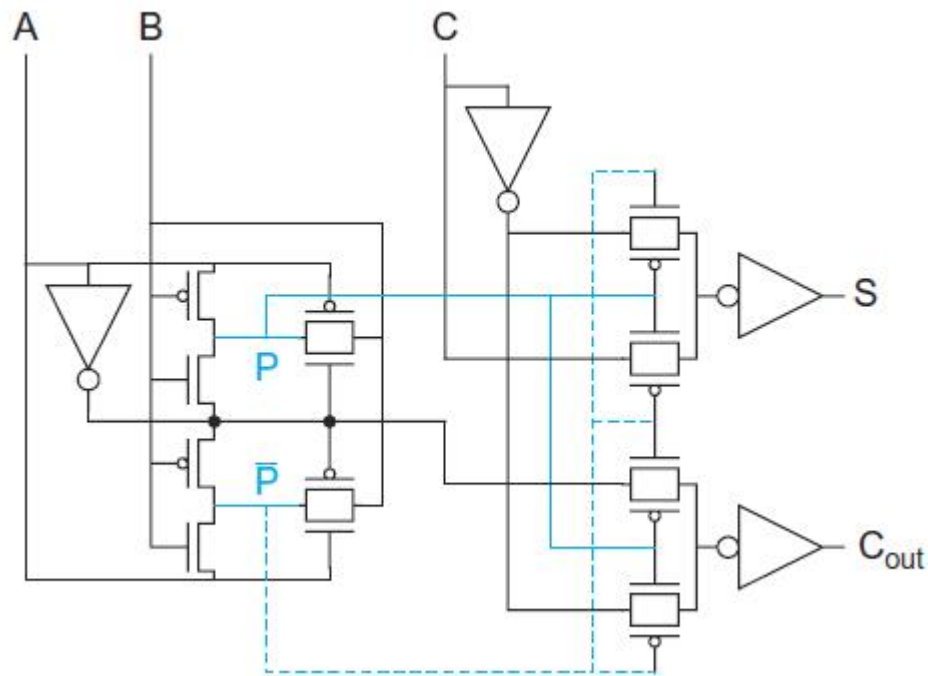

Full Adder Design IV

 

Full Adder Design V

 


Full Adder Design VI


Generate (G) = AB

Propagate (P) = A \oplus B

Delete = $\overline{A B}$

 

Inversion Property

 


$$\bar{S}(A, B, C_i) = S(\bar{A}, \bar{B}, \bar{C}_i)$$

$$\bar{C}_o(A, B, C_i) = C_o(\bar{A}, \bar{B}, \bar{C}_i)$$

Carry Propagate Adders


- N-bit Adder

 

$$\begin{array}{r}
 \text{C}_{out} \quad \text{C}_{in} \\
 \textcircled{0}0000 \\
 1111 \\
 +0000 \\
 \hline
 1111
 \end{array}$$

$$\begin{array}{r}
 \text{C}_{out} \quad \text{C}_{in} \\
 \textcircled{1}1111 \\
 1111 \quad \text{carries} \\
 +0000 \quad A_{4...1} \\
 \hline
 0000 \quad B_{4...1} \\
 \quad \quad \quad S_{4...1}
 \end{array}$$

The Ripple-Carry Adder

 


Worst case delay linear with the number of bits

$$t_d = O(N)$$

$$t_{\text{adder}} = (N-1)t_{\text{carry}} + t_{\text{sum}}$$


Goal: Make the fastest possible carry path circuit

Minimize Critical Path

 


Exploit Inversion Property
(2 different cells needed)


Carry Generation and Propagation

 



Manchester Carry Chain

 

Sizing Manchester Carry Chain

 


$$t_p = 0.69 \sum_{i=1}^N C_i \left(\sum_{j=1}^i R_j \right)$$

  Speed (normalized by $0.69RC$)


Area (in minimum size devices)

Carry-Bypass/Skip Adder

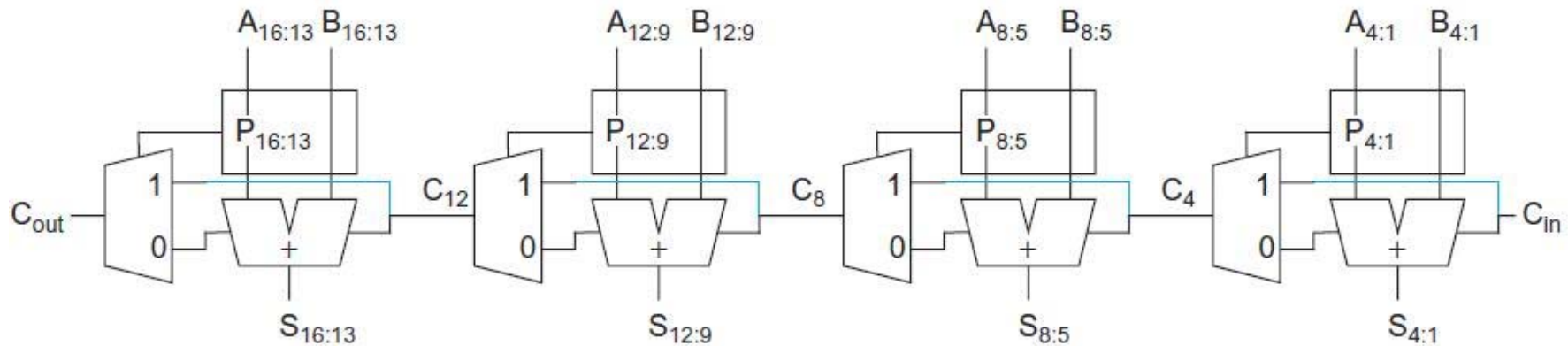- Carry-ripple is slow through all N stages
- Carry-bypass allow carry to skip over groups of n-bits




Carry-Bypass Adder

 

Idea: If (P_0 and P_1 and P_2 and $P_3 = 1$)
then $C_{o3} = C_0$, else "kill" or "generate".


Carry-Bypass Adder

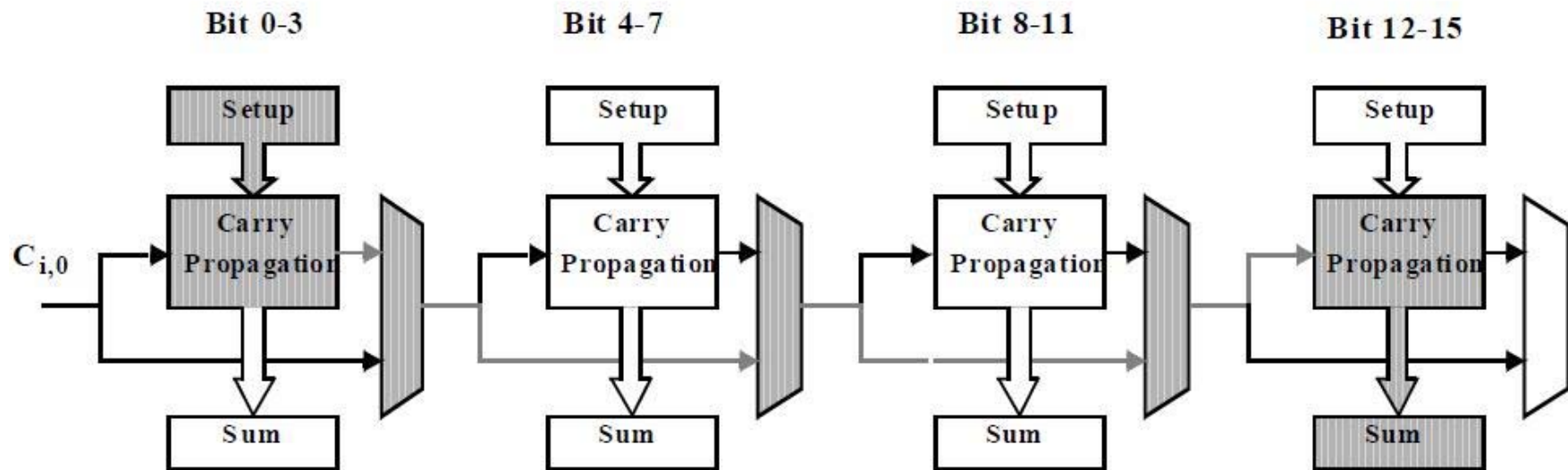

N bits, M bits per block


$$t_{adder} = t_{setup} + Mt_{carry} + (N/M-1)t_{bypass} + (M-1)t_{carry} + t_{sum}$$

Carry Ripple vs. Carry Bypass

 


Carry-Select Adder

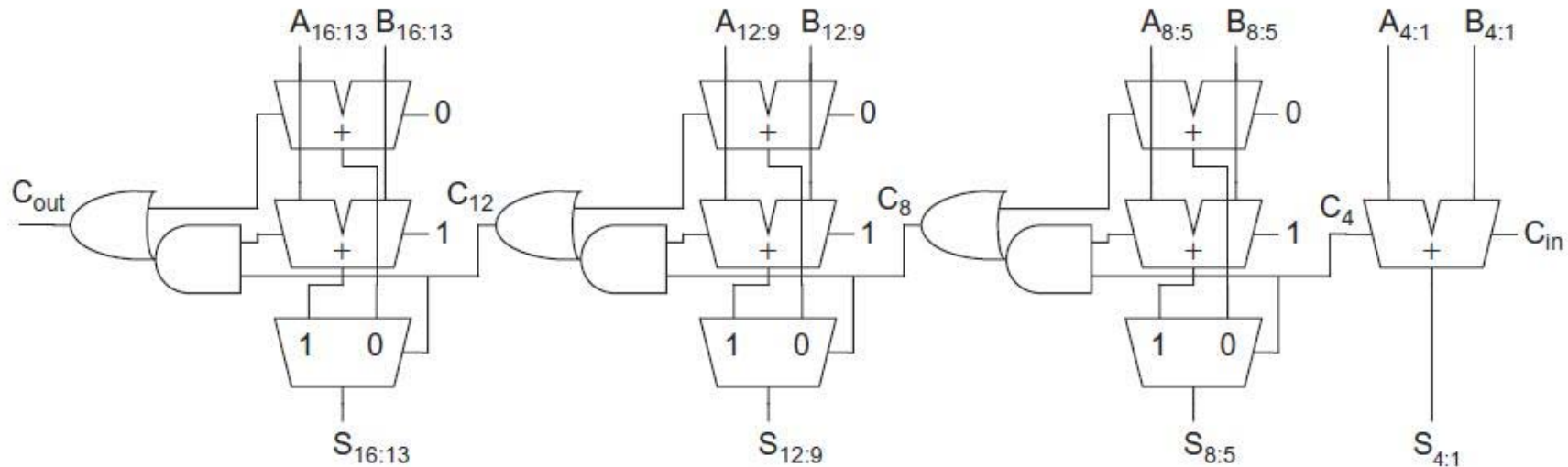
- Anticipate both possible values of the carry input
- Select the correct values when the carry input arrives




Carry-Select Adder

 

Carry-Select Adder: Critical Path

 


Linear Carry Select

 


$$t_{add} = t_{setup} + \left(\frac{N}{M}\right)t_{carry} + Mt_{mux} + t_{sum}$$

Square Root Carry Select

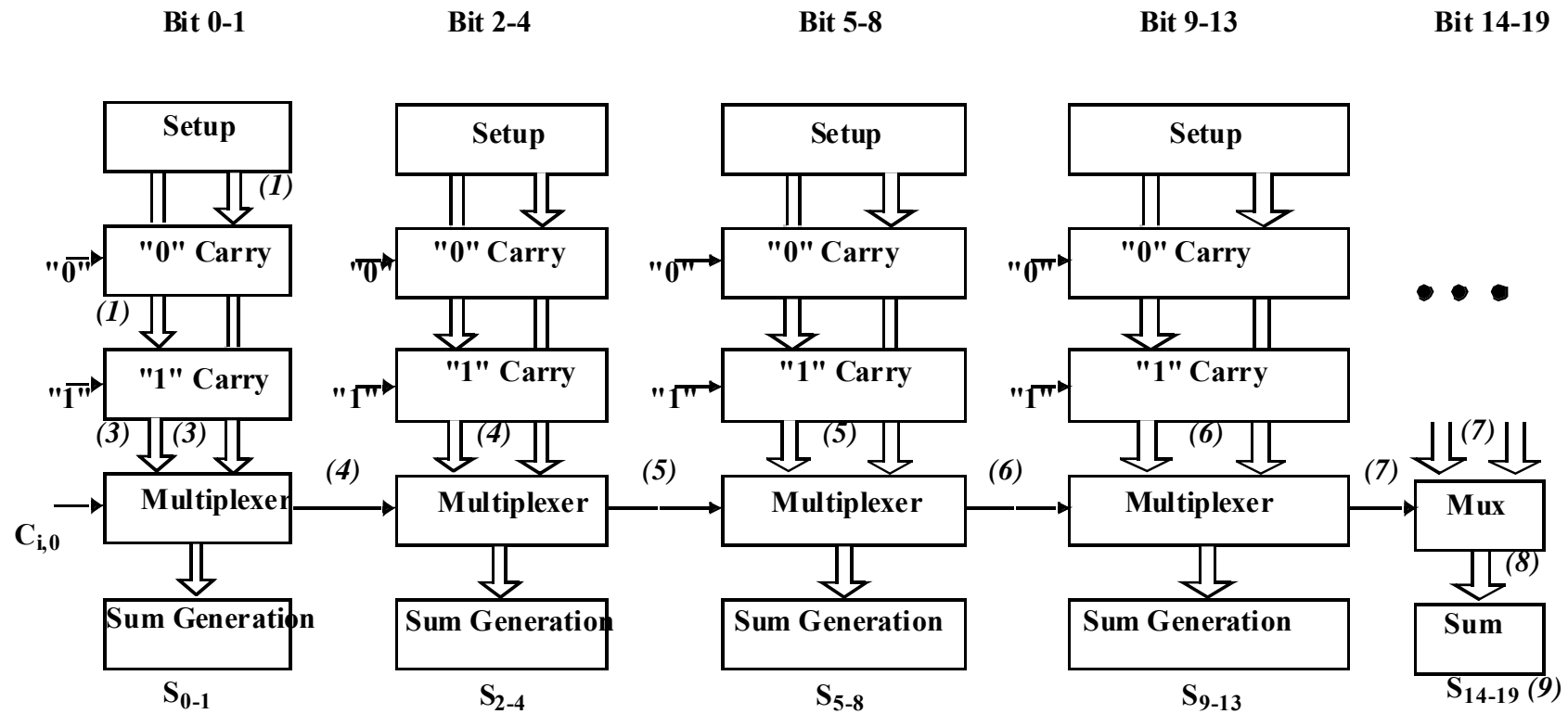


$$t_{add} = t_{setup} + P \cdot t_{carry} + (\sqrt{2N})t_{mux} + t_{sum}$$

Comparison of Adder Delay

 


Concept of Lookahead

 


$$C_{o,k} = f(A_k, B_k, C_{o,k-1}) = G_k + P_k C_{o,k-1}$$

Logarithmic Lookahead Adder

 

$$t_p \sim N$$

 

$$t_p \sim \log_2(N)$$

Carry Lookahead Trees

$$C_{o,0} = G_0 + P_0 C_{i,0}$$


$$C_{o,1} = G_1 + P_1 G_0 + P_1 P_0 C_{i,0}$$

$$C_{o,2} = G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_{i,0}$$

$$= (G_2 + P_2 G_1) + (P_2 P_1)(G_0 + P_0 C_{i,0}) = G_{2:1} + P_{2:1} C_{o,0}$$


Can continue building the tree hierarchically.

Tree Adder

 


16-bit radix-2 Kogge-Stone tree

Tree Adder

 


16-bit radix-4 Kogge-Stone Tree

Sparse Trees

 


16-bit radix-2 sparse tree with sparseness of 2

Brent-Kung Tree


 


Carry-Save Adder

 


x:		1	0	0	1	1	} <i>No carry used here</i>	
y:		1	1	0	0	1		
z:	+	0	1	0	1	1		
<hr/>		s:	0	0	0	0		1
c:	+	1	1	0	1	1	} <i>Extra adder</i>	
<hr/>		sum:	1	1	0	1		1

  To be compared with 2 std cascaded adders



Summary

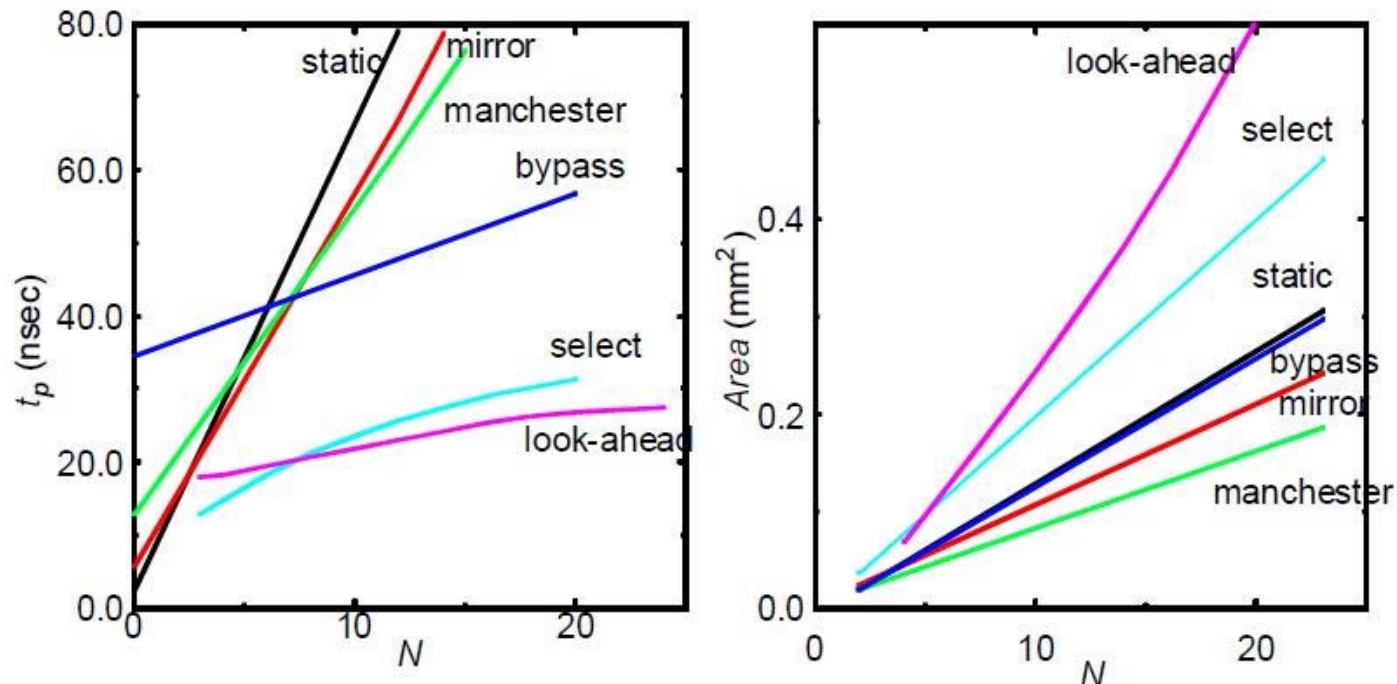

Design as a Trade-Off: Area – speed – power requirements should be verified in early design phases to choose the right structure

Reference

- *Digital Integrated Circuits*, by Jan M. Rabaey, et al.
- *CMOS VLSI Design*, by David Harris, et al.

www.liu.se