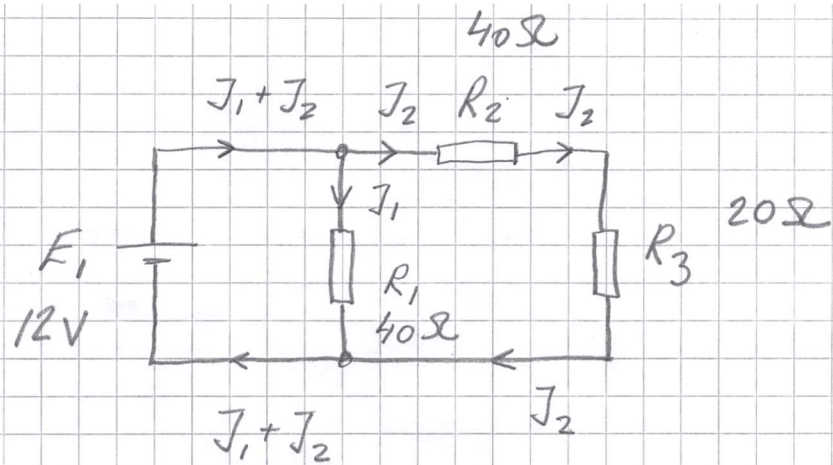


A0.1



OHMS LAG  $\Rightarrow$

$$J_1 = \frac{E_1}{R_1} \Rightarrow J_1 = 0,30 \text{ A}$$

$$J_2 = \frac{E_1}{R_2 + R_3} \Rightarrow J_2 = 0,20 \text{ A}$$