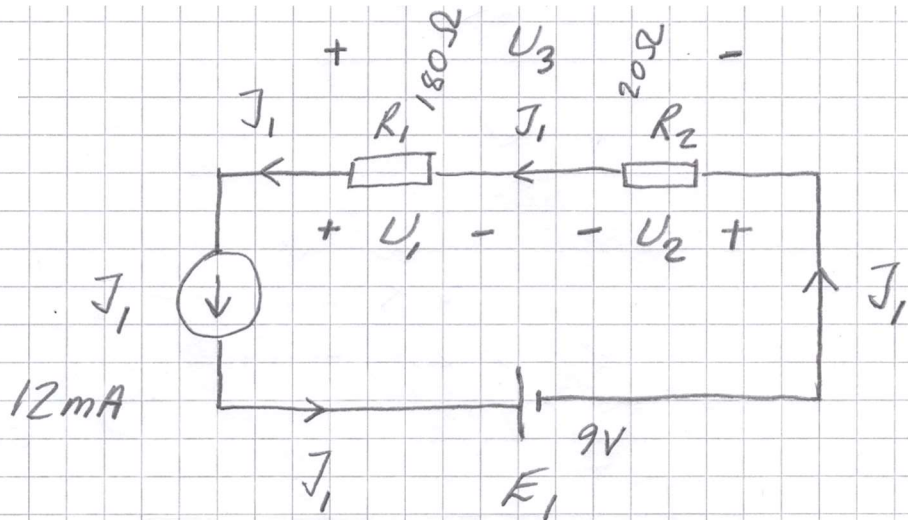


A0.4



$$U_3 = U_1 - U_2 \dots (1)$$

$$U_2 = R_2 \cdot J_1 \Rightarrow \underline{U_2 = 0,24 \text{ V}}$$

$$U_1 = -R_1 \cdot J_1 \Rightarrow \underline{U_1 = -2,16 \text{ V}}$$

$$(1) \Rightarrow \underline{U_3 = -2,4 \text{ V}}$$