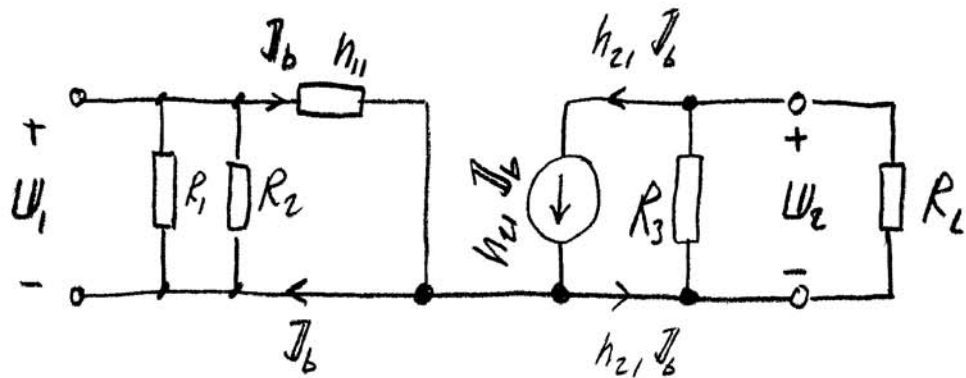


E12

EKVIVALENT SIGNALSCHEMA



$$F = \frac{U_2}{U_1} \dots (1)$$

$$U_2 = -h_{21} I_b \cdot \frac{R_3 \cdot R_L}{R_3 + R_L} \dots (2)$$

$$U_1 = h_{11} I_b \dots (3)$$

(2) OCH (3) INS I (1) →

$$F = \dots = \underline{\underline{-187}}$$

$$\frac{1}{Z_{in}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{h_{11}} \rightarrow Z_{in} = \underline{\underline{470 \Omega}}$$

$$Z_{out} = R_3 \rightarrow Z_{out} = \underline{\underline{4 k\Omega}}$$