

DIGITAL CIRCUITS

Exam TSEI03

Time:	Saturday 2017-01-07, 8:00—12:00
Place:	TER2
Teacher:	Jerzy Dąbrowski, phone 013-281224
Allowed aids:	Calculator and attached formulary (last two pages)
Max score:	70
Grades:	30 points for 3 40 points for 4 50 points for 5
Solutions:	Posted on the course web
Display:	Time and place will be posted with the LADOK results

1

- a) Which MOSFET in Figure 1 has the highest *threshold voltage* if V_{out} is positive? Motivate your answer. (2 p)
- b) What is an *overlap capacitance*? (2 p)
- c) What is the main difference in function between a *latch* and a *flip-flop* circuit? (2 p)
- d) Sketch the *voltage transfer characteristic* of an ideal inverter. Indicate V_{OL} , V_M , and V_{OH} and in the drawing. (4 p)

 


Figure 1. MOSFETs.

- 2 Consider a PMOS implemented in a 0.25 μm technology. The width-to-length ratio is $W/L = 2$ and the MOSFET is biased to $V_{GS} = -1.5\text{ V}$, $V_{DS} = -1.0\text{ V}$, and $V_{SB} = -0.50\text{ V}$. How large is the relative error in I_D if λ is assumed to be 0 instead of -0.10 V ? (10 p)

- 3 A cross section of a static CMOS inverter implemented in a 45 nm n-well CMOS technology is shown in Figure 2 below.

 


Figure 2. Cross section of a static CMOS inverter.

- a) Assign doping levels $p+$, $n+$, $p-$, and $n-$ to the objects indicated by letters A-H. (3 p)
- b) Assign the following names to the objects indicated by the numbers 1-14: field oxide, gate oxide, p-well contact, n-well contact, PMOS gate, PMOS drain, PMOS source, NMOS gate, NMOS source, NMOS drain contact, metal 1, metal 2, VIA. (7 p)

- 4 A dynamic D flip-flop should be implemented using C^2 MOS latches. Both the clock \emptyset and its complement \emptyset' are available.
- Draw the transistor schematic of a negative edge-triggered flip-flop. (6 p)
 - Assuming sharp edges of the clock phases, show that the flip-flop still works as a flip-flop even if there is clock skew delaying the complement of the clock. (6 p)

- 5 A realization of a logic function $F(A, B, C)$ is shown in Figure 3.


 


Figure 3. Transistor schematic of a logic gate.


- What logic style has been used? (2 p)
 - What logic function $F(A, B, C)$ has been implemented? (2 p)
 - What is purpose of the clocked MOSFETs? (2 p)
 - Can charge sharing occur in the circuit? Motivate your answer. (2 p)
 - Can charge leakage be a problem in the circuit? Motivate your answer. (2 p)
 - Size the devices so that the output resistance is the same as that of an inverter with an NMOS $W/L = 2$ and PMOS $W/L = 3$. (6 p)
- 6 Design a static CMOS gate that implements a Boolean function $F(A, B, C, D)$. You choose what function to implement, but it has to be a function of four variables.
- What logic function have you implemented? (2 p)
 - Draw the transistor schematic of your implementation. (6 p)
 - What input pattern(s) would give the lowest and highest equivalent pull-up or pull-down resistance? (4 p)

Equations for the MOS transistor

NMOS

 

PMOS

 

Definition of source (S) and drain (D)

NMOS: $V_S \leq V_D$ PMOS: $V_S \geq V_D$

Voltage notations

$$V_{GS} = V_G - V_S, \quad V_{DS} = V_D - V_S, \quad V_{SB} = V_S - V_B, \quad V_{GT} = V_{GS} - V_T$$

Threshold voltage

$$V_T = V_{T0} + \gamma(\sqrt{|V_{SB} - 2\Phi_F|} - \sqrt{2|\Phi_F|})$$

Unified model

NMOS: $V_{GT} \leq 0$ (PMOS: $V_{GT} \geq 0$) \Rightarrow Subthreshold region ($I_D \approx 0$)

$$\text{NMOS: } V_{GT} \geq 0 \text{ (PMOS: } V_{GT} \leq 0) \Rightarrow I_D = k' \frac{W}{L} V_{min} (|V_{GT}| - \frac{V_{min}}{2}) (1 + \lambda V_{DS})$$

$$V_{min} = \min(|V_{GT}|, |V_{DS}|, |V_{DSAT}|)$$

$$V_{min} = |V_{GT}| \Rightarrow \text{saturation region}$$

$$V_{min} = |V_{DS}| \Rightarrow \text{resistive (linear, triode) region } (\lambda = 0)$$

$$V_{min} = |V_{DSAT}| \Rightarrow \text{velocity saturation region}$$

V_{DSAT} dependency on channel length

$$V_{DSAT} = L_{\xi_c}^{\pm}$$

Subthreshold region

$$\text{NMOS: } V_{GT} \leq 0 \Rightarrow I_{Dn} = I_{0n} \frac{W}{L} e^{\frac{q(V_{GSn} - V_{Tn})}{nkT}} \left(1 - e^{-\frac{qV_{DSn}}{kT}} \right) (1 + \lambda_n V_{DSn})$$

$$\text{PMOS: } V_{GT} \geq 0 \Rightarrow I_{Dp} = I_{0p} \frac{W}{L} e^{\frac{q(V_{GSp} - |V_{Tp}|)}{nkT}} \left(1 - e^{-\frac{qV_{DSp}}{kT}} \right) (1 + \lambda_p V_{DSp})$$

Model parameters for 0.25 μm CMOS devices

Parameters for drain current calculations

	V_{T0} [V]	γ [$\sqrt{\text{V}}$]	V_{DSAT} [V]	k' [$\mu\text{A}/\text{V}^2$]	λ	Φ_F [V]
NMOS	0.43	0.40	0.63	115	0.06	-0.30
PMOS	-0.40	-0.40	-1.00	-30	-0.10	0.30

Parameters for capacitance calculations

	C_{ox} [$\text{fF}/\mu\text{m}^2$]	C_O [$\text{fF}/\mu\text{m}$]	C_j [$\text{fF}/\mu\text{m}^2$]	m_j	ϕ_b [V]	C_{jsw} [$\text{fF}/\mu\text{m}$]	m_{jsw}	ϕ_{bsw} [V]
NMOS	6	0.31	2.0	0.50	0.9	0.28	0.44	0.9
PMOS	6	0.27	1.9	0.48	0.9	0.22	0.32	0.9

Gate capacitance

Overlap capacitance

$$C_{GSO} = C_{GDO} = C_{ox} x_d W = C_O W$$

Channel capacitance

$$C_{GC} = C_{GCB} + C_{GCS} + C_{GCD}$$

Condition	C_{GCB}	C_{GCS}	C_{GCD}
$V_{GTn} \leq 0, V_{GTp} \geq 0$	$C_{ox} WL$	0	0
$V_{GTn} > 0, V_{GTp} < 0, V_{DS} \leq V_{GT} $	0	$C_{ox} WL/2$	$C_{ox} WL/2$
$V_{GTn} > 0, V_{GTp} < 0, V_{GT} \leq V_{DS} $	0	$2C_{ox} WL/3$	0

Junction capacitance

Junction capacitance as function of voltage

$$C_j(V) = \frac{C_{j0}}{(1 - V/\phi_0)^m}$$

Average capacitance during transition from V_1 to V_2

$$C_{eq} = K_{eq} C_{j0} = \frac{-\phi_0^m}{(V_2 - V_1)(1 - m)} [(\phi_0 - V_2)^{(1-m)} - (\phi_0 - V_1)^{(1-m)}] C_{j0}$$

Dynamic power consumption

$$P = \alpha f C_{tot} V_{dd}^2$$

Switch functions

$$S_N = \overline{F(A, B, \dots)}, S_P = F(\overline{A}, \overline{B}, \dots)$$

Boolean algebra

De Morgans' theorem

$$\overline{\overline{X + Y + Z + \dots}} = \overline{\overline{XYZ\dots}} = \overline{\overline{X}} + \overline{\overline{Y}} + \overline{\overline{Z}} + \dots$$

Expansion in sum

$$f(X, Y, Z, \dots) = Xf(1, Y, Z, \dots) + \overline{X}f(0, Y, Z, \dots)$$

Expansion in product

$$f(X, Y, Z, \dots) = [X + f(0, Y, Z, \dots)][\overline{X} + f(1, Y, Z, \dots)]$$

Transmission line

Characteristic impedance

$$Z_0 = \sqrt{L/c}$$

Velocity of wave

$$v = 1/\sqrt{LC}$$

Reflection coefficient for a transmission line (Z_0) terminated by a load (Z_L)

$$\Gamma = (Z_L - Z_0)/(Z_L + Z_0)$$

Elmore delay

P_i = "the path between node 0 and i ".

$P_{ij} = P_i \cap P_j$ = "the common part of the paths P_i and P_j ".

R_{ij} = "the sum of all resistances in P_{ij} ".

Time constant from node 0 to i : $\tau_{di} = \sum_{j=0}^n R_{ij} C_j$. Propagation delay: $t_{pi} \approx 0.69\tau_{di}$.

Sizing of cascaded inverters

For minimal propagation delay find the best solution to $1 = e^{(1+\gamma/k)/k}$, where

k = "tapering factor", N = "number of inverters", $F = C_L/C_{g1} = k^N$ and $\gamma = C_{int1}/C_{g1}$.