 


DIGITAL CIRCUITS

Exam TSEI03


Time:	Wednesday 2017-10-18, 8:00—12:00
Place:	TER2
Teacher:	Mark Vesterbacka, phone 013-281324
Allowed aids:	Calculator and attached formulary (last two pages)
Max score:	70
Grades:	30 points for 3 40 points for 4 50 points for 5
Solutions:	Posted on the course web
Display:	Time and place will be posted with the LADOK results

- 1 a) What terminal is the *source* and what terminal is the *drain* in a MOSFET? (2 p)
- b) What is the maximal value on the *gate capacitance* of a MOSFET? (2 p)
- c) Describe the operation of an *NMOS inverter*. (2 p)
- d) What restrictions are imposed on the flip-flop inputs to avoid *metastability*? (2 p)
- e) Draw a *six-transistor SRAM cell* schematic. (2 p)
- 2 Consider a NMOS implemented in a $0.25\ \mu\text{m}$ technology. The width-to-length ratio is $W/L = 2$ and the MOSFET is biased to $V_{GS} = 1.0\ \text{V}$, $V_{DS} = 1.5\ \text{V}$, and $V_{SB} = 0.50\ \text{V}$. How large is the relative error in I_D if λ is assumed to be 0 instead of $0.06\ \text{V}^{-1}$? (10 p)
- 3 Draw the voltage transfer characteristic of a typical CMOS inverter. Indicate V_{IL} , V_{OL} , V_{IH} , V_{OH} , and V_M in the drawing. (6 p)
- 4 Design a static CMOS circuit with function $F = (A+B)\cdot(C+D)$. Size all transistor nets to have similar output resistance as an inverter with $W_p/L_p = 4$ and $W_n/L_n = 3$. (10 p)
- 5 Design a complementary pass transistor logic circuit with function $F(A, B) = \overline{AB} + A\overline{B}$. Assume that complements to A and B are available.
- a) Implement the circuit with at most four NMOSFETs plus two inverters. (8 p)
- b) Suggest a solution to reduce the short-circuit currents of the inverters. (4 p)
- 6 Design a 16-bit ROM with the memory content $\{1,1,0,0,1,0,0,1,1,0,1,1,0,1,1,0\}$ and a one-bit output.
- a) What would be a good aspect ratio of the ROM matrix to have a short delay? (2 p)
- b) Draw a block diagram over the complete ROM containing row and column decoders, precharged bit line pull-ups, and memory matrix. (4 p)
- c) Draw the transistor schematic of the NOR ROM matrix. (4 p)
- 7 A dynamic gate with two parasitic capacitors C_x and C_y indicated is shown in the figure to the right.
- a) What logic function has been implemented? (2 p)
- b) Explain the operation of the circuit. (4 p)
- c) Explain how charge sharing may occur. (3 p)
- d) Suggest a way of mitigating the problem with charge sharing. (3 p)




Equations for the MOS transistor

NMOS

 

PMOS

 

Definition of source (S) and drain (D)

NMOS: $V_S \leq V_D$ PMOS: $V_S \geq V_D$

Voltage notations

$V_{GS} = V_G - V_S$, $V_{DS} = V_D - V_S$, $V_{SB} = V_S - V_B$, $V_{GT} = V_{GS} - V_T$

Threshold voltage

$$V_T = V_{T0} + \gamma(\sqrt{|V_{SB} - 2\Phi_F|} - \sqrt{2|\Phi_F|})$$

Unified model

NMOS: $V_{GT} \leq 0$ (PMOS: $V_{GT} \geq 0$) \Rightarrow Subthreshold region ($I_D \approx 0$)

NMOS: $V_{GT} \geq 0$ (PMOS: $V_{GT} \leq 0$) $\Rightarrow I_D = k' \frac{W}{L} V_{min} (|V_{GT}| - \frac{V_{min}}{2}) (1 + \lambda V_{DS})$

$V_{min} = \min(|V_{GT}|, |V_{DS}|, |V_{DSAT}|)$

$V_{min} = |V_{GT}| \Rightarrow$ saturation region

$V_{min} = |V_{DS}| \Rightarrow$ resistive (linear, triode) region ($\lambda = 0$)

$V_{min} = |V_{DSAT}| \Rightarrow$ velocity saturation region

V_{DSAT} dependency on channel length

$$V_{DSAT} = L_{\xi_c}^{\xi_c}$$

Subthreshold region

NMOS: $V_{GT} \leq 0 \Rightarrow I_{Dn} = I_{0n} \frac{W}{L} e^{\frac{q(V_{GS} - V_{Tn})}{nkT}} \left(1 - e^{-\frac{qV_{DS}}{kT}} \right) (1 + \lambda_n V_{DSn})$

PMOS: $V_{GT} \geq 0 \Rightarrow I_{Dp} = I_{0p} \frac{W}{L} e^{\frac{q(V_{SG} - |V_{Tp}|)}{nkT}} \left(1 - e^{-\frac{qV_{SDp}}{kT}} \right) (1 + \lambda_p V_{SDp})$

Model parameters for 0.25 μm CMOS devices

Parameters for drain current calculations

	V_{T0} [V]	γ [$\sqrt{\text{V}}$]	V_{DSAT} [V]	k' [$\mu\text{A}/\text{V}^2$]	λ	Φ_F [V]
NMOS	0.43	0.40	0.63	115	0.06	-0.30
PMOS	-0.40	-0.40	-1.00	-30	-0.10	0.30

Parameters for capacitance calculations

	C_{ox} [$\text{fF}/\mu\text{m}^2$]	C_O [$\text{fF}/\mu\text{m}^2$]	C_j [$\text{fF}/\mu\text{m}^2$]	m_j	Φ_b [V]	C_{jsw} [$\text{fF}/\mu\text{m}$]	m_{jsw}	Φ_{bsw} [V]
NMOS	6	0.31	2.0	0.50	0.9	0.28	0.44	0.9
PMOS	6	0.27	1.9	0.48	0.9	0.22	0.32	0.9

Gate capacitance

Overlap capacitance

$$C_{GSO} = C_{GDO} = C_{ox} x_d W = C_O W$$

Channel capacitance

$$C_{GC} = C_{GCB} + C_{GCS} + C_{GCD}$$

Condition	C_{GCB}	C_{GCS}	C_{GCD}
$V_{GTn} \leq 0, V_{GTp} \geq 0$	$C_{ox} WL$	0	0
$V_{GTn} > 0, V_{GTp} < 0, V_{DS} \leq V_{GT} $	0	$C_{ox} WL/2$	$C_{ox} WL/2$
$V_{GTn} > 0, V_{GTp} < 0, V_{GT} \leq V_{DS} $	0	$2C_{ox} WL/3$	0

Junction capacitance

Junction capacitance as function of voltage

$$C_j(V) = \frac{C_{j0}}{(1 - V/\phi_0)^m}$$

Average capacitance during transition from V_1 to V_2

$$C_{eq} = K_{eq} C_{j0} = \frac{-\phi_0^m}{(V_2 - V_1)(1 - m)} [(\phi_0 - V_2)^{(1-m)} - (\phi_0 - V_1)^{(1-m)}] C_{j0}$$

Dynamic power consumption

$$P = \alpha f C_{tot} V_{dd}^2$$

Switch functions

$$S_N = \overline{F(A, B, \dots)}, S_P = F(\overline{A}, \overline{B}, \dots)$$

Boolean algebra

De Morgans' theorem

$$\overline{\overline{X + Y + Z + \dots}} = \overline{\overline{XYZ\dots}} = \overline{\overline{X}} + \overline{\overline{Y}} + \overline{\overline{Z}} + \dots$$

Expansion in sum

$$f(X, Y, Z, \dots) = Xf(1, Y, Z, \dots) + \overline{X}f(0, Y, Z, \dots)$$

Expansion in product

$$f(X, Y, Z, \dots) = [X + f(0, Y, Z, \dots)][\overline{X} + f(1, Y, Z, \dots)]$$

Transmission line

Characteristic impedance

$$Z_0 = \sqrt{L/c}$$

Velocity of wave

$$v = 1/\sqrt{LC}$$

Reflection coefficient for a transmission line (Z_0) terminated by a load (Z_L)

$$\Gamma = (Z_L - Z_0)/(Z_L + Z_0)$$

Elmore delay

P_i = "the path between node 0 and i ".

$P_{ij} = P_i \cap P_j$ = "the common part of the paths P_i and P_j ".

R_{ij} = "the sum of all resistances in P_{ij} ".

Time constant from node 0 to i : $\tau_{di} = \sum_{j=0}^n R_{ij} C_j$. Propagation delay: $t_{pi} \approx 0.69\tau_{di}$.

Sizing of cascaded inverters

For minimal propagation delay find the best solution to $1 = e^{(1+\gamma/k)/k}$, where

k = "tapering factor", N = "number of inverters", $F = C_L/C_{g1} = k^N$ and $\gamma = C_{int1}/C_{g1}$.