

Solutions to exam in TSEI03 Digital Circuits 2018-10-22

1.

- The signal must be kept stable a time before (*setup time*) and a time after (*hold time*) the clock edge that initiates the memory state.
- An *overlap capacitance* is the capacitance between the part of the gate and the source or drain areas that overlaps.
- A *noise margin* is defined as the difference between the best output voltage and the worst input voltage that can be accepted. It measures the amount of noise that can be added to a node between two cascaded, identical gates without ruining the function.
- Charge leakage* will ruin the level when the gate is in dynamic state for a long time. Hence a minimal sample frequency is required for proper operation.
- The gain is less than one for voltages up to V_{IL} and for voltages above V_{IH} . Hence noise is attenuated for these voltages.

2.

- V_d is given by the voltage drop over the resistor due to constant current

$$V_d = V_{dd} - RI$$

$$V_d = V_{dd} - RI = 2.5 - 10 \cdot 10^3 \cdot 50 \cdot 10^{-6} \text{ V} = \underline{2.0 \text{ V}}$$

Small R causes small voltage drop over R , and large over MOSFET. Try with saturated operating mode and solve for V_{GS}

$$I_d = \frac{k' W}{2 L} (V_{GS} - V_T)^2 = 50 \mu\text{A} \Rightarrow V_{GS} = \sqrt{I_d \frac{2 L}{k' W}} + V_T =$$
$$= \sqrt{50 \cdot 10^{-6} \frac{2}{115 \cdot 10^{-6}} \frac{0.25}{2.5}} + 0.43 \text{ V} = 0.72 \text{ V}$$

Find V_s

$$V_s = V_G - V_{GS} = \underline{1.28 \text{ V}}$$

Check operation mode

$$V_{\min} = \min(V_{GT}, V_{DS}, V_{DSAT}) = \min(0.72 - 0.43, 2.0 - 1.28, 0.63) = V_{GT}$$

The MOSFET is saturated.

- Find V_d

$$V_d = V_{dd} - RI = 2.5 - 30 \cdot 10^3 \cdot 50 \cdot 10^{-6} \text{ V} = \underline{1.0 \text{ V}}$$

Large R causes large voltage drop over R , and small over MOSFET. Try with linear operating mode and solve for V_s

$$I_d = k' \frac{W}{L} \left[(V_{GS} - V_T) V_{DS} - \frac{V_{DS}^2}{2} \right] = k' \frac{W}{L} \left[(V_G - V_S - V_T)(V_D - V_S) - \frac{(V_D - V_S)^2}{2} \right] = 50 \mu\text{A}$$

$$\Leftrightarrow 115 \cdot 10^{-6} \frac{2.5 \cdot 10^{-6}}{0.25 \cdot 10^{-6}} \left[(2.0 - V_S - 0.43)(1.0 - V_S) - \frac{(1.0 - V_S)^2}{2} \right] = 50 \cdot 10^{-6} \Leftrightarrow$$

$$V_S^2 - 3.14V_S + \frac{2361}{1150} = 0 \Leftrightarrow V_S \approx 1.57 \pm 0.64 \text{ V} \Rightarrow$$

$$V_S \approx \underline{0.93 \text{ V}}$$

Check operation mode

$$V_{\min} = \min(V_{GT}, V_{DS}, V_{DSAT}) = \min(2.0 - 0.93 - 0.43, 1.0 - 0.93, 0.63) = V_{DS} = 0.07 \text{ V}$$

The MOSFET is linear.

3.

- Sheet resistance has unit Ω/square since the resistance is constant for a square of wire in a certain layer. This property is due to that the wire has constant thickness.
- Resistance R of the wire as a function of length L

$$R = \frac{L}{W} R_{sq} \Rightarrow L = \frac{R}{R_{sq}} W \approx 57 \mu\text{m}$$

- Total wire capacitance C

$$C = W_{\min} LC_{\text{area}} + 2LC_{\text{edge}} \approx 13 \text{ fF}$$

4.

- Simplify the logic function to contain as few variable entries as possible


$$F = AB + AC = A(B + C)$$

Since a static CMOS gate is inverting, we can design the function as the inverted output $G = F'$ and add an inverter to the output to obtain F

Switch nets for function G

$$G = \overline{A(B+C)} \Rightarrow \begin{cases} S_p = G(\overline{A}, \overline{B}, \overline{C}) = \overline{\overline{A(B+C)}} = A + BC \\ S_n = \overline{G(A, B, C)} = A(B+C) \end{cases}$$


Transistor schematic

 


b) The worst-case resistance occurs when a single path conducts. A common sizing strategy is to design the widths of every single conduction path to be equal (when possible). Using $R \propto L/W$, the aspect ratios shown by the transistors in the schematic above can be calculated using this strategy

5.

 - a) Pass transistor logic
- b) $A \neq B, C = 1$ yields a short circuit between A and $B \Rightarrow$ output F will be undefined.
- c) Below is a binary tree representing the function and its simplification in two steps.




 d) The optimized pass transistor circuit is shown below.



6.

 - a) Transistor schematic of a six-transistor CMOS SRAM cell



- b) For example, to store $\bar{Q} = 0$, $Q = 1$, WL is initially set to 0, \bar{BL} is set to 0, and BL is set to 1. Then WL is pulsed high long enough to allow the crosscoupled inverter pair to change state hence storing the wanted content.
- c) To read the cell content, WL is initially 0 while \bar{BL} and BL are precharged to 1. Then WL is pulsed high long enough for the sense amplifier to detect the voltage drop on the bit-line that is pulled towards 0 by the weak transistors in the cell. Finally the sense amplifier amplifies the voltage difference to a full swing 0 and the result is output.
- d) For proper write operation, the ratio between the pull-up PMOSFET and the select NMOSFET must be designed low enough to allow a 0 on the bit-line change the state of the corresponding memory node. For proper read operation, the ratio between the pull-down NMOSFET and the select NMOSFET needs to be designed high enough to prevent the memory node from changing state from 0 to 1 when the cell is connected to the precharged bit-line.