

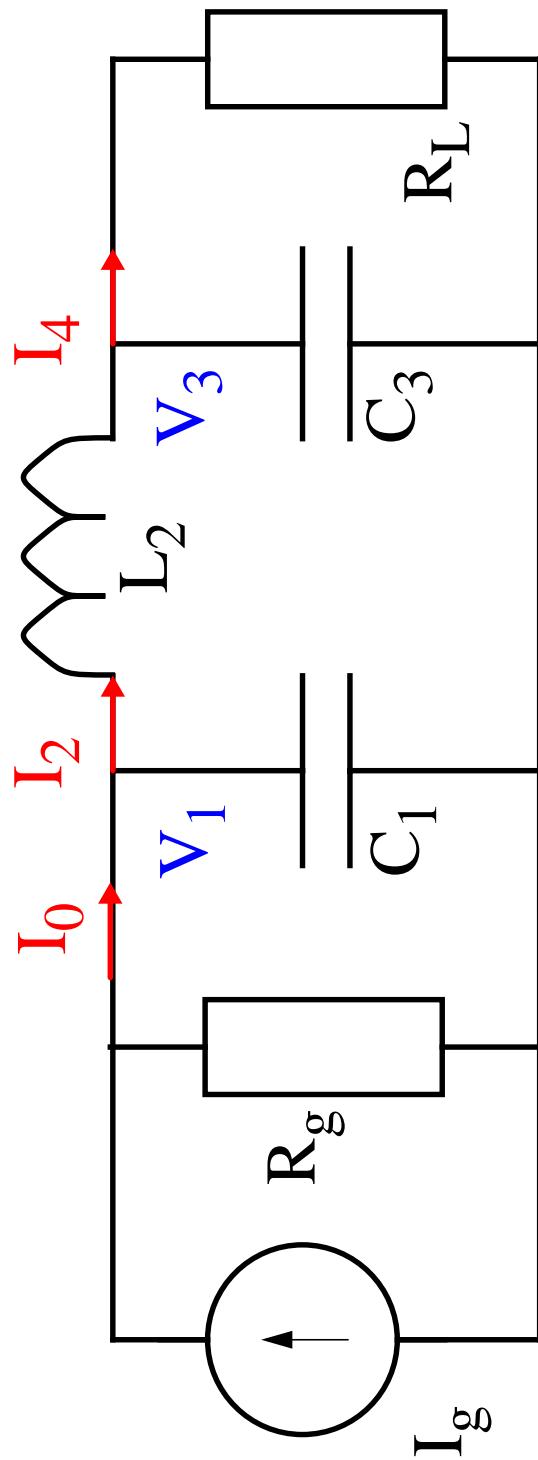


Slides for lecture 9**Ladder reference filter**


Modified signal flow graph

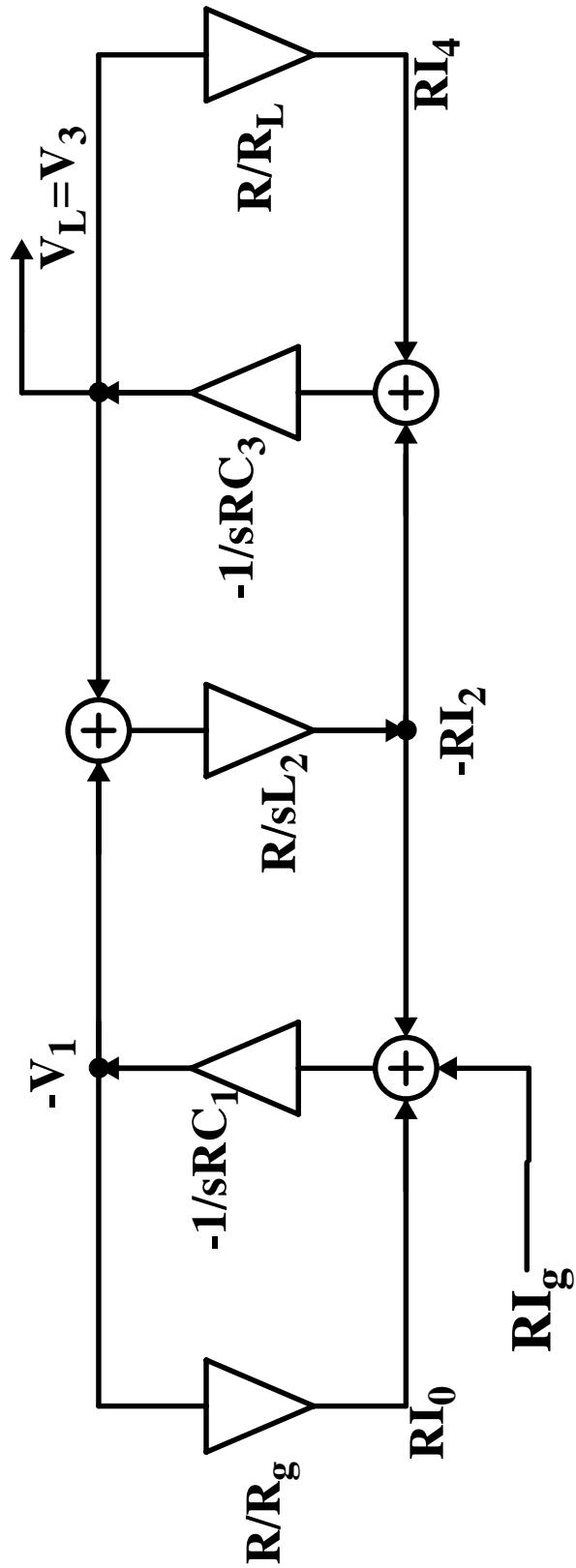


LDI transf. of Butterworth leapfrog

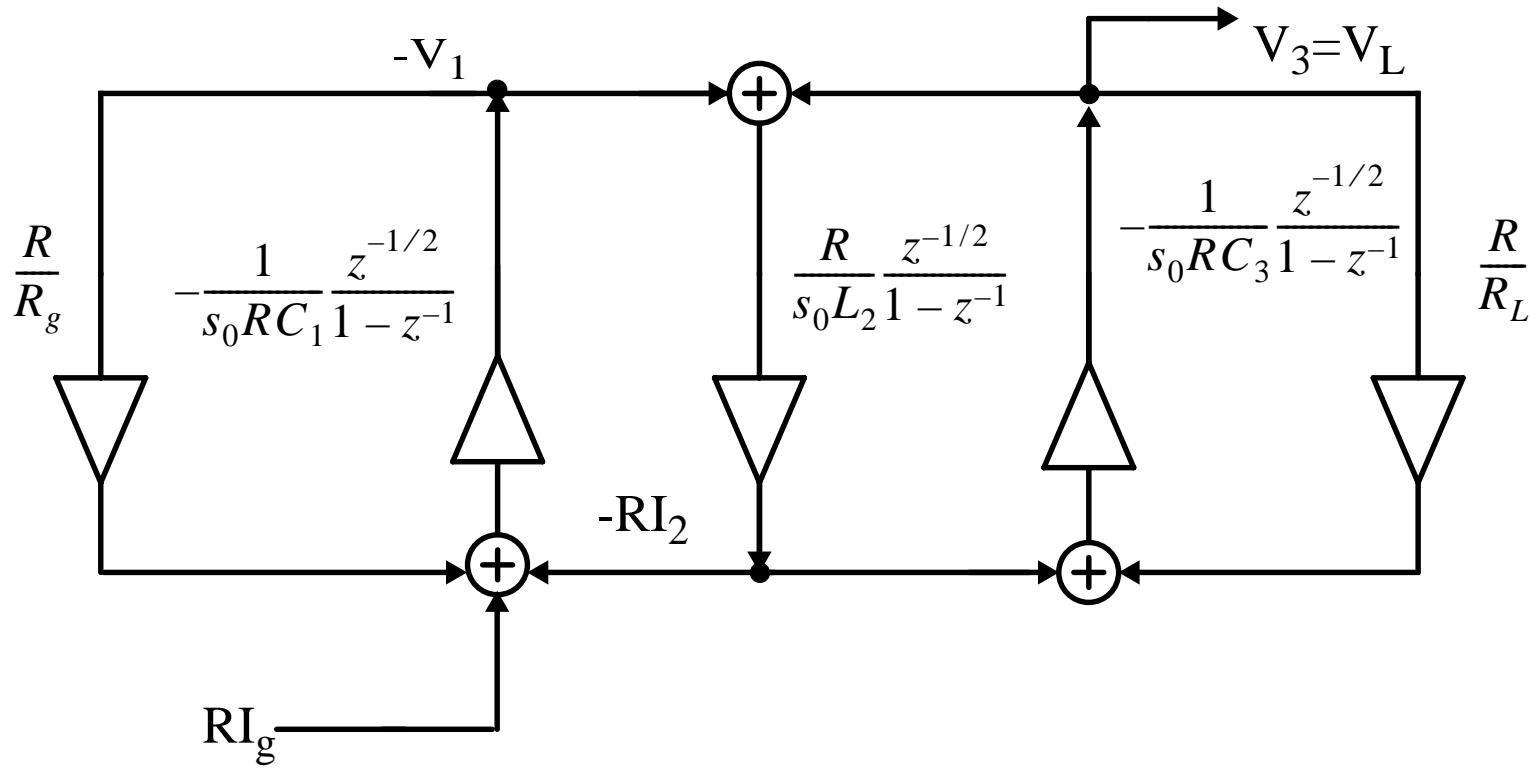


Modified signal flow graph

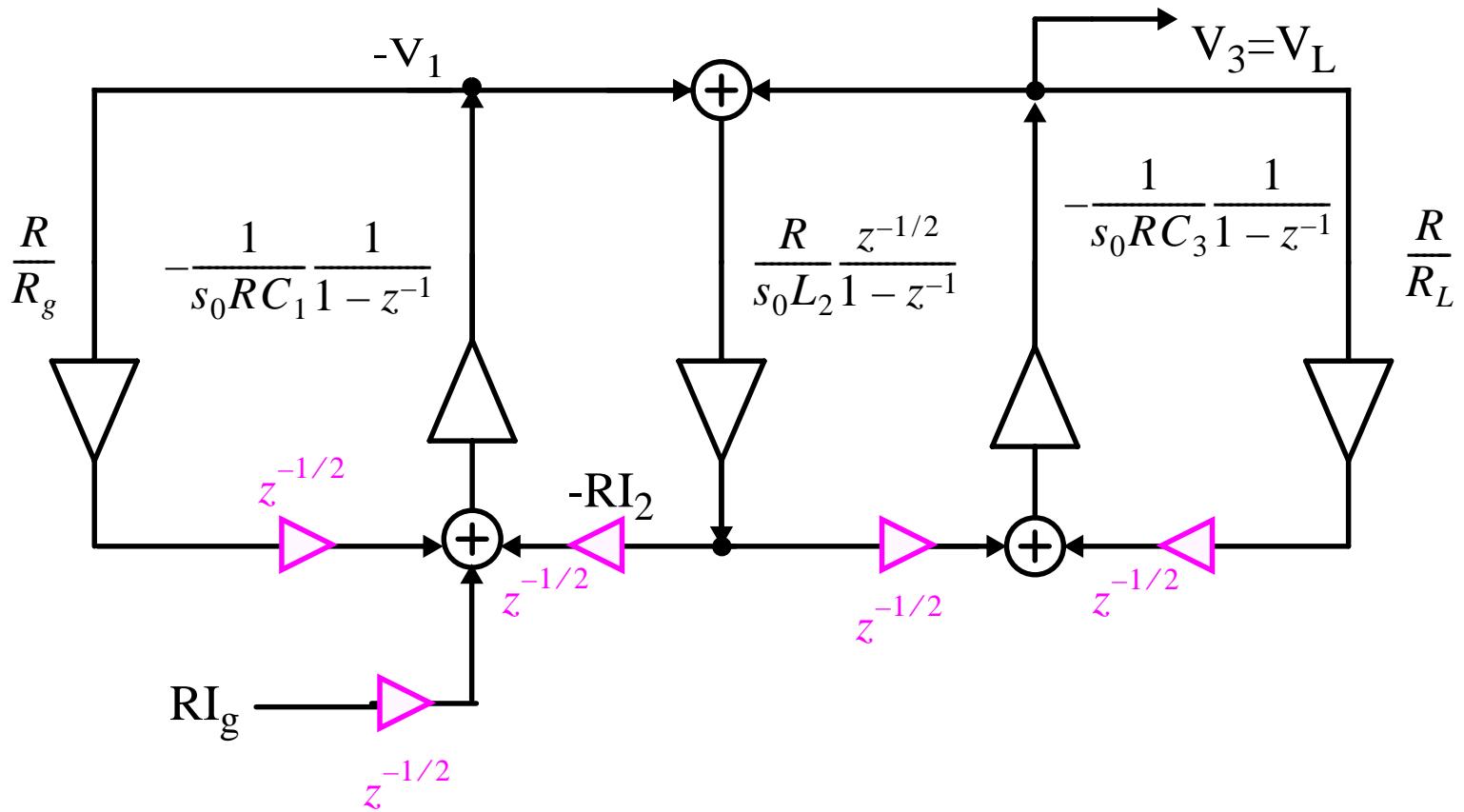

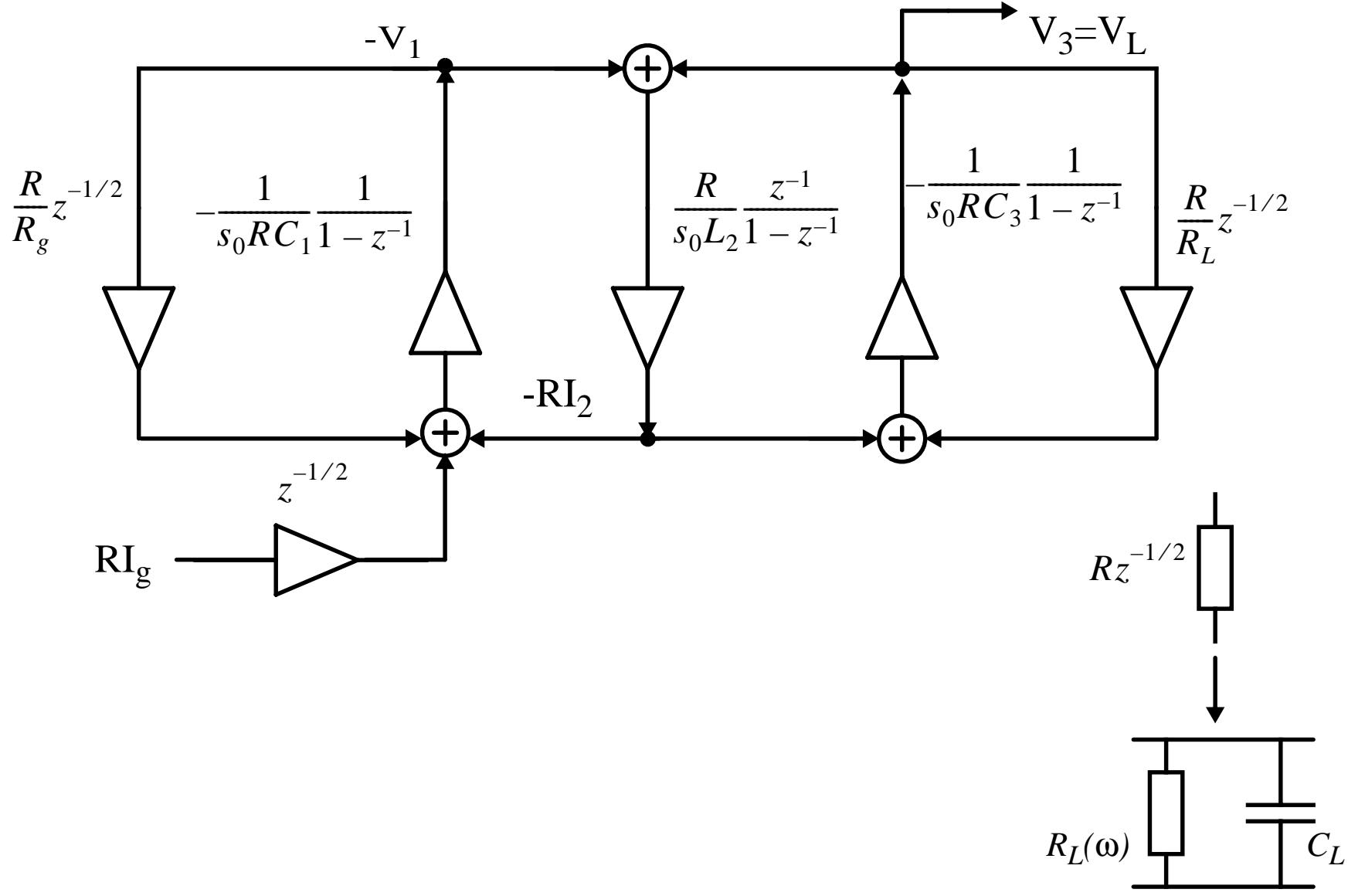LDI transf. of Butterworth leapfrog filter




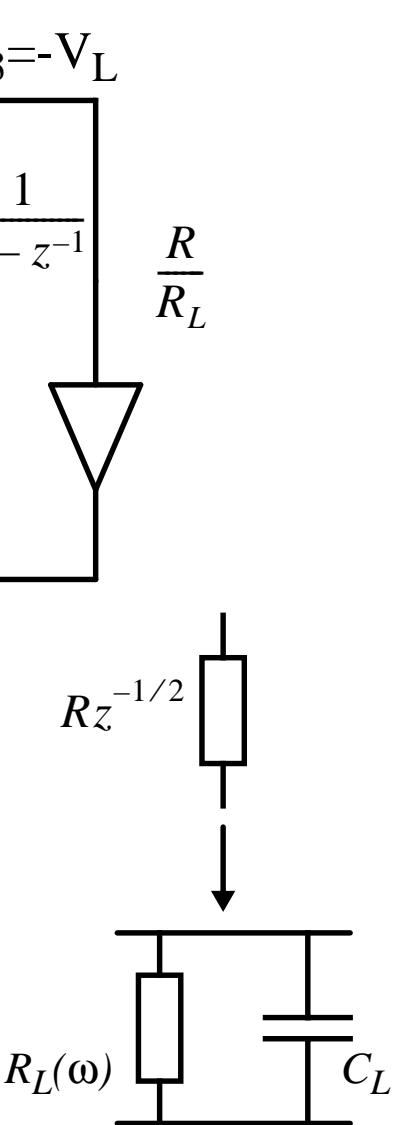Elimination of signal-dependent resistances




$$C_1' = C_1 - \frac{1}{2s_o R_g}$$

$$C_3' = C_3 - \frac{1}{2s_o R_L}$$

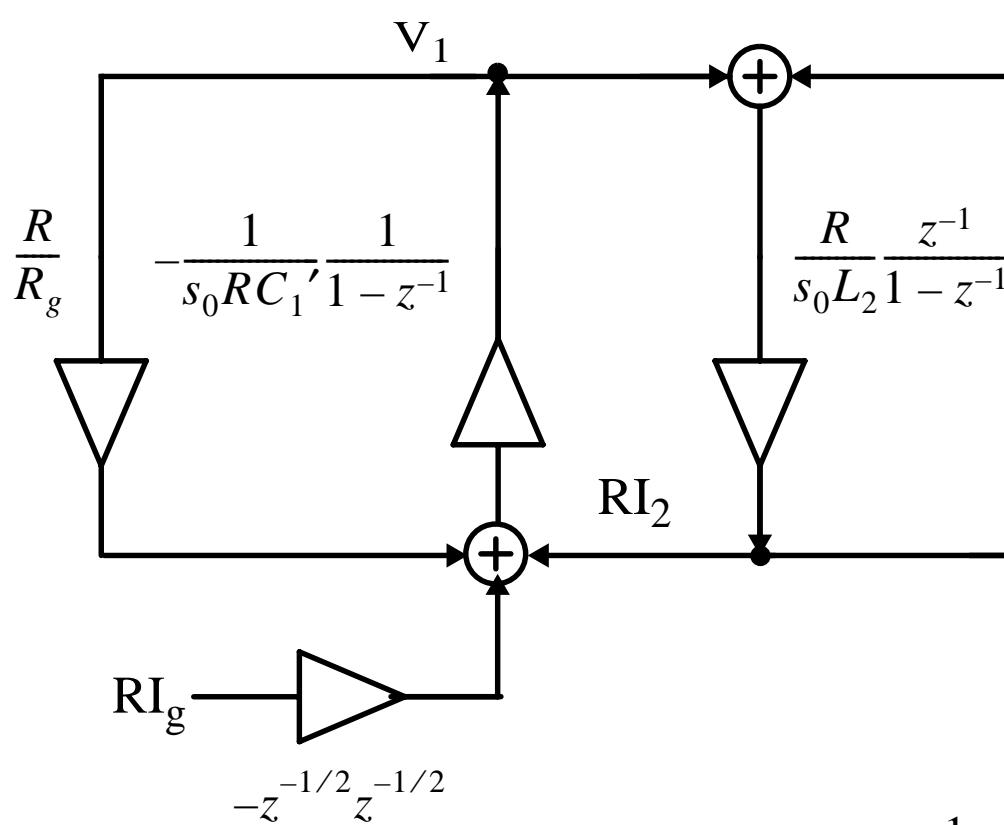

SC realization

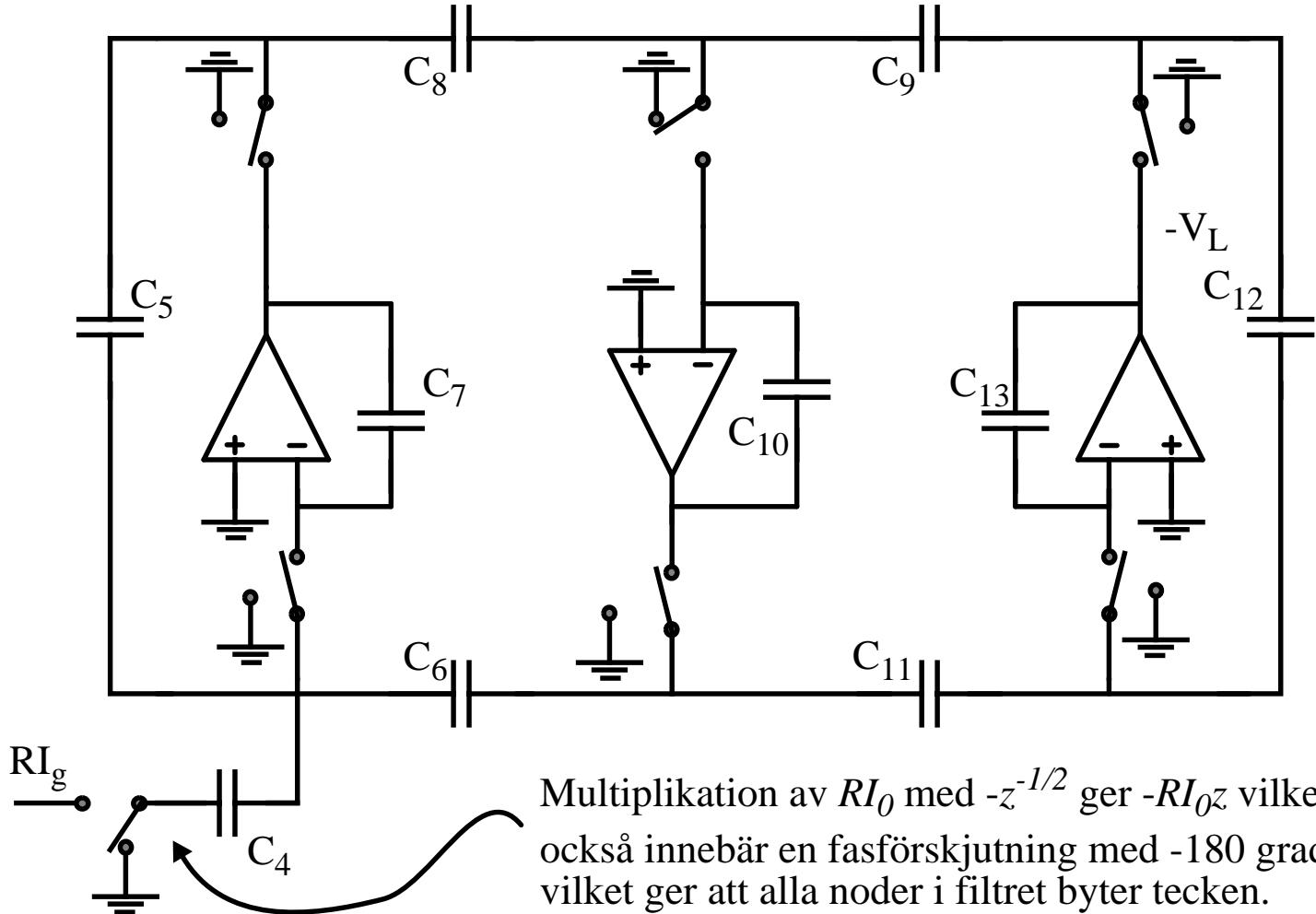

Identify signal paths

SC-filter

$$[V_1]_{RI_g} = \frac{C_4}{C_7} \frac{z^{-1}}{1-z^{-1}}$$

$$[V_1]_{RI_2} = -\frac{C_6}{C_7} \frac{1}{1-z^{-1}}$$

$$[V_1]_{V_1} = -\frac{C_5}{C_7} \frac{1}{1-z^{-1}}$$

$$[RI_2]_{V_1} = \frac{C_8}{C_{10}} \frac{z^{-1}}{1-z^{-1}}$$

$$[RI_2]_{V_3} = \frac{C_9}{C_{10}} \frac{z^{-1}}{1-z^{-1}}$$

$$[-V_3]_{RI_2} = -\frac{C_{11}}{C_{13}} \cdot \frac{1}{1-z^{-1}}$$

$$[-V_3]_{-V_3} = -\frac{C_{12}}{C_{13}} \frac{1}{1-z^{-1}}$$

Signalflödesschema

$$[V_1]_{RI_g} = \frac{1}{s_0 RC_1} \cdot \frac{z^{-1}}{1-z^{-1}}$$

$$[V_1]_{RI_2} = -\frac{1}{s_0 RC_1} \frac{1}{1-z^{-1}}$$

$$[V_1]_{V_1} = -\frac{1}{s_0 RC_1} \frac{R}{R_i} \frac{1}{1-z^{-1}}$$

$$[RI_2]_{V_1} = \frac{R}{s_0 L_2} \frac{z^{-1}}{1-z^{-1}}$$

$$[RI_2]_{V_3} = \frac{R}{s_0 L_2} \frac{z^{-1}}{1-z^{-1}}$$

$$[-V_3]_{RI_2} = -\frac{R}{R_L} \cdot \frac{1}{s_0 RC_3} \cdot \frac{1}{1-z^{-1}}$$

$$[-V_3]_{-V_3} = -\frac{R}{R_L} \cdot \frac{1}{s_0 RC_3} \cdot \frac{1}{1-z^{-1}}$$

Resultat

$$\frac{C_4}{C_7} = \frac{1}{s_0 RC_1}$$

$$\frac{C_6}{C_7} = \frac{1}{s_0 R \alpha_1 C_1}$$

$$\frac{C_5}{C_7} = \frac{1}{s_0 R_i C_1}$$

$$\frac{C_8}{C_{10}} = \frac{R}{s_0 L_2}$$


$$\frac{C_9}{C_{10}} = \frac{R}{s_0 L_2}$$

$$\frac{C_{11}}{C_{13}} = \frac{1}{s_0 R_L C_3}$$

$$\frac{C_{12}}{C_{13}} = \frac{1}{s_0 R_L C_3}$$

Dessutom kan antas att $R_i = R_L = R$

Scaling of signal flow graph

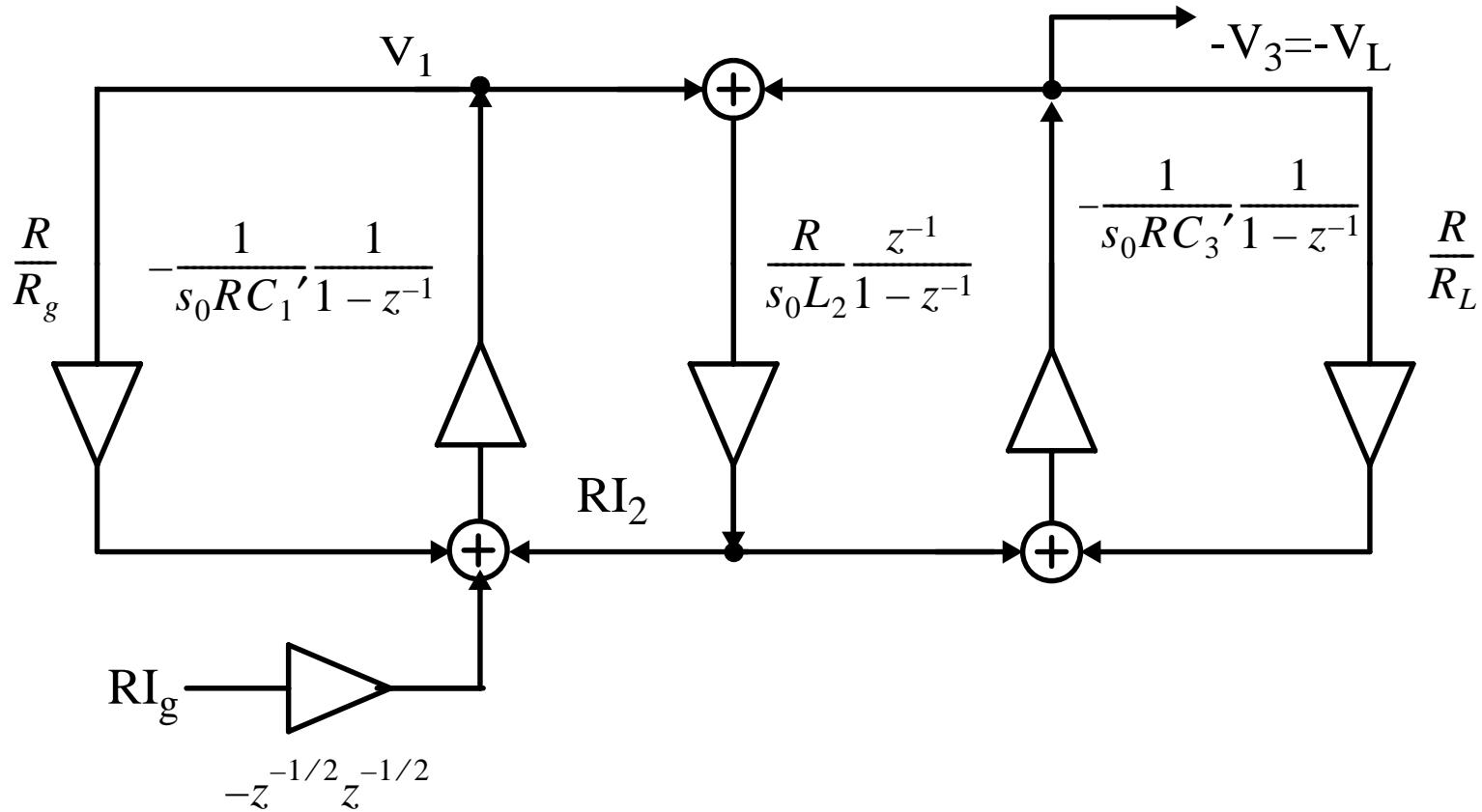

Discrete-time filter scaling

