



# Lecture 5, ATIK

Switched-capacitor circuits 1  
Basics, Accumulators

# What did we do last time?



## Differential circuits

Why differential?

CMRR, CMR

## Operational amplifiers

More on how we design them

Cookbook recipes

PSRR

## Circuit noise

Thermal and flicker noise

Noise bandwidth

# What will we do today?

Switched capacitor operation

Charge redistribution

Parasitics

Typical building blocks

Accumulators



# Switched capacitor - Background



Resistors are **evil**... bulky and noisy and nonlinear

Inductors are **evil** ... bulky and have low Q value


In CMOS design, we want to stick to transistors and capacitors  
(preferrably only the transistors)

How can we mimick a resistor using transistors and capacitors

# Switched capacitor



The first trial

 

First phase:

$$q_1(nT) = C_1 \cdot v_1(nT)$$

$$v_2(nT) = v_2(nT - \tau)$$

Second phase:

$$q_1(nT + \tau) = C_1 \cdot v_2(nT + \tau)$$


$$v_1(nT + \tau) = ?$$



# Switched capacitor, cont'd



The transferred charge

 

The net charge

$$\Delta Q(nT + \tau) = q_1(nT + \tau) - q_1(nT) = C_1 \cdot (v_2(nT + \tau) - v_1(nT))$$

The average current during one period

$$I_{avg} = \frac{\Delta Q(nT + \tau)}{T} = \frac{C_1}{T} \cdot (v_2(nT + \tau) - v_1(nT))$$

# Switched capacitor, cont'd



Compiled

$$I_{avg}(nT + \tau) = \frac{C_1}{T} \cdot (v_2(nT + T) - v_1(nT)) = \frac{C_1}{T} \cdot \Delta V(nT + \tau)$$

Simulates a resistance

$$R_{eq} = \frac{T}{C_1}$$

With shorter sampling periods, the resistance decreases

Less charge is transported in average

The larger capacitor, the resistance decreases

More current can be handled


# Characteristics



When is this assumption valid?

We're taking an average of something, indicating signal frequency has to be small compared to sample frequency

Pulse-amplitude modulated signal (PAM)

 

We should look at the flat areas where attenuation is low.

$$f_{\text{signal}} \ll f_{\text{sample}}$$



 
# Using the switched capacitor: An RC link



A first-order (incorrect!) analysis

$$\frac{V_2(s)}{V_1(s)} = \frac{1}{1 + \frac{s}{1/R_{eq}C_2}} \approx \frac{1}{1 + \frac{sT}{C_1/C_2}}$$



We get a capacitor ratio instead!

# Why are ratios better? And why should we use pears with pears?




A ratio gives

$$\frac{C_1 + \Delta C_1}{C_2 + \Delta C_2} = \frac{C_1}{C_2} \cdot \frac{1 + \frac{\Delta C_1}{C_1}}{1 + \frac{\Delta C_2}{C_2}} = \frac{C_1}{C_2} \cdot \frac{1 + \rho_1}{1 + \rho_2} \approx \frac{C_1}{C_2} \cdot (1 + \rho_1) \cdot (1 - \rho_2) \approx \frac{C_1}{C_2} \cdot (1 - \rho^2)$$

Whereas a product gives
 
$$(C + \Delta C) \cdot (R + \Delta R) = RC \cdot (1 + \rho_C) \cdot (1 + \rho_R) \approx RC \cdot (1 + 2\rho + \rho^2)$$



# Using the switched capacitor: An RC link



A first-order (correct!) analysis.

(Notice that C2 "steals" charge during one phase.)

Phase 1:

$$V_2(nT) = V_2(nT - \tau) \quad \text{and} \quad q_1(nT) = C_1 \cdot V_1(nT)$$

Phase 2:

$$q_2(nT + \tau) = C_2 \cdot V_2(nT + \tau) \quad \text{and} \quad q_1(nT + \tau) = C_1 \cdot V_2(nT + \tau)$$

Charge must be preserved on the two caps:

$$q_1(nT + \tau) + q_2(nT + \tau) = q_1(nT) + q_2(nT)$$

$$(C_1 + C_2) \cdot V_2(nT + \tau) = C_1 \cdot V_1(nT) + C_2 \cdot V_2(nT)$$

$$(C_1 + C_2) \cdot V_2(nT + T) = C_1 \cdot V_1(nT) + C_2 \cdot V_2(nT)$$

Use the frequency domain!

$$(C_1 + C_2) \cdot z \cdot V_2(z) - C_2 \cdot V_2(z) = C_1 \cdot V_1(z) \Rightarrow \frac{V_2(z)}{V_1(z)} = \frac{C_1}{(C_1 + C_2)z - C_2}$$

# Using the switched capacitor: An RC link



Do a mathematically "incorrect" substitution

When is this assumption valid?

$$\frac{V_2(s)}{V_1(s)} = \frac{C_1}{(C_1+C_2)e^{sT} - C_2} \approx \frac{C_1}{(C_1+C_2)(1+sT) - C_2} = \frac{C_1}{C_1 + (C_1+C_2)sT} = \frac{1}{1 + \frac{sT}{\frac{C_1}{C_1+C_2}}}$$

The capacitors are not isolated from each other

Loss in bandwidth

the factor can never be larger than 1 (!)

# Using the SC: Active integrator




The input capacitor will see virtual ground and thus not  $C_2$

Use the standard continuous-time approach

$$\frac{V_2(t)}{V_1(t)} \approx \frac{-1}{s R_{eq} C_2} = \frac{-C_1/C_2}{s T}$$

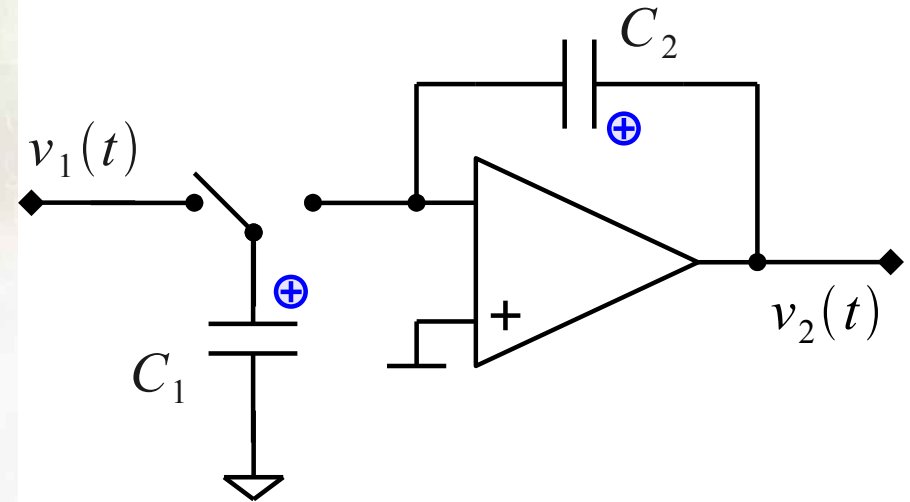The virtual ground will effectively drain  $C_1$  in every second phase, i.e., the charge drop is independent on  $C_2$ .





# Charge redistribution analysis, phase 1




However, just replacement is not accurate enough!

Input capacitor

$$q_1(nT) = C_1 \cdot V_1(nT)$$


Storage capacitor
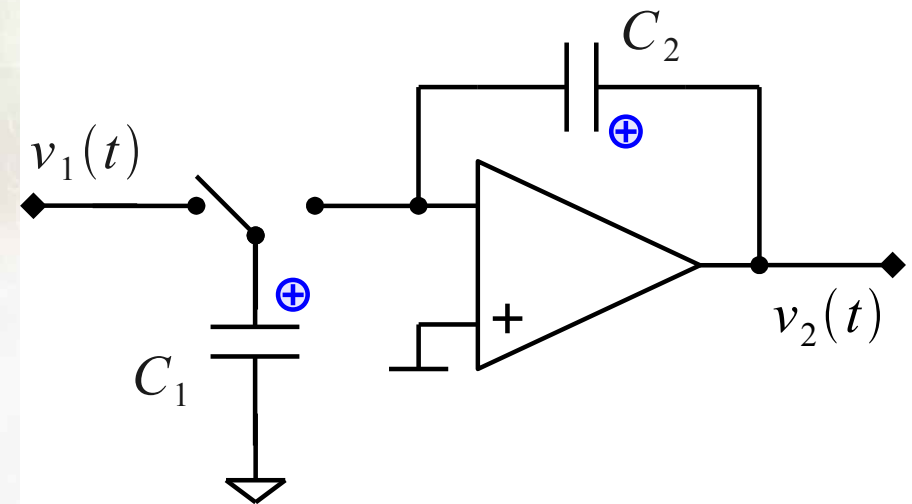
$$q_2(nT) = C_2 \cdot (V_2(nT) - 0) = C_2 \cdot V_2(nT)$$



Notice the "sign" of the capacitors. These are aid markers only.
 
# Charge redistribution analysis, phase 2




Input capacitor

$$q_1(nT + \tau) = C_1 \cdot (0 - 0) = 0 \text{ (Emptied !)}$$

Storage capacitor

$$q_2(nT + \tau) = C_2 \cdot (V_2(nT + \tau) - 0) = C_2 \cdot V_2(nT + \tau)$$

# Charge redistribution analysis, 1 to 2

 


The charge in the system must be preserved!

"Positive" charge on  $C_1$  will float to "negative" plate of  $C_2$ .

$$q_2(nT + \tau) = -q_2(nT) - q_1(nT)$$

# Charge redistribution analysis, 2 to 1

 

The "negative" charge on  $C_2$  cannot disappear, the voltage across capacitor is preserved:

$$q_2(nT + T) = q_2(nT + \tau)$$

Input capacitor is recharged

# Charge redistribution analysis, compiled



Instantaneous charging

$$q_1(nT) = C_1 \cdot V_1(nT)$$

$$q_2(nT) = C_2 \cdot V_2(nT)$$

Charge preservation

$$-q_2(nT + \tau) = -q_2(nT) + q_1(nT)$$

$$q_2(nT + T) = q_2(nT + \tau)$$

Combined

$$C_2 \cdot V_2(nT + T) - C_2 \cdot V_2(nT) = -C_1 \cdot V_1(nT)$$

Go to frequency domain

$$C_2 \cdot V_2(z) \cdot (z - 1) = -C_1 \cdot V_1(z) \Rightarrow \frac{V_2(z)}{V_1(z)} = \frac{-C_1/C_2}{z - 1}$$



# Charge redistribution analysis, checked



Once again, the sloppy frequency transform

$$z = e^{sT} \approx 1 + sT$$

Insert

$$\frac{V_2(z)}{V_1(z)} = \frac{-C_1/C_2}{1 + sT - 1} = \frac{-C_1/C_2}{sT}$$

Now, the two formulas correlate!

# Caveats

"High" sample frequency

"High" unity-gain frequency

Low on-resistance

Linear capacitors

Buffers required

Passive SC implies losses

If we go to a sampled system, e.g. ADC, we can utilize whole frequency band! (Revisited in discrete-time filter design).



# Switched-capacitor in a context



Filters

Sigma-delta modulators

Sample-and-hold

Gain circuits

Common-mode feedback circuits

Comparators

Auto-zeroing


Reset circuits

Accumulators/integrators are vital building blocks in many applications
 
# Parasitics, or a capacitor is not ideal



Sandwiched capacitor in four metal layers



Examples on parasitics

Bottom-plate parasitics

Fringing capacitance to near-by objects


Overlap capacitance (if accuracy is required)
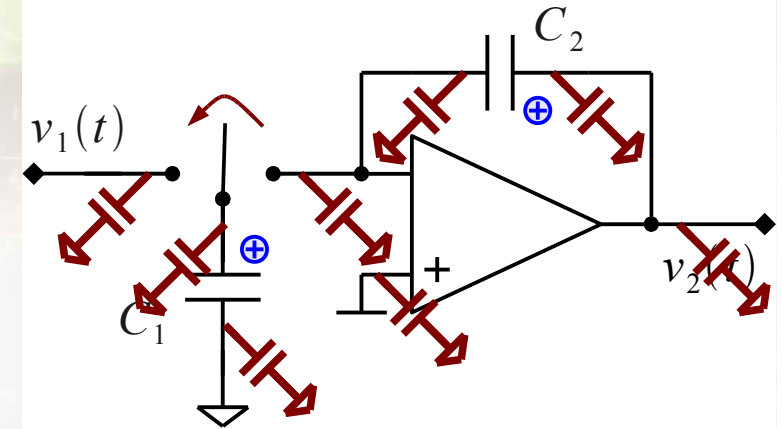
# Parasitics, sensitive example



Add parasitics "everywhere"

- Each switch
- Each capacitor plate
- Each OP node




Cancel those that do not influence the results

- Voltage sources
- Virtual grounds
- Grounded

One left!

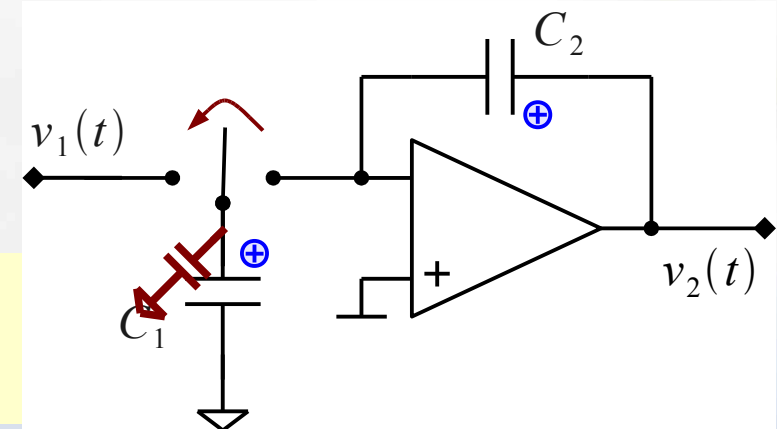Effectively changing the value of  $C_1$ .





# Parasitics, insensitive example




This is also an accumulator

Phase 1:

$$q_1(nT) = C_1 \cdot V_1(nT), \quad q_2(nT) = C_2 \cdot V_2(nT)$$

Phase 2:
 
$$q_1(nT + \tau) = 0, \quad q_2(nT + \tau) = C_2 \cdot V_2(nT + \tau)$$



Charge preservation:

$$q_2(nT + \tau) = q_2(nT) \Rightarrow V_2(nT + \tau) = V_2(nT)$$

$$-q_1(nT) - q_2(nT) = -q_1(nT - \tau) - q_2(nT - \tau) = -q_2(nT - T)$$


$$C_1 \cdot V_1(z) = -C_2 \cdot (1 - z^{-1}) \cdot V_2(z) \Rightarrow V_1(z) V_2(z) = \frac{-C_1 / C_2}{1 - z^{-1}}$$
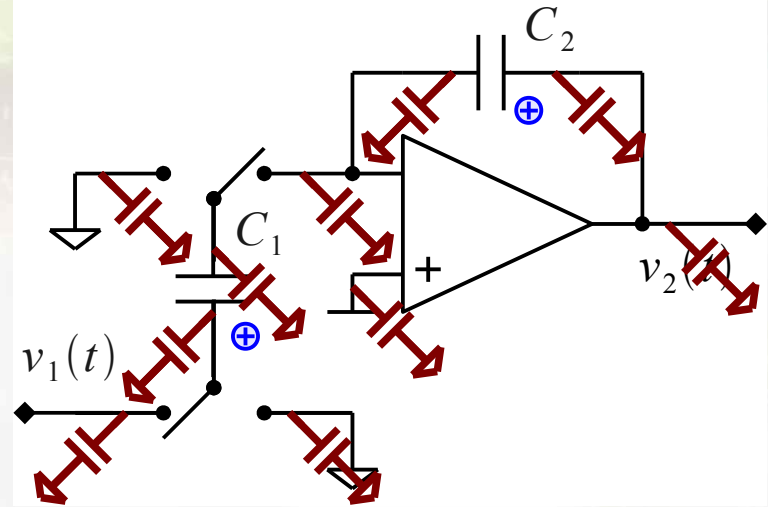
# Parasitics, insensitive example




Add parasitics "everywhere"

- Each switch
- Each capacitor plate
- Each OP node



Cancel those that do not influence the results

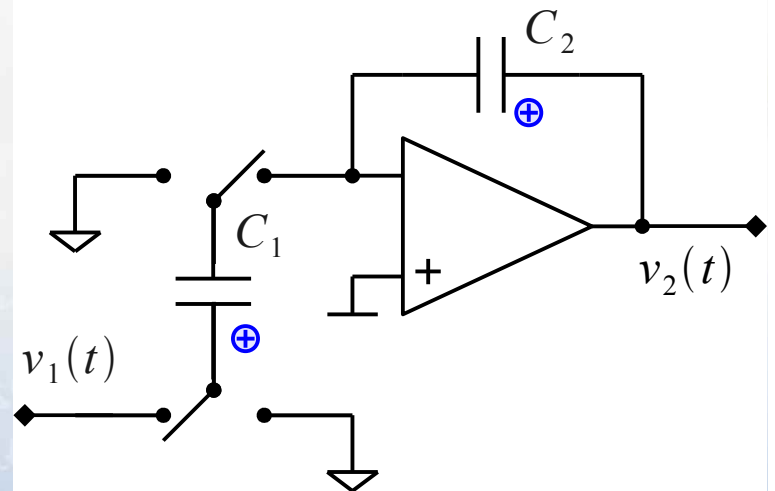- Voltage sources
- Virtual grounds
- Grounded



# Parasitics, the check list



These can be ignored:

continuously connected to input voltage source (ideal) or to OP (ideal) outputs (Ideal sources can give/take as much charge as needed)

connected between ground-ground or between "ground-virtual ground" in both phases (the effective charge is zero all the time)

charged from a voltage source or OP during one phase and is discharged to ground during next phase

capacitor plates that are charged during one phase and not connected during next phase

These have to be considered

charged from a voltage source or OP during one phase and discharged to a sensitive (another capacitor plate or virtual ground) during next phase

# What did we do today?



## Switched capacitor circuits

The basics

Charge-redistribution analysis

## Nonidealities

SC parasitics

# What will we do next time?



Switched capacitor circuits with nonideal effects in mind

What should we look out for?

What is the impact on system performance, like filters.

Continuous-time filters

Switched capacitor revisited during

Discrete-time filter lectures

Data converter lectures