
 


# Multiple voltage design

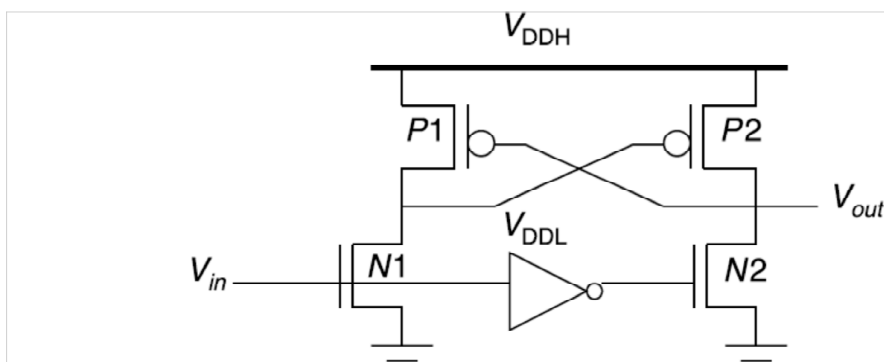

**Fig. 2** Examples  
 a CVS solution  
 b ECVS solution

# Level converter



**Fig. 1** Typical level-converter design

# Precomputation of combinational logic

 


Fig. 3 Pipeline stage of a data path

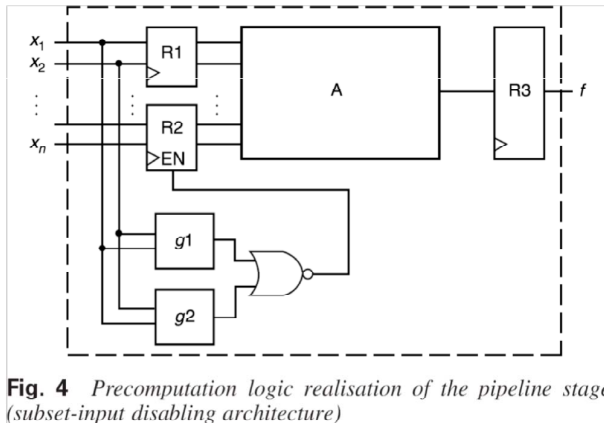


Fig. 4 Precomputation logic realisation of the pipeline stage (subset-input disabling architecture)

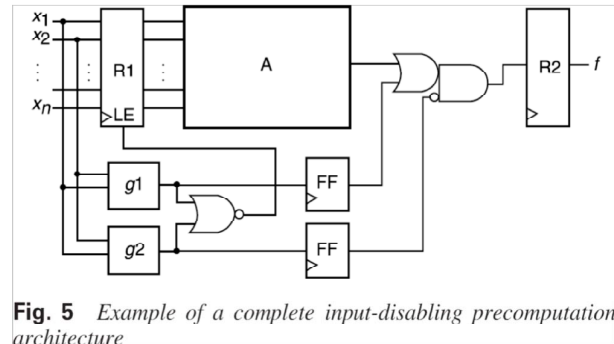


Fig. 5 Example of a complete input-disabling precomputation architecture

# Precomputation enable set

- Computation of predictor functions

Denote a logic function  $f(x_0, x_1, \dots, x_{n-1})$

The cofactor of  $f$  with respect to  $x_0$  is then  $f_{x_0}(1, x_1, \dots, x_{n-1})$


The observability don't care set for input  $x_0$  is  $ODC_{x_0} = f_{x_0} \cdot \overline{f_{x_0}} + \overline{f_{x_0}} \cdot \overline{f_{x_0}}$

This set indicates when  $x_0$  is redundant in the computation of  $f$

- The loading of inputs  $x_0, x_1, \dots, x_{n-1}$  can be disabled using


$$g = \prod_{i=0}^{n-1} ODC_i$$

# Clock gating

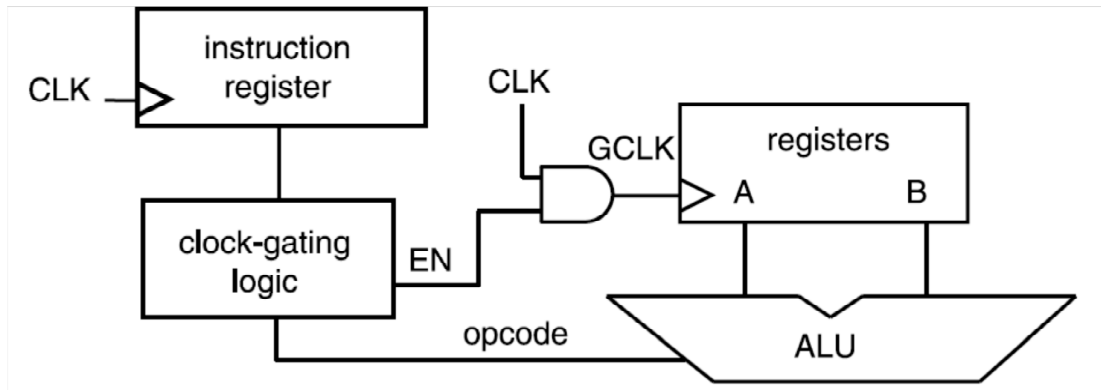

**Fig. 6** Clock gating logic for ALU in a typical processor microarchitecture with negative-edge triggered flip-flops


# Disabling clock

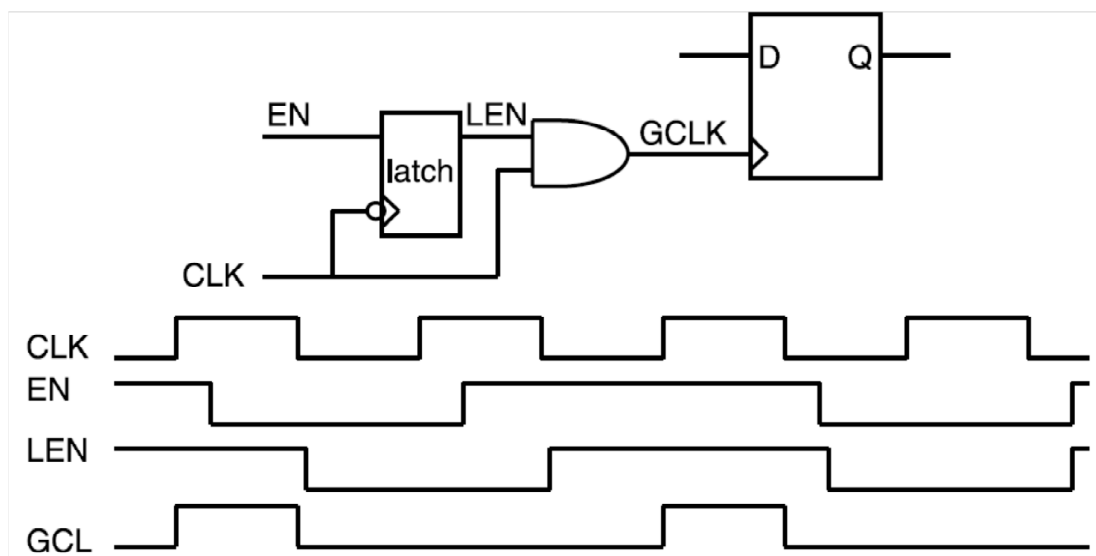

**Fig. 7** Clock is disabled when  $EN = 0$ ; furthermore, a hazard on  $EN$  will be stopped from reaching  $GCLK$




# Decomposition of FSMs

 

**Fig. 10** Example of an FSM (dk27) that may be decomposed into two sub-FSMs such that one sub-FSM can be shut off when the other is active and vice versa

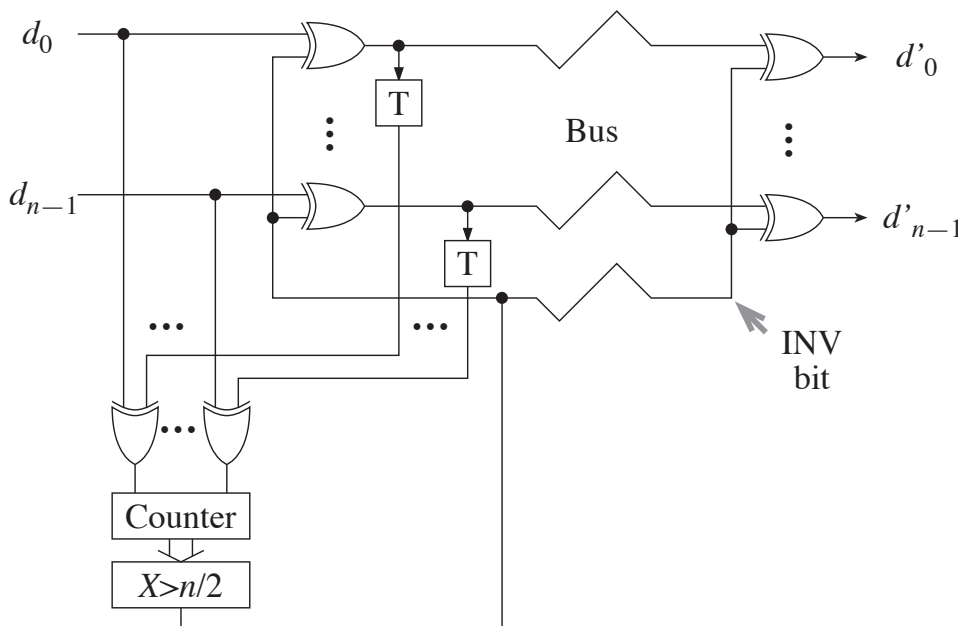
# Bus-invert code

- Invert extra bus bit when this action will save power



 
## T0 code

- Keep bus state when next value (address) is anticipated


 
## Level vs. transition signaling

- Level signaling
  - Active-low: "1" is represented by a low voltage
  - Active-high: "1" is represented by a high voltage
- Transition signaling
  - "0" is represented by no transition
  - "1" is represented by a transition  $\Rightarrow$  only 1's consume power



# Limited-weight codes

- Design code with few 1's [Stan'97]

from ["Low-power encodings for global communication in CMOS VLSI," by M.R. Stan and W.P. Burlison, IEEE TVLSI, vol. 5, no. 4, pp. 444-455]

TABLE II  
M VERSUS N FOR GIVEN K

information bits (K)	2	4	4	8	8	8	8	16
maximum nr. of 1's (M)	1	1	2	1	2	3	4	8
codeword length (N)	3	15	5	255	23	11	9	17

 


TABLE III  
2-LWC AND 1-LWC FOR A 16-SYMBOL SOURCE

symbol	minimally encoded	2-LWC	1-LWC
0	0000	00000	0000000000000000
1	0001	00001	0000000000000001
2	0010	00010	0000000000000010
3	0011	00011	0000000000000100
4	0100	00100	0000000000010000
5	0101	00101	0000000000100000
6	0110	00110	0000000001000000
7	0111	11000	0000000010000000
8	1000	01000	0000000100000000
9	1001	01001	0000000100000000
10	1010	01010	0000010000000000
11	1011	10100	0000100000000000
12	1100	01100	0001000000000000
13	1101	10010	0010000000000000
14	1110	10001	0100000000000000
15	1111	10000	1000000000000000

## References

### 04.pdf Low-power RT-level synthesis techniques: a tutorial

M. Pedram and A. Abdollahi

IEE Proceedings on Computers and Digital Techniques, volume 152, issue 3, May 2005, pages 333-343

### [Stan'97] Low-power encodings for global communication in CMOS VLSI

M.R. Stan and W.P. Burlison

IEEE Transactions on Very Large Scale Integration (VLSI) Systems, volume 5, issue 4, Dec. 1997, pages 444-455