

### Exercise 1

What is a glitch? How can glitches be reduced in digital circuits?

### Exercise 2

- The propagation time  $t_d$  (the time required to drive the output voltage from  $V_{dd}$  to  $V_{dd}/2$  or from ground to  $V_{dd}/2$ ) for the XNOR gates in Figure 1 is 10 ns. Sketch the signals in node  $f$  and  $x$  as functions of time when the inputs  $\langle a,b,c \rangle$  changes from  $\langle 0,1,1 \rangle$  to  $\langle 0,0,0 \rangle$ . Consider  $a$ ,  $b$ , and  $c$  as ideal.
- Calculate the dissipated energy due to the two capacitances  $C_L$ .
- A delay of 10 ns is introduced for signal  $c$  relative to  $a$  and  $b$ . Sketch the output signal and calculate the dissipated energy.

 


Figure 1. Cascaded XNOR gates.

### Exercise 3

In Figure 2 an  $N$ -bits ripple carry adder is shown. The input signals  $a$ ,  $b$  and  $c_0$  are random and synchronized to a global clock signal. The propagation times for both sum and carry of a full adder is  $t_a$ . The full adder is free from glitches if its inputs are synchronized. The probability that an input bit is high is 0.5 (i.e.  $P(a_j=1) = P(b_j=1) = P(c_0=1) = 0.5$  where  $0 \leq j \leq N-1$ ). Assume short rise and fall times of all signals.

 


Figure 2.  $N$ -bit ripple carry adder.

- Determine  $P(s_0)$  and  $P(c_1)$ .
- Assume that the signals  $a_j$  and  $b_j$  are stable and that  $c_j$  makes one transition. Determine the probability of a transition for  $s_j$  and  $c_{j+1}$ , respectively.
- Determine the transition activity of  $s_j$  and  $c_{j+1}$  when  $a$ ,  $b$  and  $c_0$  are random and synchronized to a global clock signal.
- The propagation delay of a 16-bits ripple carry adder is due to pipelining decreased from  $16t_a$  to  $4t_a + t_D$  where  $t_D$  is the propagation delay of one D flip-flop. Sketch how the pipelining is implemented

### Exercise 4

The circuit in Figure 3 realizes the logic function  $F = AC + BC$ . Even with identical gates the circuit can produce undesired glitches at the output node  $F$ . For example assume  $A = B = C = 1$ . At this stage the output  $F = 1$ . If  $C$  goes low, the output  $F$  can make an undesired transition  $1 \rightarrow 0 \rightarrow 1$  due to the finite propagation time of the inverter that generates  $\bar{C}$ . Redesign the circuit so that a logic transition on one of the inputs will not cause glitches at the output.

 


Figure 3. Digital circuit.

### Exercise 5

Design a digital circuit according to Table 1 where the output signal must be glitch free for single input changes.

<b>ab\cd</b>	<b>00</b>	<b>01</b>	<b>11</b>	<b>10</b>
00	1	1	1	1
01	0	1	-	-
11	0	1	1	0
10	0	-	0	0

Table 1: Truth table for the digital circuits.

### Exercise 6

- Determine the transition activity  $\alpha_f$  of the output node of a static CMOS NAND gate where the two input signals  $a$  and  $b$  has the transition activities  $\alpha_a$  and  $\alpha_b$ , respectively ( $P(a) = P(b) = 1/2$ ). Assume that the input signals are outputs from a register.
- Calculate the transition activity at the output node for the four cases below.
  - $\alpha_a = \alpha_b = 1/2$ , 2)  $\alpha_a = \alpha_b = 1/4$ , 3)  $\alpha_a = 1/2, \alpha_b = 1/4$ , 4)  $\alpha_a = 0$
- Is the answer in the fourth case in b) reasonable?

### Exercise 7

In the dashed box in Figure 4 a precharged gate is shown. The input capacitances of this gate are estimated to  $C_A$ ,  $C_B$  and  $C_C$ , respectively and the output capacitance is estimated to  $C_F$ .  $A$  and  $B$  are uncorrelated. During the precharge phase  $A$  and  $B$  are always zero. During the evaluation phase  $P(A=1) = 0.64$  and  $P(B=1) = 0.35$ .

 


Figure 4. Precharged gate.

- Determine the transition activity  $\alpha_F$ .
- Determine the transition activities  $\alpha_A$ ,  $\alpha_B$  and  $\alpha_C$ .
- Determine the switching activity  $a$  and the switched capacitance  $C_{sw}$ .
- Determine the power consumption and explain where and how the energy is dissipated.
- Determine the power consumption when  $A$  and  $B$  are constants.
- Compare the results with Exercise 6.

### Exercise 8

A logic circuit is shown in Figure 5. Determine the power consumption due to charging and discharging of the capacitors  $C_a$ ,  $C_b$ ,  $C_c$ ,  $C_x$  and  $C_F$  associated with nodes  $a$ ,  $b$ ,  $c$ ,  $x$ , and  $F$ . Assume static CMOS logic and a power supply of  $V_{DD}$ . The input signals are glitch free, uncorrelated, and random, the clock frequency is  $f$  and the supply voltage is  $V_{DD}$ .  $P(a=1) = 0.4$ ,  $P(b=1) = 0.5$ ,  $P(c=1) = 0.6$ .

 


Figure 5. Logic circuit.

- Solve the problem assuming a zero-delay model.
- Solve the problem assuming a unit-delay model.

Solution 1

- a) Glitches are unwanted transitions that may occur before the signal settles to its intended value.
- b) By delay balancing of input signals (see exercise 2).  
By adding redundant logic (see exercise 4).  
Shorten the logic depth of combinational logic by registers.

Solution 2

a)

 


Figure 6. Glitch in node f.

b) 
$$E = \frac{V_{dd}^2 C_L}{2} + \frac{V_{dd}^2 C_L}{2} = V_{dd}^2 C_L$$

c)

 


Figure 7. Glitch eliminated.

$$E = \frac{V_{dd}^2 C_L}{2}$$

Solution 3

a)  $P(s_0) = P(c_1) = 1/2$

b) Truth table for analyzing carry transitions:

$a_j b_j$	$c_{j+1}$	$s_j$	$P_{state}$
00	0	$c_j$	1/4
01	$c_j$	$c_j'$	1/4
10	$c_j$	$c_j'$	1/4
11	1	$c_j$	1/4

$P(\text{"s}_j \text{ makes one transition when } c_j \text{ makes one transition"}) = 1$

$P(\text{"c}_{j+1} \text{ makes one transition when } c_j \text{ makes one transition"}) = 1/4+1/4 = 1/2$

c) When inputs  $a_j$  and  $b_j$  get new values, input  $c_j$  keeps its old value during the delay time of one FA ( $j \geq 1$ ). Table with state transitions due to update of inputs  $a_j$  and  $b_j$ :

$c_j$	$a_j b_j$	$c_{j+1}$	$s_j$	$P_{state}$
0	00→00	0→0	0→0	1/32
0	00→01	0→0	<b>0→1</b>	1/32
0	00→10	0→0	<b>0→1</b>	1/32
0	00→11	<b>0→1</b>	0→0	1/32
0	01→00	0→0	<b>1→0</b>	1/32
0	01→01	0→0	1→1	1/32
0	01→10	0→0	1→1	1/32
0	01→11	<b>0→1</b>	<b>1→0</b>	1/32
0	10→00	0→0	<b>1→0</b>	1/32
0	10→01	0→0	1→1	1/32
0	10→10	0→0	1→1	1/32
0	10→11	<b>0→1</b>	<b>1→0</b>	1/32
0	11→00	<b>1→0</b>	0→0	1/32
0	11→01	<b>1→0</b>	<b>0→1</b>	1/32
0	11→10	<b>1→0</b>	<b>0→1</b>	1/32
0	11→11	1→1	0→0	1/32

$c_j$	$a_j b_j$	$c_{j+1}$	$s_{j+1}$	$P_{state}$
1	00→00	0→0	1→1	1/32
1	00→01	<b>0→1</b>	<b>1→0</b>	1/32
1	00→10	<b>0→1</b>	<b>1→0</b>	1/32
1	00→11	<b>0→1</b>	1→1	1/32
1	01→00	<b>1→0</b>	<b>0→1</b>	1/32
1	01→01	1→1	0→0	1/32
1	01→10	1→1	0→0	1/32
1	01→11	1→1	<b>0→1</b>	1/32
1	10→00	<b>1→0</b>	<b>0→1</b>	1/32
1	10→01	1→1	0→0	1/32
1	10→10	1→1	0→0	1/32
1	10→11	1→1	<b>0→1</b>	1/32
1	11→00	<b>1→0</b>	1→1	1/32
1	11→01	1→1	<b>1→0</b>	1/32
1	11→10	1→1	<b>1→0</b>	1/32
1	11→11	1→1	1→1	1/32

Determine the transition activities for the output considering that the carry input is not changed until after  $t_{FA}$

$$\alpha_{C_1} = P(\overline{C_1})P(C_1) + P(C_1)P(\overline{C_1}) = \frac{1}{2}$$

$$\alpha_{C_2} = \frac{3}{8} + \frac{\alpha_{C_1}}{2} = \frac{3}{8} + \frac{1}{2} \cdot \frac{1}{2}$$

$$\alpha_{C_3} = \frac{3}{8} + \frac{\alpha_{C_2}}{2} = \frac{3}{8} \left(1 + \frac{1}{2}\right) + \frac{1}{2} \cdot \frac{1}{2} \cdot \frac{1}{2}$$

$$\alpha_{C_4} = \frac{3}{8} + \frac{\alpha_{C_3}}{2} = \frac{3}{8} \left(1 + \frac{1}{2} + \frac{1}{4}\right) + \frac{1}{2} \cdot \frac{1}{2} \cdot \frac{1}{2} \cdot \frac{1}{2}$$

$$\alpha_{C_j} = \frac{3}{8} \sum_{i=0}^{j-1} \frac{1}{2^i} + \frac{1}{2^j} = \frac{3}{8} \cdot 2(1 - 2^{-j}) + 2^{-j} = \frac{3 + 2^{-j}}{4}$$

$$\alpha_{s_0} = P(\overline{S_0})P(S_0) + P(S_0)P(\overline{S_0}) = \frac{1}{2}, \quad \alpha_{s_j} = \frac{1}{2} + 1 \cdot \alpha_{c_j} = \frac{5+2^{-j}}{4}$$

Answer:  $\alpha_{s_j} = \frac{5+2^{-j}}{4}$  and  $\alpha_{c_j} = \frac{3+2^{-j}}{4}$  for  $j \geq 1$

Solution 4

A glitch-free realization of  $F$  when one of  $A$ ,  $B$ , and  $C$  is changed is shown below.

 


Figure 8. Karnaugh maps.

 


Figure 9. A glitch-free circuit using redundant logic.

Solution 5

The two areas marked by solid lines (two prime implicants) in Truth table for the digital circuits. are enough to realize the desired function ( $f = (a \cdot b) + (b \cdot d)$ ), but a change of the input signals from  $(a, b, c, d) = (0, 1, 0, 1)$  to  $(a, b, c, d) = (0, 0, 0, 1)$  is not within any marked area. This means that we can not guarantee that the output signal is glitch free for a single input change.

ab\cd	00	01	11	10
00	1	1	1	1
01	0	1	1	0
11	0	1	1	0
10	0	0	0	0

Table 2. Karnaugh map.

The digital circuit is glitch free if the input signals starts and ends in the same marked area. In Table 3 three areas is marked (three prime implicants) corresponding to  $f = (\overline{a} \cdot \overline{b}) + (b \cdot d) + (\overline{a} \cdot d)$ . With this solution, a single input change can not produce a glitch. The digital circuit is shown in Figure 10.

ab\cd	00	01	11	10
00	1	1	1	1
01	0	1	1	0
11	0	1	1	0
10	0	0	0	0

Table 3: Karnaugh map.

 


Figure 10. Two complementary bit lines.

### Solution 6

$$\begin{aligned} \alpha_a &= \alpha_{a(01)} + \alpha_{a(10)} \\ \alpha_b &= \alpha_{b(01)} + \alpha_{b(10)} \end{aligned}$$

Let  $P\{(a_j, b_j) \rightarrow (a_{j+1}, b_{j+1})\}$  denote the probability of the scenario  $(a_j, b_j) \rightarrow (a_{j+1}, b_{j+1})$

There are six scenarios which results in a transition at the output  $f = \overline{a} \overline{b}$

$$P\{(0, 0) \rightarrow (1, 1)\} = \alpha_{a(01)} \alpha_{b(01)}$$

$$P\{(0, 1) \rightarrow (1, 1)\} = \alpha_{a(01)} \alpha_{b(11)}$$

$$P\{(1, 0) \rightarrow (1, 1)\} = \alpha_{a(11)} \alpha_{b(01)}$$

$$P\{(1, 1) \rightarrow (0, 0)\} = \alpha_{a(10)} \alpha_{b(10)}$$

$$P\{(1, 1) \rightarrow (0, 1)\} = \alpha_{a(10)} \alpha_{b(11)}$$

$$P\{(1, 1) \rightarrow (1, 0)\} = \alpha_{a(11)} \alpha_{b(10)}$$

$$\alpha_f = \alpha_{f(01)} + \alpha_{f(10)} = 2 \left( \frac{\alpha_a \alpha_b}{4} + \frac{\alpha_a (1 - \alpha_b)}{4} + \frac{\alpha_b (1 - \alpha_a)}{4} \right)$$

$$\alpha_f = \frac{1}{2} (\alpha_a + \alpha_b - \alpha_a \alpha_b)$$

b)  $3/8, 7/32, 5/16, a_b/2$

- c)  $\alpha_a = 0$  means that  $a$  is constantly equal to 0 or 1.  $P(a=1) = P(a=0) = 0.5$   
 $a = 0 \Rightarrow \alpha_f = 0$   
 $a = 1 \Rightarrow \alpha_f = \alpha_b$

The probability of  $\alpha_f = 0$  is 1/2 and the probability of  $\alpha_f = \alpha_b$  is also 1/2.

Hence, the expected value of the transition activity:  $\alpha_f = \frac{0 + \alpha_b}{2} = \alpha_b/2$

### Solution 7

- a) Transition activity  $\alpha_F = \alpha_{F01} + \alpha_{F10}$

$$P(A=1) = 0.64, P(B=1) = 0.35 \Rightarrow P(A=0) = 0.36, P(B=0) = 0.65$$

$F$  is always one at the end of the precharge phase. In Table 4 the probability of the four possible states, at the end of the evaluation phase, are listed.

State ( $AB$ )	$F$	Probability
00	1	$0.36 \cdot 0.65 = 0.234$
01	0	$0.36 \cdot 0.35 = 0.126$
10	0	$0.64 \cdot 0.65 = 0.416$
11	0	$0.64 \cdot 0.35 = 0.224$

Table 4: Two uncorrelated bit lines.

Assume that  $F$  is precharged to 1. During the evaluation phase the probability of  $F$  being discharged to 0 is  $0.126 + 0.416 + 0.224 = 0.766$ . If  $F$  is discharged to 0 it will then be charged to 1 during the next precharge phase. Hence, if  $F$  is discharged it will make two transitions during one clock cycle (see Figure 11).

Hence,  $\alpha_F = \alpha_{F10} + \alpha_{F01} = 0.766(1 + 1) = 1.532 \approx 1.53$ .

 


Figure 11. Discharge and charge of  $F$ .



b)  $\alpha_{A01} = 1 \cdot 0.64 = 0.64$ ,  $\alpha_{A10} = 0.64 \cdot 1 = 0.64 \Rightarrow \alpha_A = \alpha_{A01} + \alpha_{A10} = 1.28$   
 $\alpha_{B01} = 1 \cdot 0.35 = 0.35$ ,  $\alpha_{B10} = 0.35 \cdot 1 = 0.35 \Rightarrow \alpha_B = \alpha_{B01} + \alpha_{B10} = 0.70$   
 $\alpha_C = \alpha_{C01} + \alpha_{C10} = 2$

c) 
$$a = \frac{\sum_i \alpha_{i01} C_i}{\sum_i C_i} = \frac{\alpha_{A01} C_A + \alpha_{B01} C_B + \alpha_{C01} C_C + \alpha_{F01} C_F}{C_A + C_B + C_C + C_F} =$$

$$\frac{0.64 C_A + 0.35 C_B + C_C + 0.766 C_F}{C_A + C_B + C_C + C_F}$$

d) 
$$C_{sw} = a \sum_i C_i = 0.64 C_A + 0.35 C_B + C_C + 0.766 C_F$$

$$P = fa C V_{dd}^2 = f(0.64 C_A + 0.35 C_B + C_C + 0.766 C_F) V_{dd}^2$$

When a signal is rising, energy is dissipated as heat in the p-net. When a signal is falling, energy is dissipated as heat in the n-net.

e)  $A = B = 0$  during the precharge phase.  $A = A_0$ ,  $B = B_0$  during evaluation phase, where  $A_0$  and  $B_0$  are constants.

There are four cases:

1)  $AB = 00 \Rightarrow P = fa C V_{dd}^2 = f C_C V_{dd}^2$   
 2)  $AB = 01 \Rightarrow P = fa C V_{dd}^2 = f(C_B + C_C + C_F) V_{dd}^2$   
 3)  $AB = 10 \Rightarrow P = fa C V_{dd}^2 = f(C_A + C_C + C_F) V_{dd}^2$   
 4)  $AB = 11 \Rightarrow P = fa C V_{dd}^2 = f(C_A + C_B + C_C + C_F) V_{dd}^2$

### Solution 8

a) Assume a zero-delay model:

$$P(x) = P(\bar{a}) P(\bar{b}) = (1 - 0.4)(1 - 0.5) = 0.3$$

$$P(F) = P(x) P(c) = 0.3 \cdot 0.6 = 0.18$$

$$\alpha_{a01} = [1 - P(a)] P(a) = (1 - 0.4) \cdot 0.4 = 0.24$$

$$\alpha_{b01} = [1 - P(b)] P(b) = (1 - 0.5) \cdot 0.5 = 0.25$$

$$\alpha_{c01} = [1 - P(c)] P(c) = (1 - 0.6) \cdot 0.6 = 0.24$$

$$\alpha_{x01} = [1 - P(x)] P(x) = (1 - 0.3) \cdot 0.3 = 0.21$$

$$\alpha_{F01} = [1 - P(F)] P(F) = (1 - 0.18) \cdot 0.18 \approx 0.15$$

$$C_{sw} = C_a \alpha_{a01} + C_b \alpha_{b01} + C_c \alpha_{c01} + C_x \alpha_{x01} + C_F \alpha_{F01}$$

$$P = f V_{dd}^2 C_{sw}$$

b) Introducing delay will delay  $x$  and cause glitches at the output  $F$ . The table below shows all transition cases ( $x'$ ,  $c'$ ,  $F''$  denote a previous value, and  $F'$  a transient value):

$x'c' \rightarrow x'c \rightarrow xc$	$F'' \rightarrow F' \rightarrow F$
00→00→00	0→0→0
00→01→01	0→0→0
00→00→10	0→0→0
00→01→11	0→0→1
01→00→00	0→0→0
01→01→01	0→0→0
01→00→10	0→0→0
01→01→11	0→0→1

$x'c' \rightarrow x'c \rightarrow xc$	$F'' \rightarrow F' \rightarrow F$
10→10→00	0→0→0
10→11→01	0→1→0
10→10→10	0→0→0
10→11→11	0→1→1
11→10→00	1→0→0
11→11→01	1→1→0
11→10→10	1→0→0
11→11→11	1→1→1

From the table it can be seen that there will be a glitch for the case  $x'c' \rightarrow xc = 10 \rightarrow 01$ . The probability for this state is

$$P(\text{glitch}) = P(x)P(\bar{c})P(\bar{x})P(c) = 0.3(1-0.6)(1-0.3)0.6 = 0.0504 \approx 0.05$$

Adding the glitch to the switch activity yields

$$C_{sw+g} = C_{sw} + C_F P(\text{glitch}) \text{ and } P = fV_{dd}^2 C_{sw+g}$$