 


# Digital ICs — Lectures

1) <b>Introduction</b> [Ch. 1]	TSEI03/TSTE86
2) <b>Devices</b> [Ch. 3, 4]	TSEI03/TSTE86
3) <b>Interconnect</b> [Ch. 4, 9]	TSTE86
4) <b>Circuits</b> [Ch. 5]	TSEI03/TSTE86
5) <b>Combinational logic</b> [Ch. 6]	TSEI03/TSTE86
6) <b>Sequential circuits</b> [Ch. 7]	TSEI03/TSTE86
7) <b>Synchronization</b> [Ch. 10]	TSTE86
8) <b>Adders</b> [Ch. 11]	TSEI03/TSTE86
9) <b>Multipliers</b> [Ch. 11]	TSTE86
10) <b>Memory</b> [Ch. 12]	TSEI03/TSTE86
11) <b>Manufacturing</b> [Ch. 2]	TSTE86
12) <b>System design</b> [Ch. 8]	TSTE86

# Switch Activity




Dynamic power dissipation is

$$P_d = I_{av} V_{DD} = \frac{Q_C}{T} V_{DD} = f C V_{DD} \cdot V_{DD} = a f_{clk} C V_{DD}^2$$

where  $a$  is the switch activity



# Sequential Logic

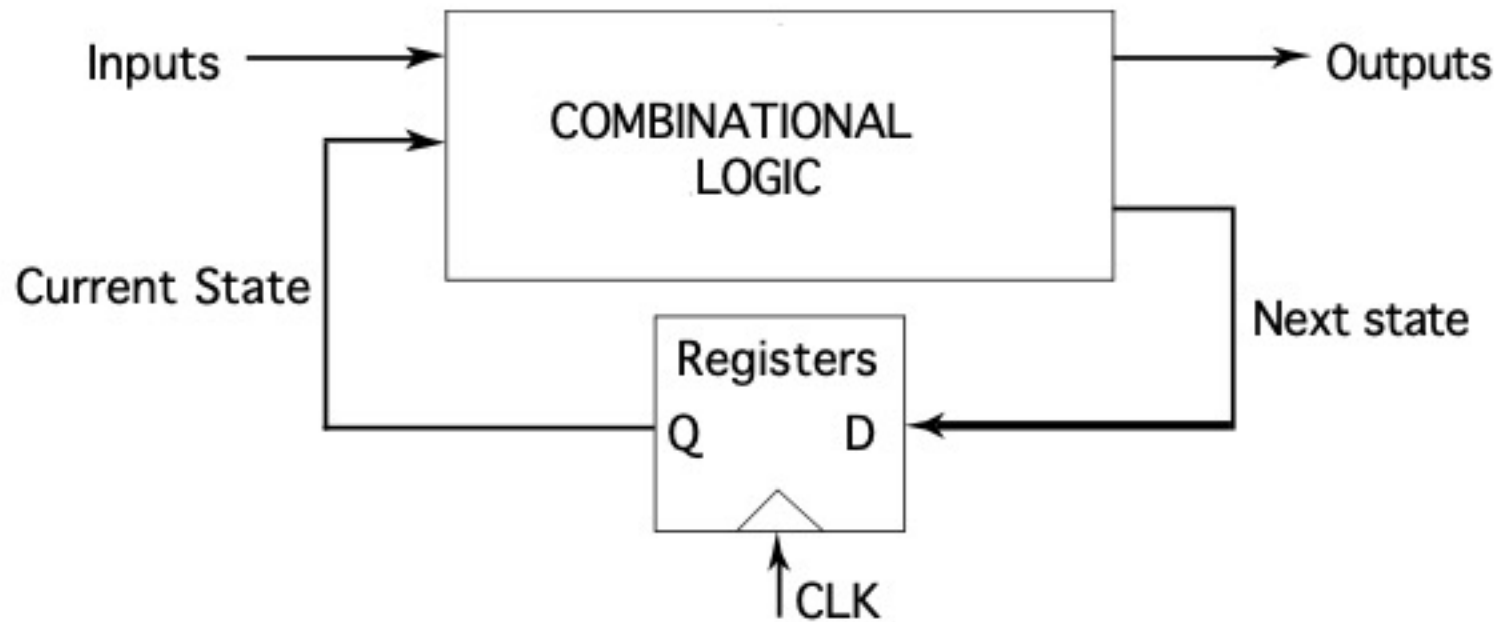

2 storage mechanisms

- positive feedback
- charge-based

# Pipelining

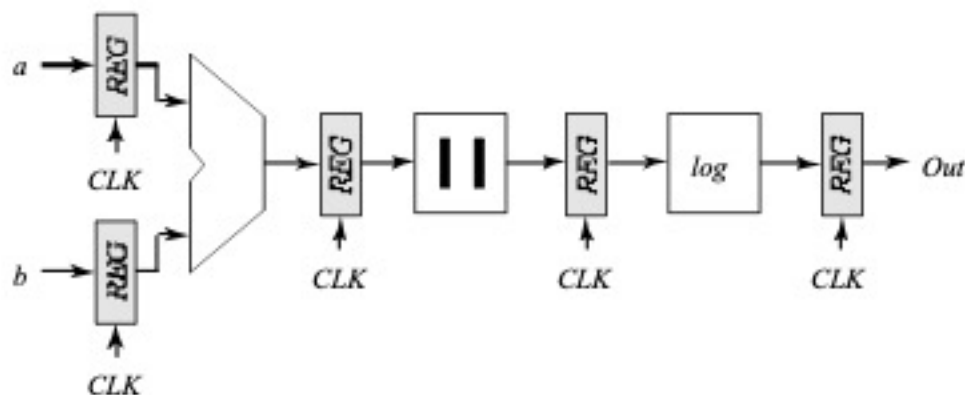
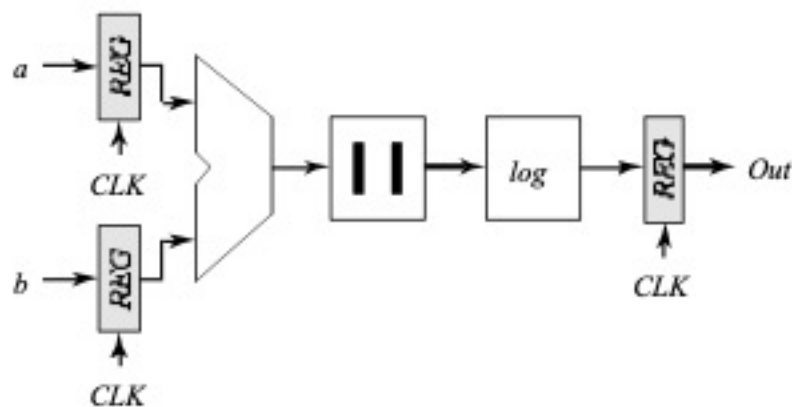


Reference


Clock Period	Adder	Absolute Value	Logarithm
1	$a_1 + b_1$		
2	$a_2 + b_2$	$ a_1 + b_1 $	
3	$a_3 + b_3$	$ a_2 + b_2 $	$\log(a_1 + b_1)$
4	$a_4 + b_4$	$ a_3 + b_3 $	$\log(a_2 + b_2)$
5	$a_5 + b_5$	$ a_4 + b_4 $	$\log(a_3 + b_3)$

Pipelined

# Transmission Gate

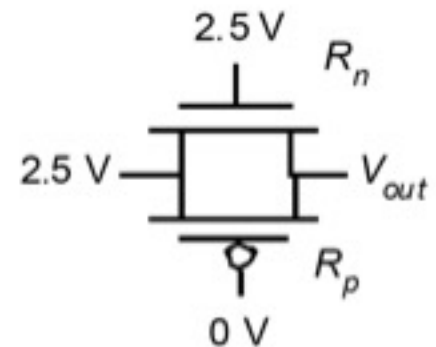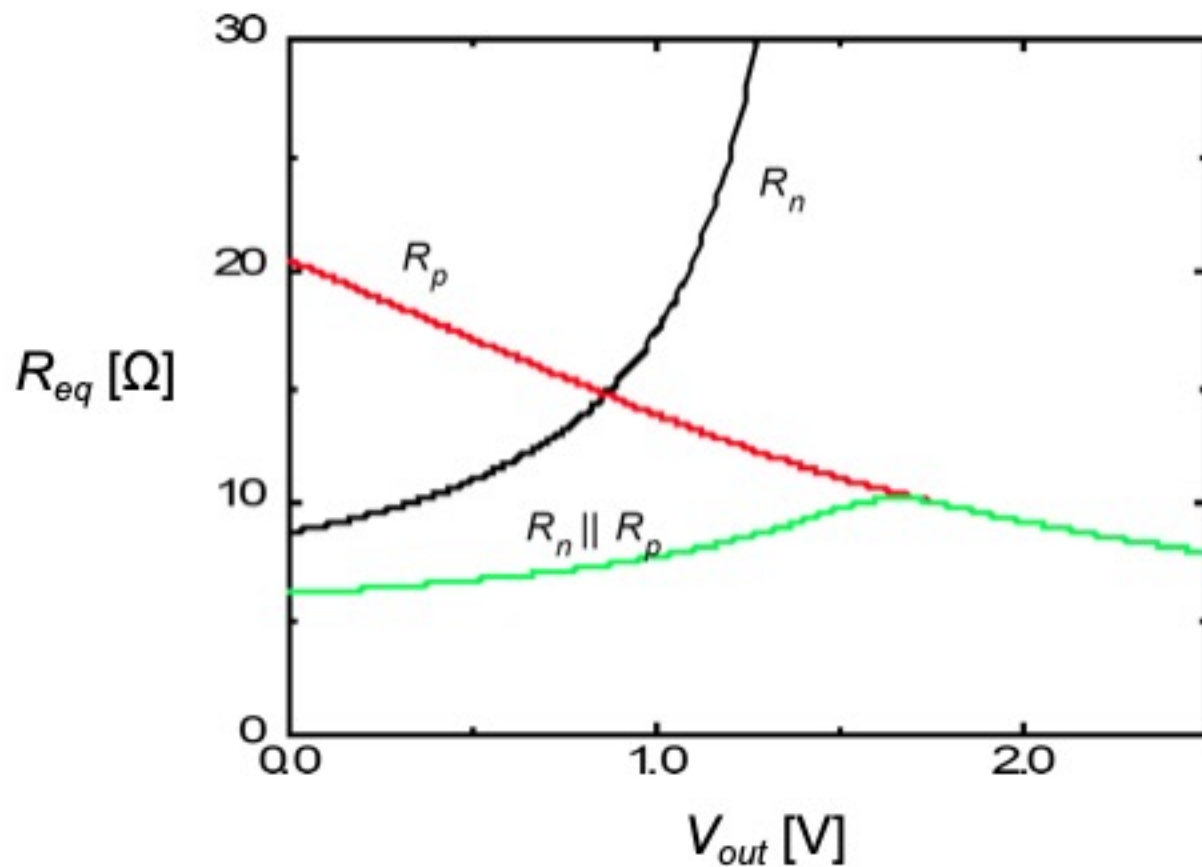


# Master-Slave Register


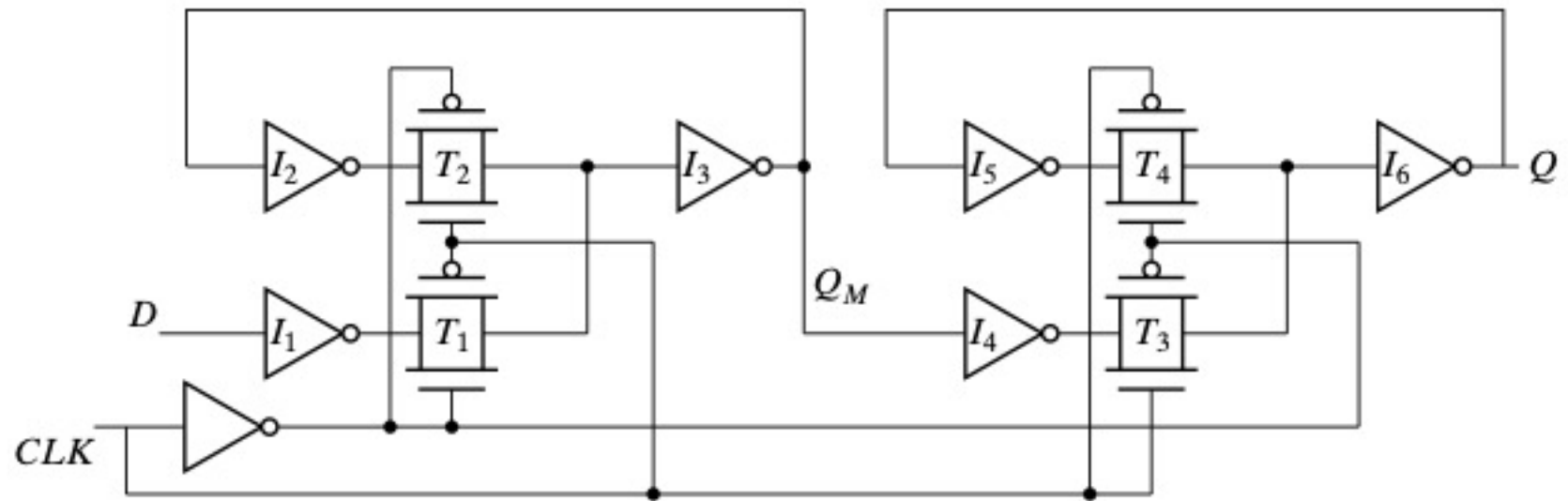


Multiplexer-based latch pair

# Positive Feedback

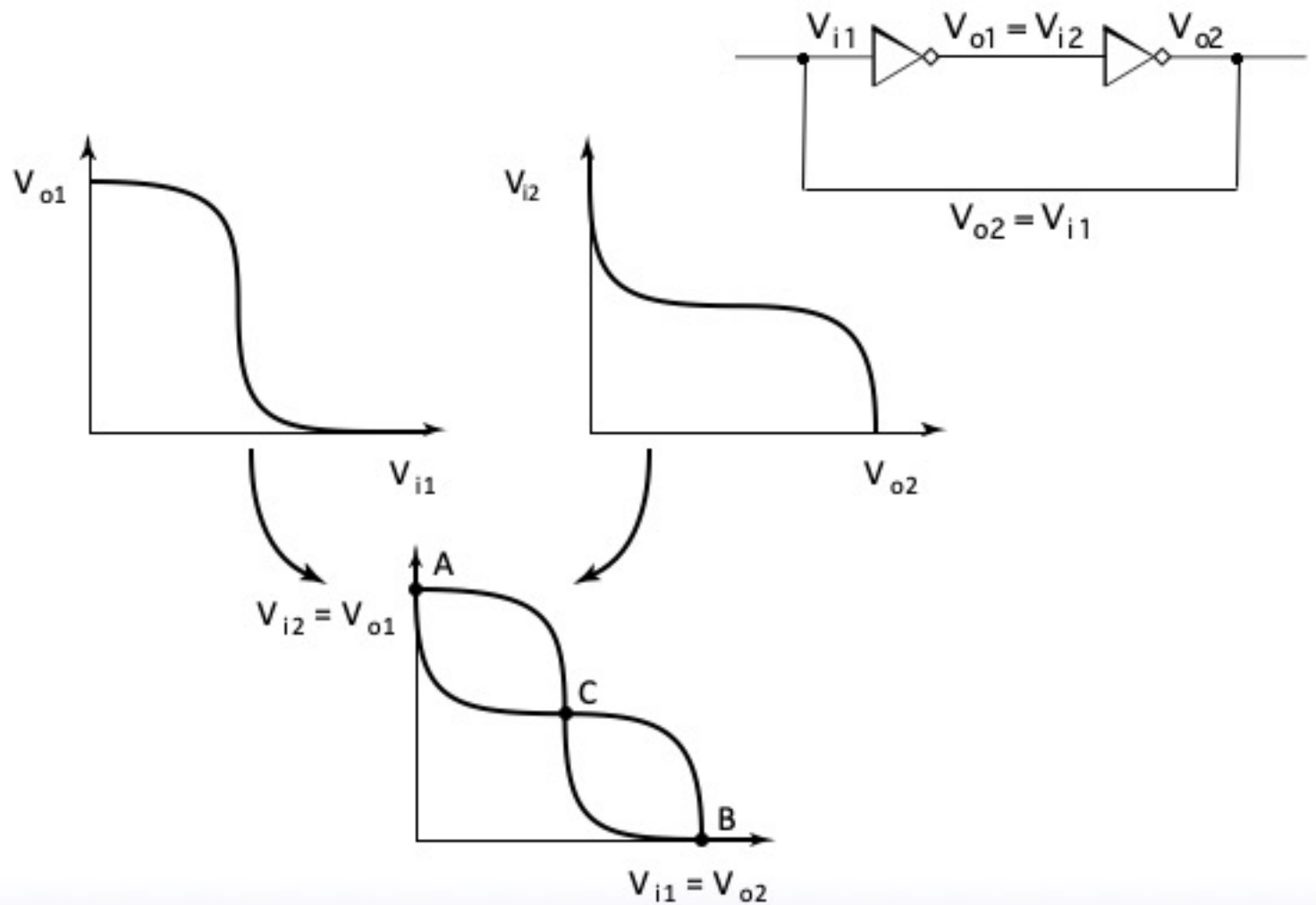


# Metastability

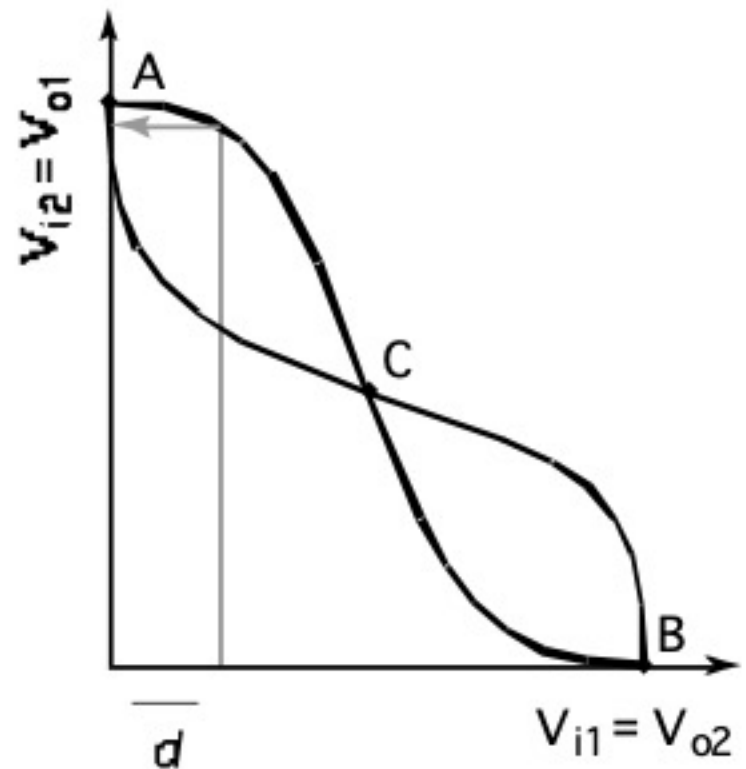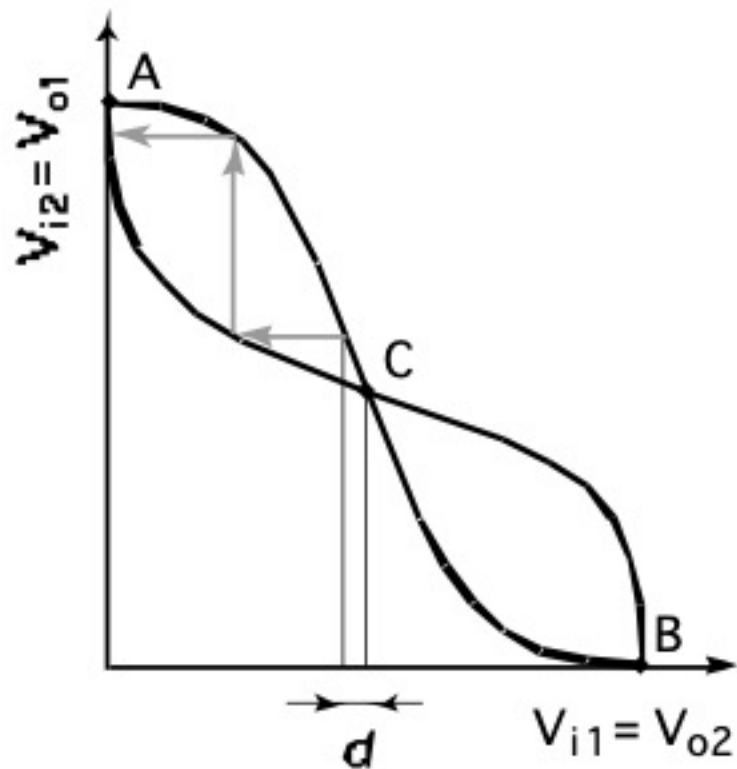


Gain is larger than 1 in the transition region



# Setup Time


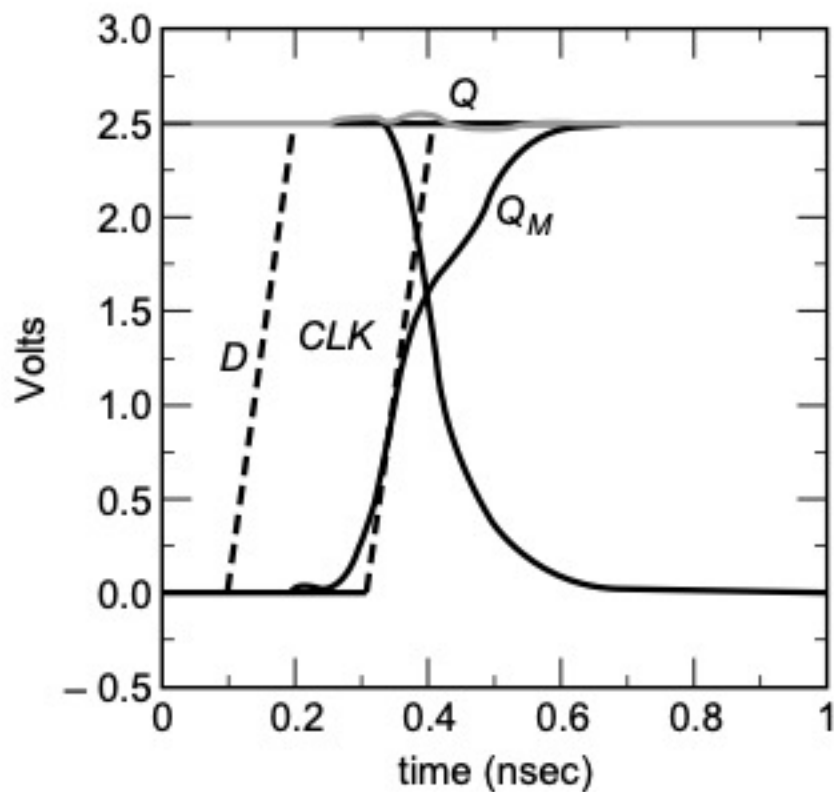


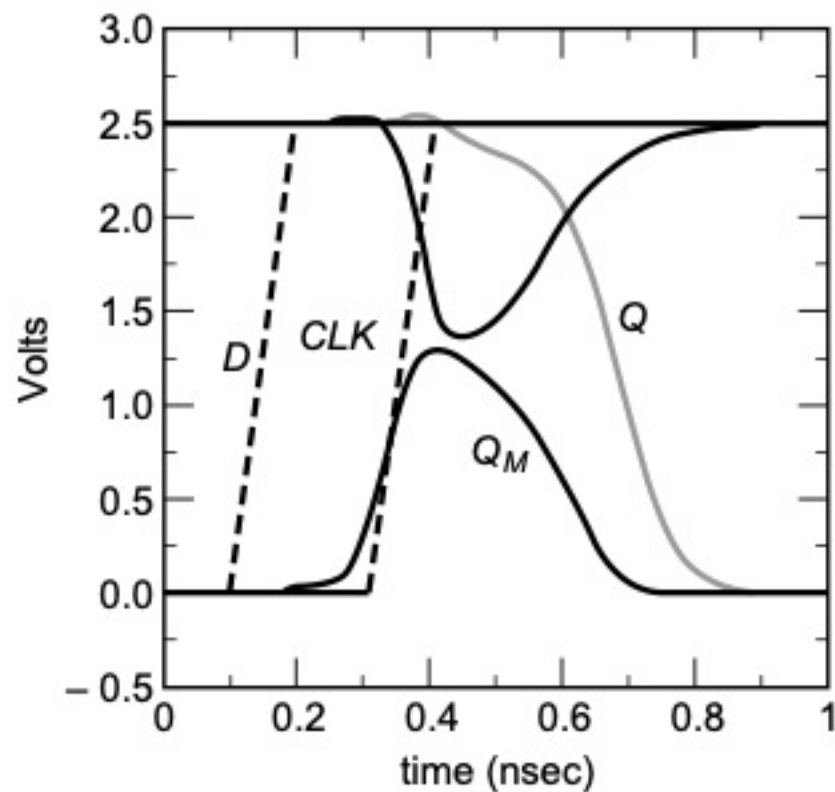(a)  $T_{D \rightarrow CLK} = 0.21$  nsec





(b)  $T_{D \rightarrow CLK} = 0.20$  nsec


# Setup and Hold Times

  


# Timing Definitions

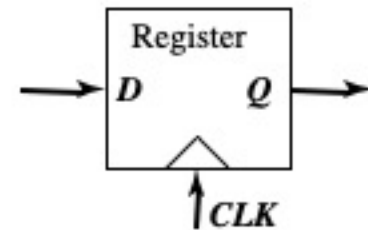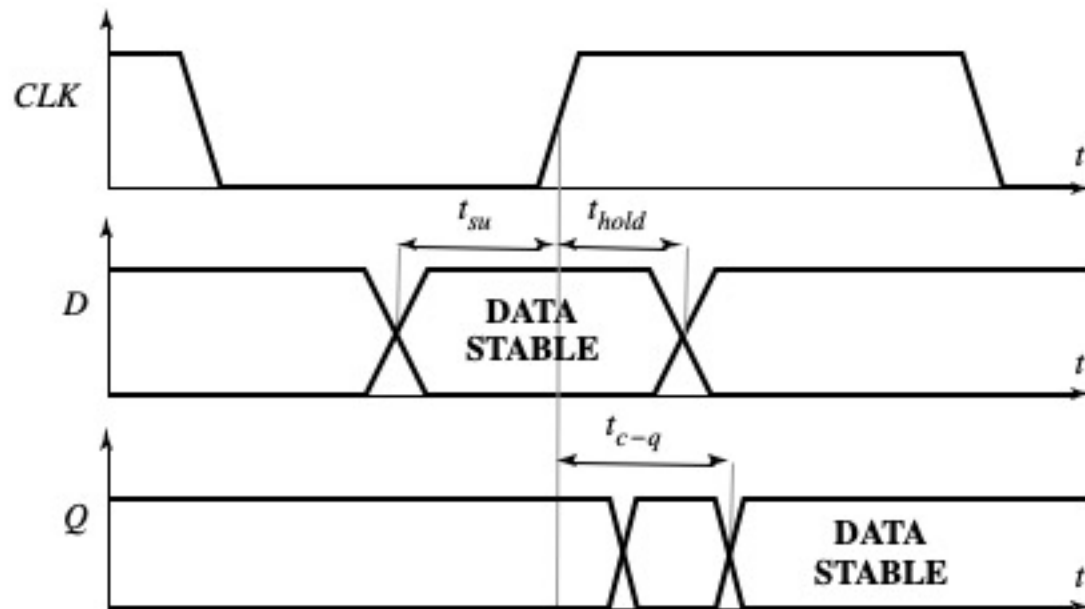

# Storage Mechanisms

 


Static latch

 


Dynamic latch

# Keeper

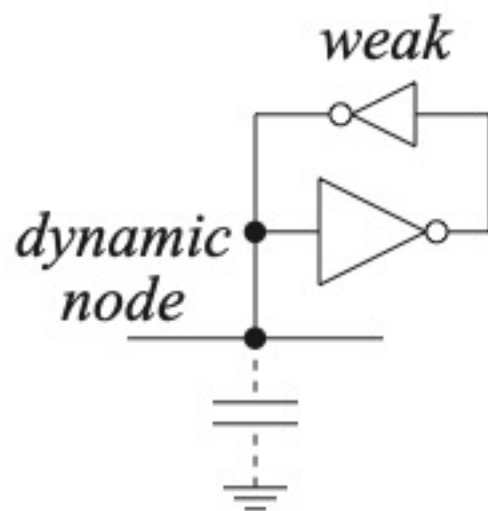


A keeper makes a dynamic circuit static

# C<sup>2</sup>MOS Dynamic Latch

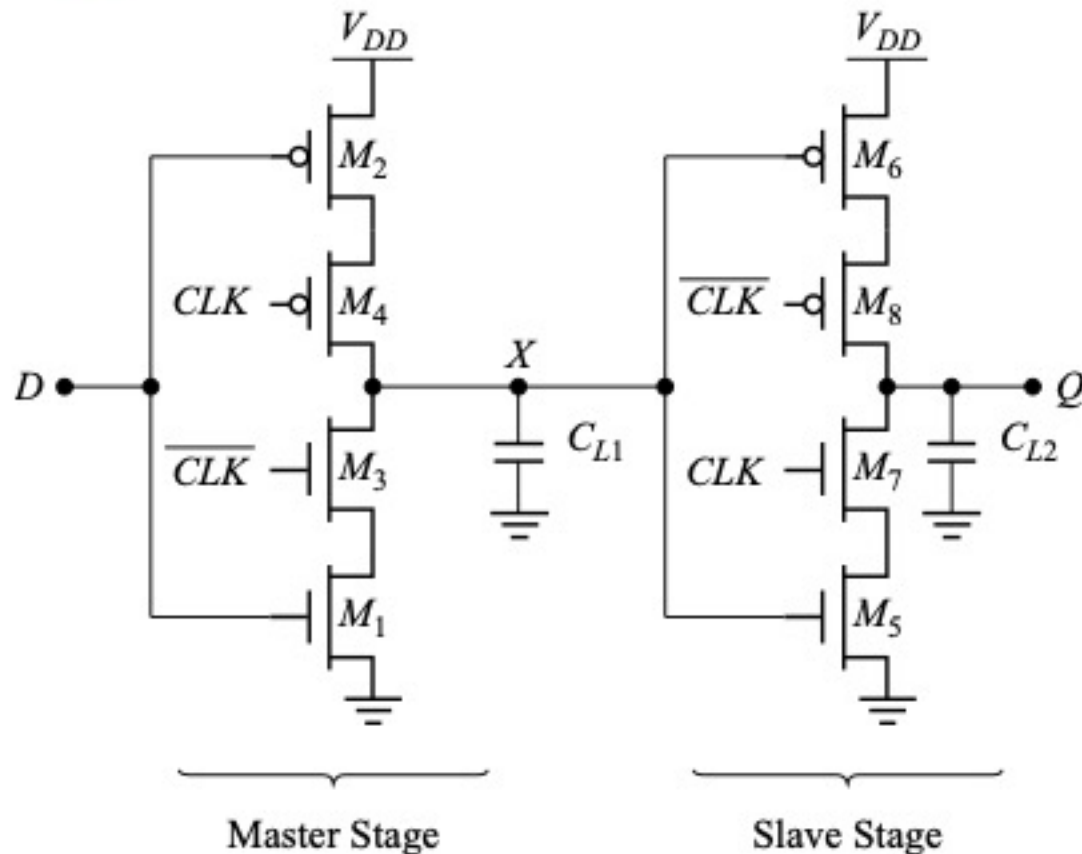


Keepers are often used to make the flip-flop static

# TSPC Dynamic Latch

 


 Positive latch  
(transparent when  $CLK = 1$ )




Negative latch  
(transparent when  $CLK = 0$ )

# Precharged Logic

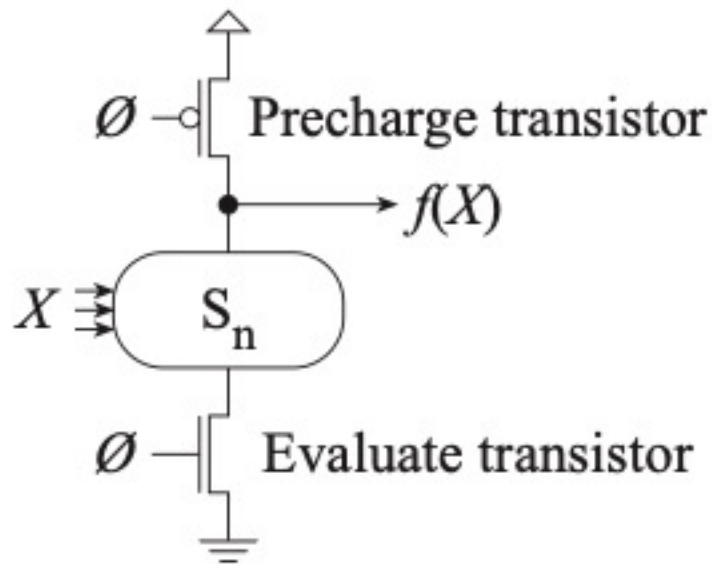


NMOS logic

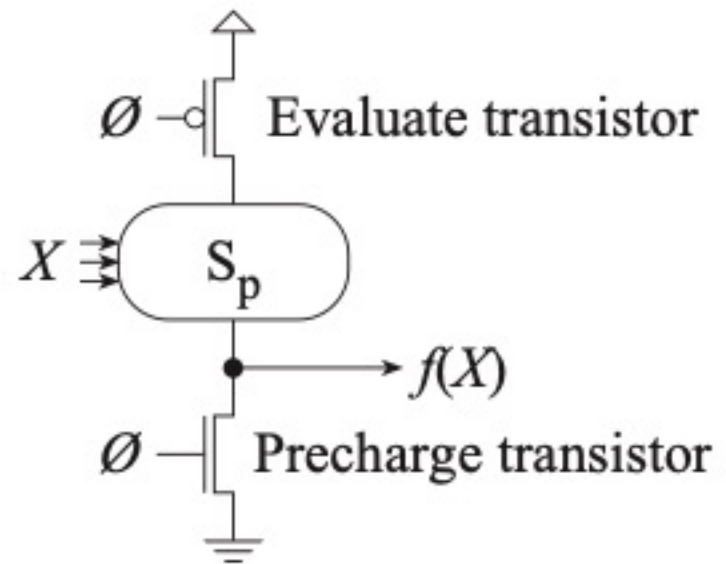


PMOS logic



# Operation

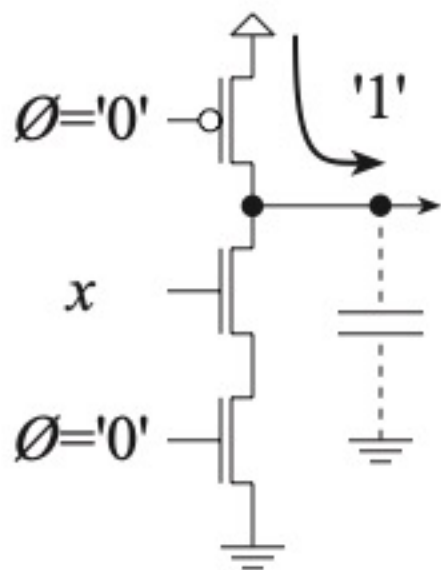


Precharge phase


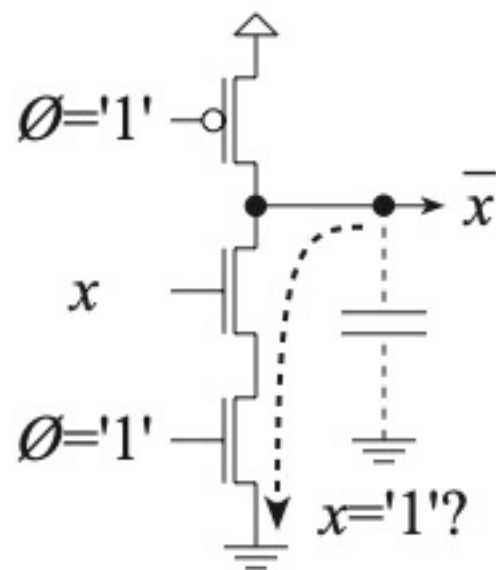


Evaluate phase

# Domino Logic

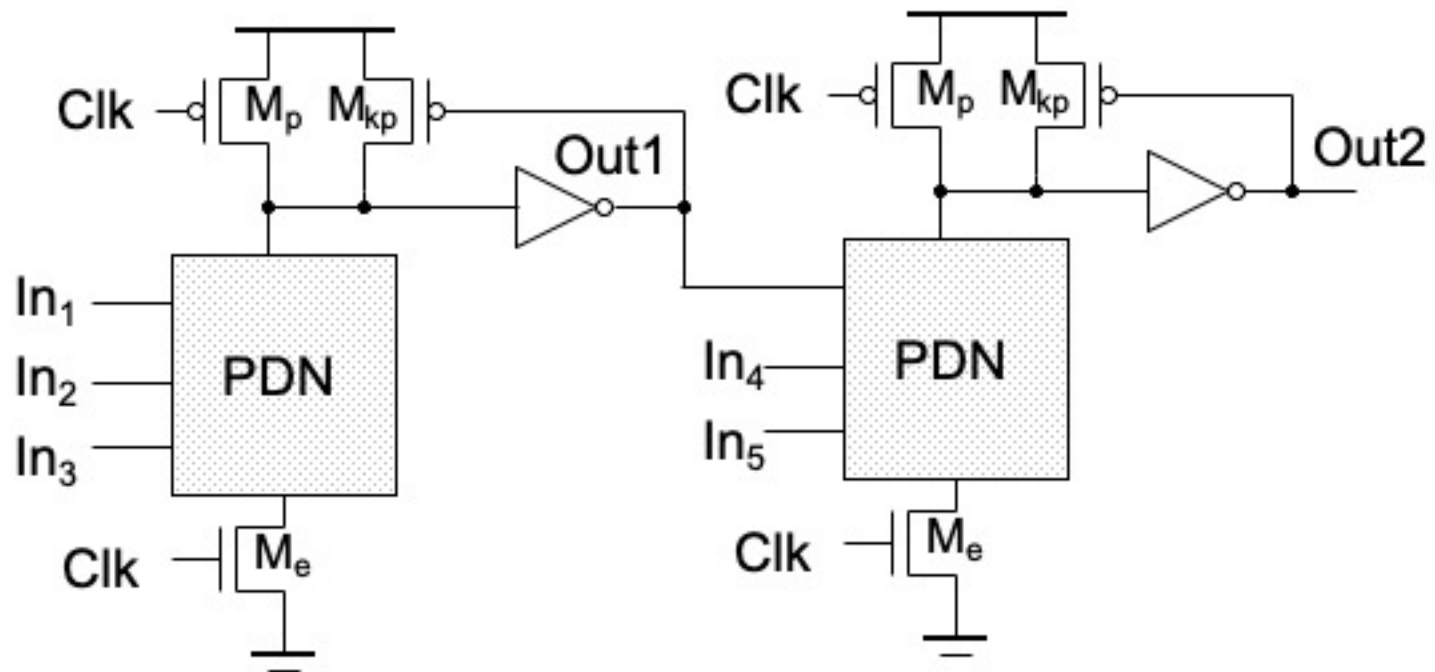


# Level Restoring Transistor

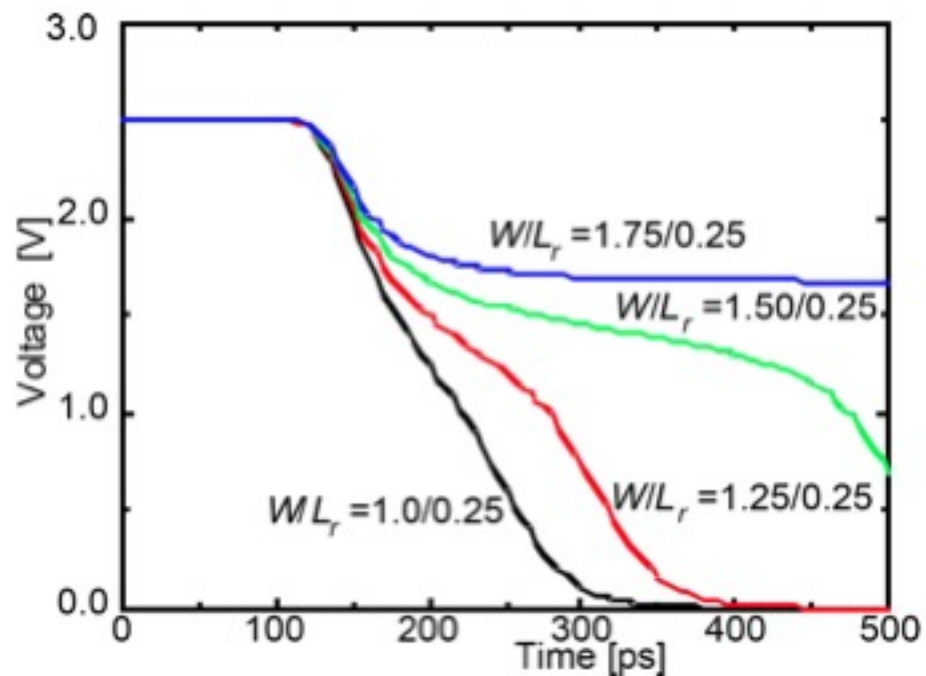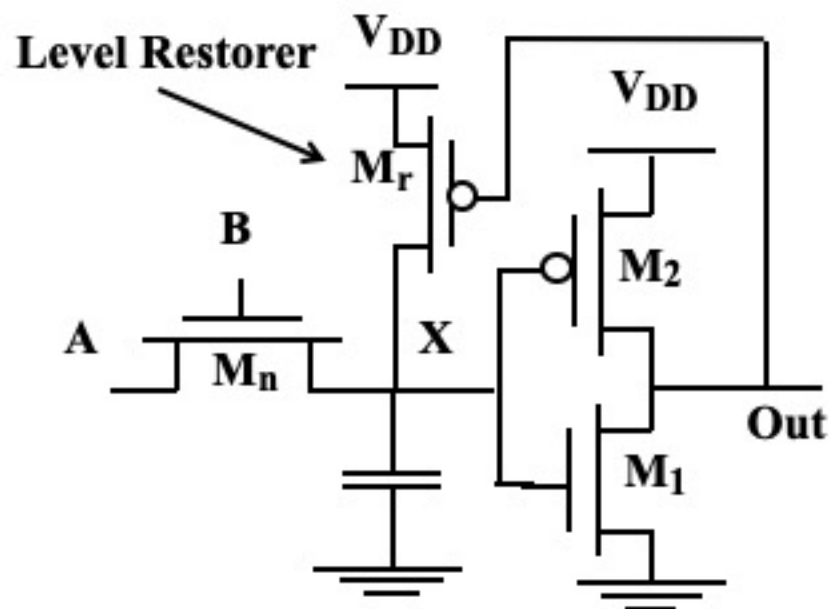


Useful in CPL and Domino logic

# Charge Sharing

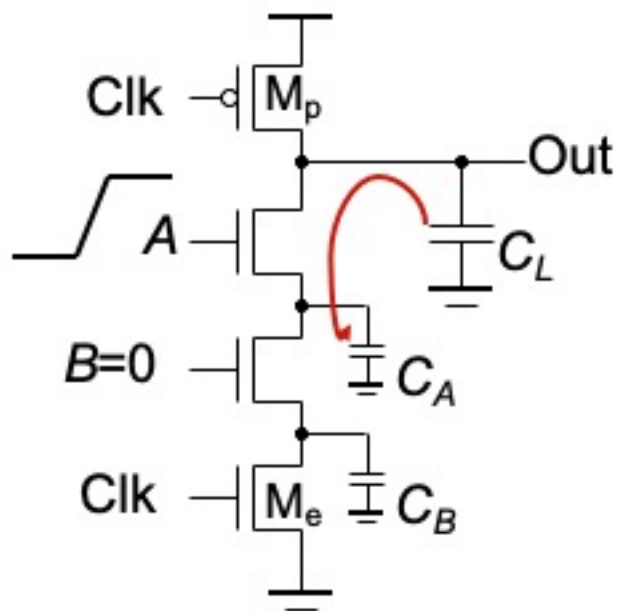


Charge stored originally on  $C_L$  is redistributed (shared) over  $C_L$  and  $C_A$  leading to reduced robustness

# Sub-Threshold Conduction

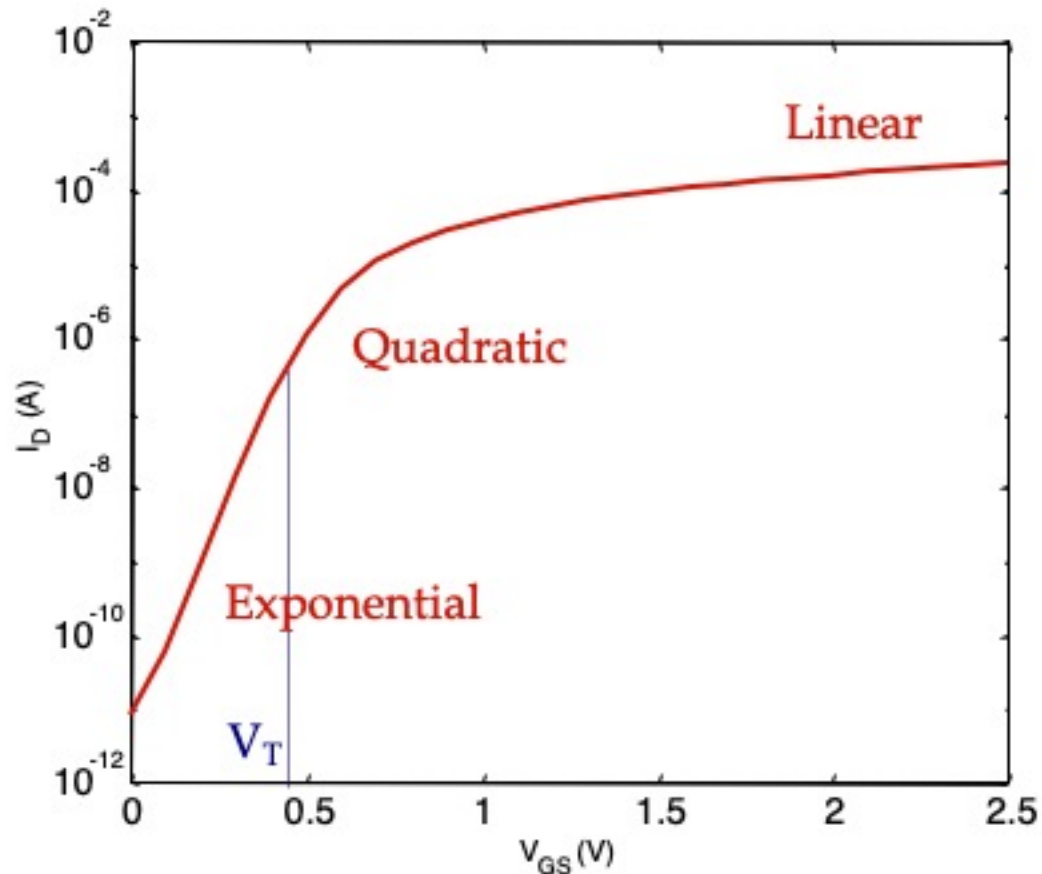


$$I_D = I_0 e^{\frac{qV_{GS}}{nkT}} \left( 1 - e^{-\frac{qV_{DS}}{kT}} \right)$$

# Charge Leakage

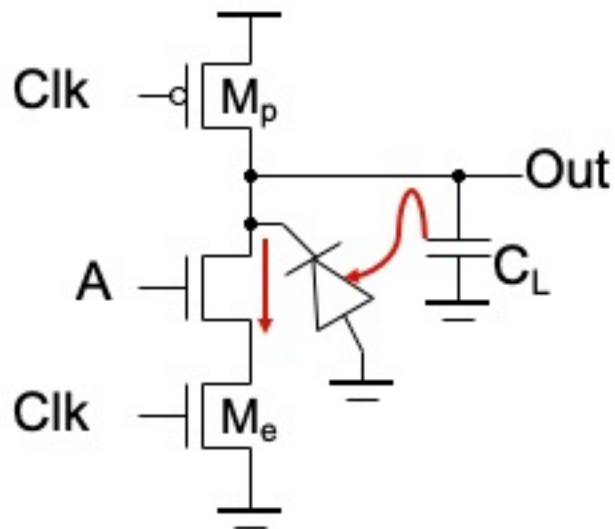

Leakage sources

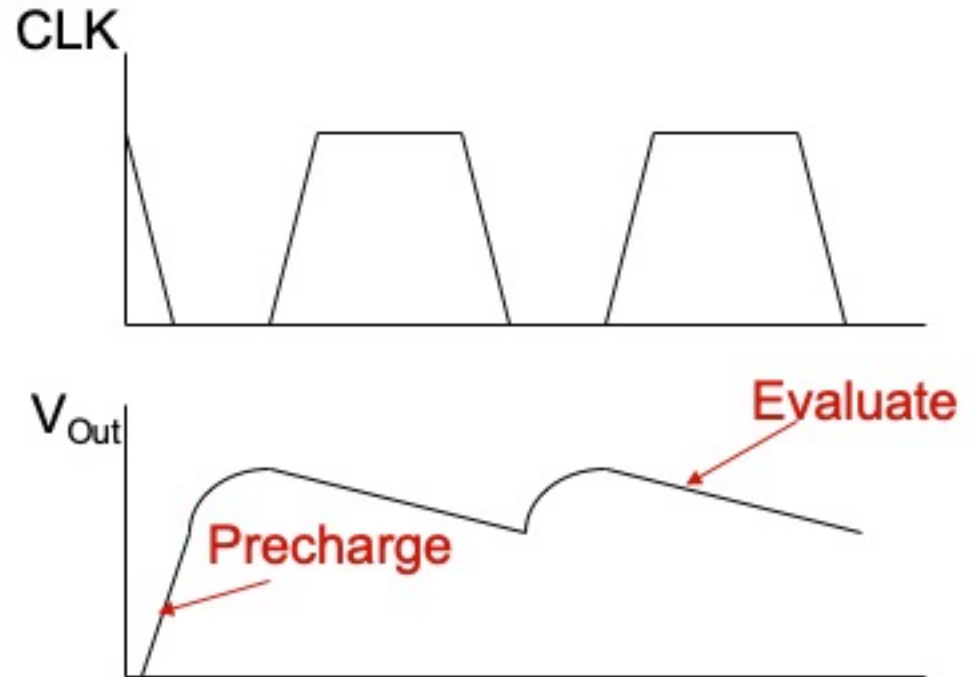

Dominant component is subthreshold current