

Exam TEN1 in TSTE86 Digital Integrated Circuits

Time: Tuesday 7 January 2020, 14:00–18:00

Place: U1

Responsible teacher: Mark Vesterbacka, phone 013-281324

Allowed aid: Calculator

Maximum score: 60 points

Grades:
45 points for 5
35 points for 4
25 points for 3

Solutions: Posted on the course web

Result: Posted through LADOK by 23 January 2020

1. A domino logic circuit realizing the function $F(A, B, C)$ is shown in Figure 1. The parasitic capacitances C_x , C_y , C_G , and C_F have been indicated in the schematic.

 


Figure 1. Schematic of a domino logic circuit.

- a) What logic function $F(A, B, C)$ has been implemented? (2 p)
 - b) What is the purpose of the MOSFETs clocked with \emptyset ? (2 p)
 - c) Can charge sharing occur in the circuit? Motivate your answer. (2 p)
 - d) Size the devices so that the worst-case output resistance of node G is the same as that of an inverter with an NMOS $W/L = 3$ and PMOS $W/L = 5$. (4 p)
2. An NMOS transistor is plugged into the test configuration shown in Figure 2. Determine the operation region, V_D , and V_S for the two cases below. For simplicity, assume $\lambda = 0$ and $\gamma = 0$.

 


Figure 2. Test configuration for NMOSFET.

- a) $R = 10 \text{ k}\Omega$. (5 p)
- b) $R = 30 \text{ k}\Omega$. (5 p)

3. A NAND gate shown to the left in Figure 3. To the right in Figure 3, there is a plot showing the output responses of the circuit due to different input transitions.

 


Figure 3. NAND gate and its output response due to different input patterns.

- a) Draw an equivalent *RC* switch model for this circuit that includes internal node capacitances. (4 p)
- b) Explain why case $A = 1 \rightarrow 0, B = 1 \rightarrow 0$ has the smallest delay. (3 p)
- c) Explain why case $A = 1 \rightarrow 0, B = 1$ is slower than case $A = 1, B = 1 \rightarrow 0$. (3 p)

4. A wire is used to connect two inverters as shown in Figure 4. The wire has length $L = 50$ mm, resistance per wire length $r = 0.075 \Omega/\mu\text{m}$, and capacitance per wire length $c = 0.11 \text{ fF}/\mu\text{m}$.

 


Figure 4. Two inverters connected by a long wire.

- a) Estimate the propagation delay between the input 'in' and node 'B' of this circuit. Assume the inverters are identical and have an inherent propagation delay $t_{inv} = 35$ ps and equivalent input/output capacitances $C_{in} = C_{out} = 5.0 \text{ fF}$. (6 p)
- b) What will be the propagation delay when an extra inverter is placed as a repeater in the middle of the wire? Assume the same delay and capacitances for this inverter as for the other two. (4 p)

5. Design a 3-bit Carry-Lookahead Adder (CLA) with inputs $A = \sum_{i=0}^2 a_i 2^i$, $B = \sum_{i=0}^2 b_i 2^i$, carry in c_{in} , and outputs $S = \sum_{i=0}^2 s_i 2^i = A + B$ and carry out c_{out} .
- State Boolean functions of the output bits s_i using propagate and generate functions. (3 p)
 - State the Boolean function of c_{out} using input bits a_i , b_i , and c_{in} . (3 p)
 - Estimate the critical path of an implementation that uses instances of gates with propagation delay according to Figure 5 below. (4 p)

Gate	Propagation delay
$\text{AND} = x \cdot y$	50 ps
$\text{ANDOR} = x \cdot y + z$	70 ps
$\text{XOR} = x \oplus y$	90 ps

Figure 5. Propagation delay of some basic gates.

6. Consider Design for Testability (DfT) for digital ICs.
- What is *observability*? (2 p)
 - What is *controllability*? (2 p)
 - What is an *ad-hoc test*? (2 p)
 - What is a *scan-based test*? (2 p)
 - What is a *built-in self-test*? (2 p)

Equations for the MOS transistor



Definition of source (S) and drain (D)

NMOS: $V_S \leq V_D$
PMOS: $V_S \geq V_D$

Voltage notations

$V_{GS} = V_G - V_S$, $V_{DS} = V_D - V_S$, $V_{SB} = V_S - V_B$, $V_{GT} = V_{GS} - V_T$

Threshold voltage

$$V_T = V_{T0} + \gamma \left(\sqrt{|V_{SB} - 2\Phi_F|} - \sqrt{2|\Phi_F|} \right)$$

Unified model

NMOS: $V_{GT} \leq 0$ (PMOS: $V_{GT} \geq 0$) \Rightarrow Subthreshold region ($I_D \approx 0$)

$$\text{NMOS: } V_{GT} \geq 0 \quad (\text{PMOS: } V_{GT} \leq 0) \Rightarrow I_D = k' \frac{W}{L} V_{min} \left(|V_{GT}| - \frac{V_{min}}{2} \right) (1 + \lambda V_{DS})$$

$$V_{min} = \min(|V_{GT}|, |V_{DS}|, |V_{DSAT}|)$$

$$V_{min} = |V_{GT}| \Rightarrow \text{saturation region}$$

$$V_{min} = |V_{DS}| \Rightarrow \text{resistive (linear, triode) region} (\lambda = 0)$$

$$V_{min} = |V_{DSAT}| \Rightarrow \text{velocity saturation region}$$

V_{DSAT} dependency on channel length

$$V_{DSAT} = L \xi_c$$

Subthreshold region

$$\text{NMOS: } V_{GT} \leq 0 \Rightarrow I_{Dn} = I_{Dn} \frac{W}{L} e^{\frac{q(V_{GSn} - V_{Tn})}{nkT}} \left(1 - e^{-\frac{qV_{DSn}}{kT}} \right) (1 + \lambda_n V_{DSn})$$

$$\text{PMOS: } V_{GT} \geq 0 \Rightarrow I_{Dp} = I_{Dp} \frac{W}{L} e^{\frac{q(V_{SGp} - |V_{Tp}|)}{nkT}} \left(1 - e^{-\frac{qV_{SDp}}{kT}} \right) (1 + \lambda_p V_{DSp})$$

Model parameters for 0.25 μm CMOS devices

Parameters for drain current calculations

	V_{T0} [V]	γ [$\sqrt{\text{V}}$]	V_{DSAT} [V]	k' [$\mu\text{A}/\text{V}^2$]	λ	Φ_F [V]
NMOS	0.43	0.40	0.63	115	0.06	-0.30
PMOS	-0.40	-0.40	-1.00	-30	-0.10	0.30

Parameters for capacitance calculations

	C_{ox} [fF/ μm^2]	C_O [fF/ μm]	C_j [fF/ μm^2]	m_j	ϕ_b [V]	C_{jsw} [fF/ μm]	m_{jsw}	$\Phi_{b_{sw}}$ [V]
NMOS	6	0.31	2.0	0.50	0.9	0.28	0.44	0.9
PMOS	6	0.27	1.9	0.48	0.9	0.22	0.32	0.9

Gate capacitance

Overlap capacitance

$$C_{GSO} = C_{GDO} = C_{ox} x_d W = C_O W$$

Channel capacitance

$$C_{GC} = C_{GCB} + C_{GCS} + C_{GCD}$$

Condition	C_{GCB}	C_{GCS}	C_{GCD}
$V_{GTn} \leq 0, V_{GTp} \geq 0$	$C_{ox} WL$	0	0
$V_{GTn} > 0, V_{GTp} < 0, V_{DS} \leq V_{GT} $	0	$C_{ox} WL/2$	$C_{ox} WL/2$
$V_{GTn} > 0, V_{GTp} < 0, V_{GT} \leq V_{DS} $	0	$2C_{ox} WL/3$	0

Junction capacitance

Junction capacitance as function of voltage

$$C_j(V) = \frac{C_{j0}}{(1 - V/\phi_0)^m}$$

Average capacitance during transition from V_1 to V_2

$$C_{eq} = K_{eq} C_{j0} = \frac{-\phi_0^m}{(V_2 - V_1)(1-m)} [(\phi_0 - V_2)^{(1-m)} - (\phi_0 - V_1)^{(1-m)}] C_{j0}$$

Dynamic power consumption

$$P = \alpha f C_{tot} V_{dd}^2$$

Switch functions

$$S_N = \overline{F(A, B, \dots)}, S_P = F(\bar{A}, \bar{B}, \dots)$$

Transmission line

Characteristic impedance

$$Z_0 = \sqrt{L/c}$$

Velocity of wave

$$v = 1/\sqrt{Lc}$$

Average capacitance during transition from V_1 to V_2

$$C_{eq} = K_{eq} C_{j0} = \frac{-\phi_0^m}{(V_2 - V_1)(1-m)} [(\phi_0 - V_2)^{(1-m)} - (\phi_0 - V_1)^{(1-m)}] C_{j0}$$

Elmore delay

P_i = “the path between node 0 and i ”.

$P_{ij} = P_i \cap P_j$ = “the common part of the paths P_i and P_j ”.

R_{ij} = “the sum of all resistances in P_{ij} ”.

Time constant from node 0 to i : $\tau_{di} = \sum_{j=0}^n R_{ij} C_j$. Propagation delay: $t_{pi} \approx 0.69 \tau_{di}$.

Boolean algebra

De Morgans’ theorem

$$\overline{X + Y + Z + \dots} = \overline{\overline{XYZ\dots}} = \overline{XYZ\dots}$$

Expansion in sum

$$f(X, Y, Z, \dots) = XY(1, Y, Z, \dots) + \bar{X}\bar{Y}(0, Y, Z, \dots)$$

Expansion in product

$$f(X, Y, Z, \dots) = [X + f(0, Y, Z, \dots)][\bar{X} + f(1, Y, Z, \dots)]$$

Sizing of cascaded inverters

For minimal propagation delay find the best solution to $1 = e^{(1+\gamma/k)/k}$, where k = “tapering factor”, N = “number of inverters”, $F = C_L/C_{g1} = k^N$ and $\gamma = C_{int1}/C_{g1}$.