

Solutions to exam 2019-08-30 in TSTE86 Digital ICs


1.

- a) Three inverters are needed if we implement F directly, while two are sufficient if we first implement the inverted function $G = \bar{F}$ and then invert the output to obtain F .

Design switch net functions for G :

$$G = \overline{A\bar{S} + BS} \Rightarrow \begin{cases} S_p = G(\bar{A}, \bar{B}, \bar{S}) = \overline{A\bar{S} + BS} = (A + \bar{S})(B + S) = AS + B\bar{S} \\ S_n = \overline{G(A, B, S)} = A\bar{S} + BS \end{cases}$$

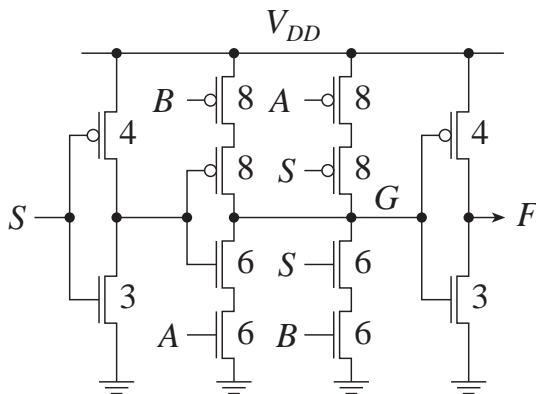Two CMOS inverters are added for inverting S and G . Complete transistor schematic:



- b) Aspect ratios are indicated directly by the transistors in the schematic above.

2.

- a) Find MOSFET's operating mode at V_M

$$\begin{aligned} V_{min} &= \min(V_{GT}, V_{DS}, V_{DSAT}) = \min(V_M - V_{Tn}, V_M, V_{DSAT}) = \\ &= \min(1.25 - 0.43, 1.25, 0.63) \text{ V} = 0.63 \text{ V} \Rightarrow \text{velocity saturated} \end{aligned}$$

Equate current through resistor with current through MOSFET to obtain R_L

$$\begin{aligned} \frac{V_{DD} - V_M}{R_L} &= k' \frac{W}{L} V_{min} \left(V_{GT} - \frac{V_{min}}{2} \right) (1 + \lambda V_{DS}) \Leftrightarrow \\ \frac{2.5 - 1.25}{R_L} &= 115 \cdot 10^{-6} \cdot \frac{2.5}{0.25} \cdot 0.63 \cdot \left(1.25 - 0.43 - \frac{0.63}{2} \right) (1 + 0.06 \cdot 1.25) \Rightarrow R_L \approx 3.2 \text{ k}\Omega \end{aligned}$$

- b) MOSFET is off during charge $\Rightarrow t_{pLH} = 0.69 R_L C_L$

Find t_{pHL} by discharging C_L from V_{DD} to $V_{DD}/2$

MOSFET's operating mode at $V_{out} = V_{DD}$

$$\begin{aligned} V_{min} &= \min(V_{GT}, V_{DS}, V_{DSAT}) = \min(V_{DD} - V_{Tn}, V_{DD}, V_{DSAT}) = \\ &= \min(2.5 - 0.43, 2.5, 0.63) \text{ V} = 0.63 \text{ V} \Rightarrow \text{velocity saturated} \end{aligned}$$

Derive an expression for the discharge current at V_{DD}

$$I_D(V_{DD}) = k' \frac{W}{L} V_{min} \left(V_{DD} - V_{Tn} - \frac{V_{min}}{2} \right) (1 + \lambda V_{DD}) =$$

$$= 115 \cdot 10^{-6} \cdot \frac{2.5}{0.25} \cdot 0.63 \cdot \left(2.5 - 0.43 - \frac{0.63}{2} \right) (1 + 0.06 \cdot 2.5) \text{ A} \approx 1.46 \cdot 10^{-3} \text{ A}$$

MOSFET's operating mode at $V_{out} = V_{DD} / 2$

$$V_{min} = \min \left(V_{DD} - V_{Tn}, \frac{V_{DD}}{2}, V_{DSAT} \right) =$$

$$= \min(2.5 - 0.43, 1.25, 0.63) \text{ V} = 0.63 \text{ V} \Rightarrow \text{velocity saturated}$$

Derive an expression for the discharge current at $V_{DD}/2$

$$I_D \left(\frac{V_{DD}}{2} \right) = k' \frac{W}{L} V_{min} \left(V_{DD} - V_{Tn} - \frac{V_{min}}{2} \right) \left(1 + \lambda \frac{V_{DD}}{2} \right) - \frac{V_{DD}/2}{R_L} =$$

$$= 115 \cdot 10^{-6} \cdot \frac{2.5}{0.25} \cdot 0.63 \cdot \left(2.5 - 0.43 - \frac{0.63}{2} \right) (1 + 0.06 \cdot 1.25) - \frac{1.25}{R_L} \text{ A} =$$

$$\approx 1.37 \cdot 10^{-3} \text{ A} - \frac{1.25}{R_L}$$

Approximate t_{pHL} by calculating discharge of C_L with average current


$$t_{pHL} = \frac{C_L V_{DD} - C_L \frac{V_{DD}}{2}}{\frac{1}{2} \left(I(V_{DD}) + I \left(\frac{V_{DD}}{2} \right) \right)} = \frac{C_L V_{DD}}{I(V_{DD}) + I \left(\frac{V_{DD}}{2} \right)} \approx \frac{C_L \cdot 2.5}{(1.46 + 1.37) \cdot 10^{-3} - \frac{1.25}{R_L}}$$

Equate t_{pLH} and t_{pHL} and solve for R_L

$$t_{pHL} = t_{pLH} \Rightarrow \frac{C_L \cdot 2.5}{(1.46 + 1.37) \cdot 10^{-3} - \frac{1.25}{R_L}} \approx 0.69 R_L C_L \Rightarrow R_L \approx 1.7 \text{ k}\Omega$$

3.

 a) RC-chain model with N identical segments




$$b) \tau = \frac{R}{N} \cdot \frac{C}{N} + \frac{2R}{N} \cdot \frac{C}{N} + \dots + \frac{NR}{N} \cdot \frac{C}{N} = \frac{RC}{N^2} \sum_{i=1}^N i = \frac{RC}{N^2} \cdot \frac{N(N+1)}{2} = \frac{RC}{2} \left(1 + \frac{1}{N} \right)$$

$$c) \lim_{N \rightarrow \infty} (\tau) = \frac{RC}{2} \lim_{N \rightarrow \infty} \left(1 + \frac{1}{N} \right) = \frac{RC}{2} \cdot 1 = \frac{RC}{2}$$


$$d) t_p = \ln(2) \tau \approx 0.35 RC$$

4. Techniques for dealing with capacitive cross talk
 1. Avoid floating nodes by e.g. introducing keeper devices.
 2. Separate sensitive nodes from full-swing signals.
 3. Make the rise and fall time as large as possible.
 4. Use differential signaling to turn cross talk into a common-mode noise.
 5. Avoid large capacitance between wires, e.g. parallel wires over long distance
 6. Provide a shielding wire connected to the ground or power supply between wires.
 7. Reduce interwire capacitance by adding extra routing layers.

 5.
 - a) Positive edge-triggered master-slave D flip-flop



- b) Timing diagram

 

Setup time t_{su} : The time before the rising edge of the clock that the input data D must be valid.


Hold time t_h : The time that the input must be held stable after the rising edge of the clock. Note that the hold time of a circuit can be negative in certain situations.

Clock-to-output delays $T_{c-q,LH}$ and $T_{c-q,HL}$: The time after the clock edge before the output Q is stable.


If the setup time or the hold time is violated the circuit might enter a metastable, undecided, state. The output will eventually reach a stable point, either high or low, but the final state will be more or less random.

6. Block schematics with critical path in red-dash (LS = least significant, MS = most significant)


a) Ripple-carry

 

 b) Ripple-carry with inverter elimination (two types of FA:s with carry inversion)



c) Carry-skip

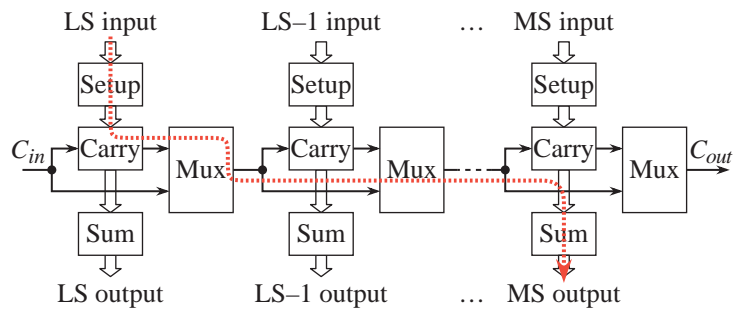

d) Carry-select

