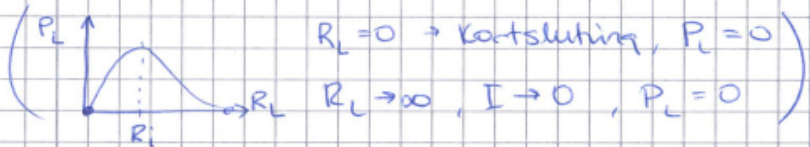


Lektion 2

2.1

$$\begin{aligned} \left/ \begin{aligned} P &= R \cdot I^2 \\ U &= (R_i + R_L)I \end{aligned} \right/ &\Rightarrow P_L = R_L \left(\frac{U}{R_i + R_L} \right)^2 \end{aligned}$$



$$\begin{aligned} \frac{dP_L}{dR_L} &= \left/ \frac{d}{dx} \frac{g(x)}{h(x)} = \frac{g'(x)h(x) - g(x)h'(x)}{h(x)^2} \right/ \\ &= \frac{U^2 (R_i + R_L) - R_L U^2 \cdot 2}{(R_i + R_L)^3} \\ &= U^2 (R_i - R_L) / (R_i + R_L)^3 \end{aligned}$$

Hitta max : $\frac{dP_L}{dR_L} = 0$ när $\underline{\underline{R_L = R_i}}$

Dubbelkolla maxipunkten mha
andradderivatan $\frac{2U^2 (R_L - 2R_i)}{(R_L + R_i)^4}$

a)

b) $\eta = \frac{P_L}{P_U} = \frac{R_L I^2}{(R_i + R_L) I^2} = \frac{R_L}{(R_i + R_L)}$

c) Maximal effekt fås när $R_L = R_i$. Sätt in det i uttrycket för effektivitet $\rightarrow \eta = \frac{R_i}{R_i + R_i} = 0.5$

2.2

$$\begin{aligned} \vec{V}_s &= \vec{V}_R + jX_L \vec{I} \\ \vec{I} &= \frac{\vec{V}_s - \vec{V}_R}{jX_L} \end{aligned}$$

$$\begin{aligned} \bar{S}_s &= 3 \cdot \frac{\vec{V}_s}{\sqrt{3}} \vec{I}^* = 3 \frac{\vec{V}_s}{\sqrt{3}} \left(\frac{\vec{V}_s - \vec{V}_R}{\sqrt{3} j X_L} \right)^* \\ &= j 3 \frac{\vec{V}_s}{\sqrt{3}} \left(\frac{\vec{V}_s - \vec{V}_R}{\sqrt{3} X_L} \right)^* = j \frac{\vec{V}_s \vec{V}_s^*}{X_L} - j \frac{\vec{V}_s \vec{V}_R^*}{X_L} \\ &= j \frac{V_s^2}{X_L} - j \frac{V_s V_R}{X_L} (\cos \psi - j \sin \psi) \\ &= j \frac{V_s^2}{X_L} - \frac{V_s V_R}{X_L} (j \cos \psi + \sin \psi) \end{aligned}$$

$$\begin{aligned} \bar{S}_s &= P_s + jQ_s \\ P_s &= -\frac{V_s V_R}{X_L} \sin \psi \\ Q_s &= \frac{V_s^2}{X_L} - \frac{V_s V_R}{X_L} \cos \psi \end{aligned}$$

$$\begin{aligned} \bar{S}_R &= 3 \frac{\vec{V}_R}{\sqrt{3}} \left(\frac{\vec{V}_s - \vec{V}_R}{\sqrt{3} j X_L} \right)^* \\ &= \frac{V_R V_s}{X_L} (j \cos \psi + \sin \psi) - j \frac{V_R^2}{X_L} \end{aligned}$$

$$\begin{aligned} P_R &= \frac{V_R V_s}{X_L} \sin \psi \\ Q_R &= \frac{V_s V_R}{X_L} \cos \psi - \frac{V_R^2}{X_L} \end{aligned}$$

2.5

120:460 V
 $Z_{eq} = 0.013 + j0.042 \text{ pu.}$

$$S_{base} = 15 \text{ kVA}$$

$$V_{baseL} = 120 \text{ V}, \quad V_{baseH} = 460 \text{ V}$$

$$(Z_{base} = V_{base}^2 / S_{base})$$

$$Z_{baseL} = 120^2 / 15000 = 0.96 \Omega$$

$$Z_{baseH} = 460^2 / 15000 = 14.1 \Omega$$

$$(Z_{pu} = Z_{actual \ value} / Z_{base} \rightarrow)$$

$$Z_{eqL} = Z_{eq} \cdot Z_{baseL} = 0.017 + j0.040 \Omega$$

$$Z_{eqH} = Z_{eq} \cdot Z_{baseH} = 0.25 + j0.60 \Omega$$

2.6

First the base values in each zone are determined. $S_{\text{base}} = 30 \text{ kVA}$ is the same for the entire network. Also, $V_{\text{base1}} = 240 \text{ volts}$, as specified for zone 1. When moving across a transformer, the voltage base is changed in proportion to the transformer voltage ratings. Thus,

$$V_{\text{base2}} = \left(\frac{480}{240}\right)(240) = 480 \text{ volts}$$

and

$$V_{\text{base3}} = \left(\frac{115}{460}\right)(480) = 120 \text{ volts}$$

The base impedances in zones 2 and 3 are

$$Z_{\text{base2}} = \frac{V_{\text{base2}}^2}{S_{\text{base}}} = \frac{480^2}{30,000} = 7.68 \text{ } \Omega$$

and

$$Z_{\text{base3}} = \frac{V_{\text{base3}}^2}{S_{\text{base}}} = \frac{120^2}{30,000} = 0.48 \text{ } \Omega$$

and the base current in zone 3 is

$$I_{\text{base3}} = \frac{S_{\text{base}}}{V_{\text{base3}}} = \frac{30,000}{120} = 250 \text{ A}$$

Next, the per-unit circuit impedances are calculated using the system base values. Since $S_{\text{base}} = 30 \text{ kVA}$ is the same as the kVA rating of transformer T_1 , and $V_{\text{base1}} = 240 \text{ volts}$ is the same as the voltage rating of the zone 1 side of transformer T_1 , the per-unit leakage reactance of T_1 is the same as its nameplate value, $X_{T1\text{p.u.}} = 0.1$ per unit. However, the per-unit leakage reactance of transformer T_2 must be converted from its nameplate rating to the system base. Using (3.3.11) and $V_{\text{base2}} = 480 \text{ volts}$,

$$X_{T2\text{p.u.}} = (0.10) \left(\frac{460}{480}\right)^2 \left(\frac{30,000}{20,000}\right) = 0.1378 \text{ per unit}$$

Alternatively, using $V_{\text{base3}} = 120 \text{ volts}$,

$$X_{T2\text{p.u.}} = (0.10) \left(\frac{115}{120}\right)^2 \left(\frac{30,000}{20,000}\right) = 0.1378 \text{ per unit}$$

which gives the same result. The line, which is located in zone 2, has a per-unit reactance

$$X_{\text{linep.u.}} = \frac{X_{\text{line}}}{Z_{\text{base2}}} = \frac{2}{7.68} = 0.2604 \text{ per unit}$$

and the load, which is located in zone 3, has a per-unit impedance

$$Z_{\text{loadp.u.}} = \frac{Z_{\text{load}}}{Z_{\text{base3}}} = \frac{0.9 + j0.2}{0.48} = 1.875 + j0.4167 \text{ per unit}$$

The per-unit circuit is shown in Figure 3.10(b), where the base values for each zone, per-unit impedances, and the per-unit source voltage are shown. The per-unit load current is then easily calculated from Figure 3.10(b) as follows:

$$\begin{aligned} I_{\text{loadp.u.}} = I_{\text{sp.u.}} &= \frac{V_{\text{sp.u.}}}{j(X_{T1\text{p.u.}} + X_{\text{linep.u.}} + X_{T2\text{p.u.}}) + Z_{\text{loadp.u.}}} \\ &= \frac{0.9167 \angle 0^\circ}{j(0.10 + 0.2604 + 0.1378) + (1.875 + j0.4167)} \\ &= \frac{0.9167 \angle 0^\circ}{1.875 + j0.9149} = \frac{0.9167 \angle 0^\circ}{2.086 \angle 26.01^\circ} \\ &= 0.4395 \angle -26.01^\circ \text{ per unit} \end{aligned}$$

The actual load current is

$$I_{\text{load}} = (I_{\text{loadp.u.}})I_{\text{base3}} = (0.4395 \angle -26.01^\circ) (250) = 109.9 \angle -26.01^\circ \text{ A}$$

Note that the per-unit equivalent circuit of Figure 3.10(b) is relatively easy to analyze, since ideal transformer windings have been eliminated by proper selection of base values.

