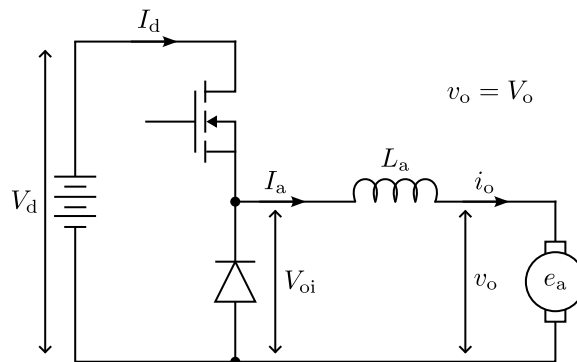


Försättsblad till skriftlig tentamen vid Linköpings Universitet

Datum för tentamen	2023-10-20
Sal	TER1, TERD, TERF
Tid	14-18
Kurskod	TSTE25
Provkod	TEN1
Kursnamn	Effektelektronik (Power Electronics)
Institution	ISY
Antal uppgifter som ingår i tentamen	5
Antal sidor på tentamen (inkl. försättsbladet)	5
Jour/kursansvarig	Lars Eriksson
Telefon under skrivtid	079-061 20 73 (Arvind)
Besöker salen ca.	15 och 17
Tillåtna hjälpmedel	Vetenskaplig räknare, miniräknare, 1 A4 medformler och information
Övrigt	Betygsgränser: 20 poäng = godkänd

1. (a) (1 point) Draw the ideal characteristics for the Diode.
 (b) (2 points) Draw the MOSFET drain current and the drain-to-source voltage when a positive pulse voltage is applied across the gate-source terminal.
 (c) (2 points) When are the ideal characteristics used, and when are the more complicated characteristics (non-ideal) used?

2. The switched dc-dc step-down converter shown in Figure 1 controls a dc machine with an armature inductance $L_a = 0.2 \text{ mH}$. The armature resistance can be neglected. The armature current i_o is 5 A. The switching frequency $f_{\text{sw}} = 30 \text{ kHz}$ and the duty cycle, $D = 0.8$. Consider all the components to be ideal.




Figur 1: Step-down DC-DC converter.

- (a) (1 point) The output voltage, $V_o = 200 \text{ V}$. Calculate the input voltage, V_d .
- (b) (2 points) Find the ripple in the armature current.
- (c) (2 points) Calculate the maximum and the minimum value of the armature current.
- (d) (2 points) The load on the machine is reduced. Calculate I_a when the converter is on the boundary between continuous and discontinuous mode.
- (e) (4 points) The load on the DC machine gives $I_a = 2 \text{ A}$. Is the converter in discontinuous mode?
 Note: The duty-cycle of the converter is changed

3. An n-channel power MOSFET, a VMO 400-02F made by IXYS, is to be used in a converter (*datasheet is attached*). The MOSFET is to conduct a continuous current of 300 A when on and the switching frequency is 10 kHz with a 50% duty cycle. The input voltage is 100 V. The internal junction temperature is not to exceed 100°C and the maximum ambient temperature is 35°C .
 - (a) (5 points) Calculate the total MOSFET power losses (assume the same time for voltage and current transients, i.e., $t_{\text{ri}} = t_{\text{fv}} = t_{\text{r}}$ and $t_{\text{fi}} = t_{\text{rv}} = t_{\text{f}}$).
 - (b) (2 points) Specify the thermal resistance of the required heat sink (Assume that the MOSTFET has no heat transfer paste).
 - (c) (2 points) Determine the peak MOSFET drain-to-source voltage during the switching transient if the blocking voltage (MOSFET drain-to-source voltage when it is completely turned off) is 100 V and the parasitic inductance is 100 nH.

4. The output voltages and current of a single-phase full-bridge inverter are shown in the figure. Determine the following:
- (1 point) Type of modulation (unipolar or bipolar).
 - (2 points) Switching frequency.
 - (3 points) Inductance.
 - (2 points) Peak fundamental current.
 - (2 points) Pole-to-pole DC-link voltage (V_d) and modulation index (m_a).
 - (2 points) Active power on the load at the fundamental frequency.
 - (1 point) Phase angle of the fundamental current with respect to the inverter side voltage.
 - (2 points) Active and reactive power on the converter at the fundamental frequency.

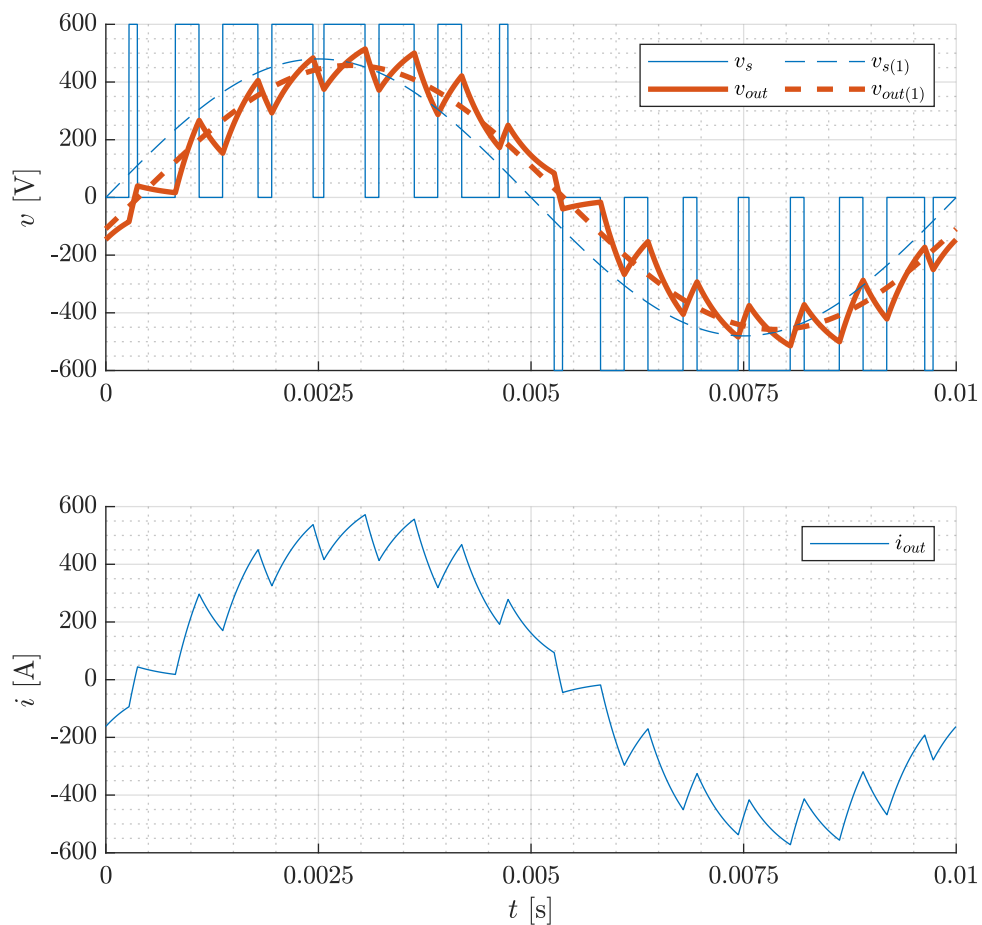

Figur 2: Single-phase DC to AC full-bridge inverter output waveforms.

5. The problem with ripple in the output current from a single-phase full bridge converter is to be studied. The first harmonic of the output voltage is given by $V_{o(1)}$ at $f_1 = 50$ Hz. The load is given in the figure as $L = 10$ mH in series with an ideal voltage source $e_o(t)$. It is assumed that the converter operates in sinusoidal PWM mode, bipolar modulation.

$$e_o(t) = \sqrt{2} 220 \sin(2\pi f_1 t)$$

- (a) (1 point) The frequency of the triangular signal is 1050 Hz. Calculate the frequency modulation ratio (or pulse number), m_f .
- (b) (1 point) Find the dc-voltage when the converter fundamental RMS output voltage $V_{o(1)}$ is 230 V and modulation index, $m_a = 0.6$.
- (c) (2 points) Determine the RMS fundamental output current (i.e., current through the inductor).
- (d) (3 points) Determine the RMS and frequency of the highest output ripple current component.
- (e) (3 points) If a Unipolar modulation is used, determine the RMS and frequency of the highest output ripple current component.

Note: Ripple here is referred to as distortion, which is the alteration of the original shape of a signal. Here ripple means the alteration of the waveform from an ideal sinusoidal signal.

Tabell 1: Generalized harmonics of a half-bridge inverter output voltage for a large m_f .

$h \downarrow \quad m_a \rightarrow$	0.2	0.4	0.6	0.8	1
1	0.2	0.4	0.6	0.8	1
Fundamental					
m_f	1.242	1.15	1.006	0.818	0.6023
$m_f \pm 2$	0.061	0.061	0.131	0.22	0.318
$m_f \pm 4$					0.018
$2m_f \pm 1$	0.19	0.326	0.37	0.314	0.181
$2m_f \pm 3$		0.024	0.071	0.139	0.212
$2m_f \pm 5$				0.013	0.033
$3m_f$	0.335	0.123	0.083	0.171	0.133
$3m_f \pm 2$	0.044	0.139	0.203	0.176	0.062
$3m_f \pm 4$		0.012	0.047	0.104	0.157
$3m_f \pm 6$				0.016	0.044
$4m_f \pm 1$	0.163	0.157	0.088	0.105	0.068
$4m_f \pm 3$	0.012	0.070	0.132	0.115	0.009
$4m_f \pm 5$			0.034	0.084	0.119
$4m_f \pm 7$				0.017	0.05

Note: output voltage (\hat{V}_o) is $\hat{V}_o = m_a V_d/2$.





MegaMOS™FET Module

VMO 400-02F

$V_{DSS} = 200 \text{ V}$
 $I_{D25} = 418 \text{ A}$
 $R_{DS(on)} = 4.2 \text{ m}\Omega$

N-Channel Enhancement Mode

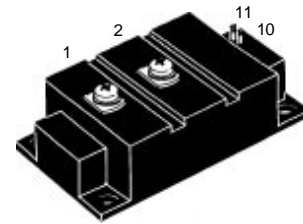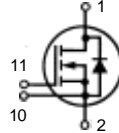

1 = Drain 2 = Source
 10 = Kelvin Source 11 = Gate

Symbol	Test Conditions	Maximum Ratings	
V_{DSS}	$T_J = 25^\circ\text{C}$ to 150°C	200	V
V_{DGR}	$T_J = 25^\circ\text{C}$ to 150°C ; $R_{GS} = 10 \text{ k}\Omega$	200	V
V_{GS}	Continuous	± 20	V
V_{GSM}	Transient	± 30	V
I_{D25}	$T_K = 25^\circ\text{C}$	418	A
I_{DM}	$T_K = 25^\circ\text{C}$, $t_p = 10 \mu\text{s}$	1672	A
P_D	$T_C = 25^\circ\text{C}$	2450	W
	$T_K = 25^\circ\text{C}$	1640	W
T_J		-40 ... +150	$^\circ\text{C}$
T_{JM}		150	$^\circ\text{C}$
T_{stg}		-40 ... +125	$^\circ\text{C}$
V_{ISOL}	50/60 Hz $t = 1 \text{ min}$	3000	V~
	$I_{ISOL} \leq 1 \text{ mA}$ $t = 1 \text{ s}$	3600	V~
M_d	Mounting torque (M6)	2.25-2.75/20-25	Nm/lb.in.
	Terminal connection torque (M5)	2.5-3.7/22-33	Nm/lb.in.
Weight	typical including screws	250	g

Features

- International standard package
- Direct Copper Bonded Al_2O_3 ceramic base plate
- Isolation voltage 3600 V~
- Low $R_{DS(on)}$ HDMOS™ process
- Low package inductance for high speed switching
- Kelvin Source contact for easy drive

Applications

- AC motor speed control for electric vehicles
- DC servo and robot drives
- Switched-mode and resonant-mode power supplies
- DC choppers

Advantages

- Easy to mount
- Space and weight savings
- High power density
- Low losses


Symbol	Test Conditions	Characteristic Values ($T_J = 25^\circ\text{C}$, unless otherwise specified)		
		min.	typ.	max.
V_{DSS}	$V_{GS} = 0 \text{ V}$, $I_D = 12 \text{ mA}$	200		V
$V_{GS(th)}$	$V_{DS} = 20 \text{ V}$, $I_D = 120 \text{ mA}$	3		6 V
I_{GSS}	$V_{GS} = \pm 20 \text{ V DC}$, $V_{DS} = 0$			$\pm 500 \text{ nA}$
I_{DSS}	$V_{DS} = V_{DSS}^*$, $V_{GS} = 0 \text{ V}$, $T_J = 25^\circ\text{C}$			2.5 mA
	$V_{DS} = 0.8 \cdot V_{DSS}^*$, $V_{GS} = 0 \text{ V}$, $T_J = 125^\circ\text{C}$			12 mA
$R_{DS(on)}$	$V_{GS} = 10 \text{ V}$, $I_D = 0.5 \cdot I_{D25}$ Pulse test, $t \leq 300 \mu\text{s}$, duty cycle $d \leq 2\%$			4.2 m Ω

IXYS reserves the right to change limits, test conditions, and dimensions.

IXYS Corporation
 3540 Bassett Street, Santa Clara, CA 95054
 Tel: 408-982-0700 Fax: 408-496-0670

IXYS Semiconductor
 Edisonstr. 15, D-68623 Lampertheim, Germany
 Tel: +49-6206-5030 Fax: +49-6206-503629

Symbol	Test Conditions	Characteristic Values ($T_J = 25^\circ\text{C}$, unless otherwise specified)		
		min.	typ.	max.
g_{fs}	$V_{DS} = 10\text{ V}; I_D = 0.5 \cdot I_{D25}$ pulsed		380	S
C_{iss}	$V_{GS} = 0\text{ V}, V_{DS} = 25\text{ V}, f = 1\text{ MHz}$		53	nF
C_{oss}			9.6	nF
C_{rss}			3.4	nF
$t_{d(on)}$	$V_{GS} = 10\text{ V}, V_{DS} = 0.5 \cdot V_{DSS}, I_D = 0.5 \cdot I_{D25}$ $R_G = 1\ \Omega$ (External)		210	ns
t_r			500	ns
$t_{d(off)}$			900	ns
t_f			350	ns
Q_g	$V_{GS} = 10\text{ V}, V_{DS} = 0.5 \cdot V_{DSS}, I_D = 0.5 \cdot I_{D25}$		2300	nC
Q_{gs}			420	nC
Q_{gd}			1150	nC
R_{thJC}				0.051 K/W
R_{thJK}	with 30 μm heat transfer paste			0.076 K/W

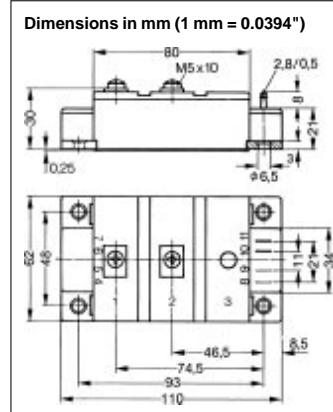

Symbol	Test Conditions	Characteristic Values ($T_J = 25^\circ\text{C}$, unless otherwise specified)		
		min.	typ.	max.
I_S	$V_{GS} = 0\text{ V}$			418 A
I_{SM}	Repetitive; pulse width limited by T_{JM}			1672 A
V_{SD}	$I_F = I_S; V_{GS} = 0\text{ V}$, Pulse test, $t \leq 300\ \mu\text{s}$, duty cycle $d \leq 2\%$		0.9	1.2 V
t_{rr}	$I_F = I_S, -di/dt = 1200\text{ A}/\mu\text{s}, V_{DS} = 100\text{ V}$		600	ns