

1. You probably figured this one out :)

2. The switched dc-dc step-down converter shown in Figure 1 controls a dc machine with an armature inductance  $L_a = 0.2$  mH. The armature resistance can be neglected. The armature current  $i_o$  is 5 A. The switching frequency  $f_{sw} = 30$  kHz and the duty cycle,  $D = 0.8$ . Consider all the components to be ideal.

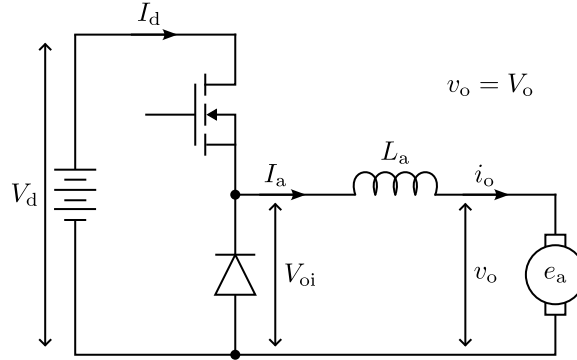


Figure 1: Step-down DC-DC converter.

- (a) **The output voltage,  $V_o = 200$  V. Calculate the input voltage,  $V_d$ .**  
The duty cycle is given by

$$D = \frac{V_o}{V_d}$$

The input voltage is

$$V_d = \frac{V_o}{D} = \frac{200}{0.8} = 250 \text{ V.}$$

- (b) **Find the ripple in the armature current.**

The peak-to-peak armature (inductor) current ripple ( $\Delta I_a$ ) is

$$\Delta I_a = \frac{D}{L f_{sw}} (V_d - V_o) = \frac{0.8}{200 \times 10^{-6} \times 30 \times 10^3} (250 - 200) = 6.67 \text{ A}$$

- (c) **Calculate the maximum and the minimum value of the armature current.**

The average armature current  $I_a = 5$  A. The peak armature current ripple  $\delta I_a$  is

$$\delta I_a = \frac{\Delta I_a}{2} = 3.33 \text{ A}$$

The maximum and minimum values of the armature current ( $I_a^{\max}$  and  $I_a^{\min}$ , respectively) are

$$I_a^{\max} = I_a + \delta I_a = 8.33 \text{ A}$$

$$I_a^{\min} = I_a - \delta I_a = 1.67 \text{ A}$$

- (d) **The load on the machine is reduced. Calculate  $I_a$  when the converter is on the boundary between continuous and discontinuous mode.**

The peak-to-peak armature (inductor) current ripple ( $\Delta I_a$ ) is

$$\Delta I_a = \frac{D}{L f_{sw}} (V_d - V_o) = \frac{D}{L f_{sw}} (V_d - D V_d) = \frac{D(1-D)}{L f_{sw}} V_d.$$

From the above equation, it is clear that  $\Delta I_a$  is maximum when  $D = 0.5$ . Therefore, The armature current ripple when the converter is on the boundary between continuous and discontinuous mode ( $\Delta I_a^B$ ) is

$$\Delta I_a^B = \frac{V_d}{4 L f_{sw}} = \frac{250}{4 \times 0.2 \times 10^{-3} \times 30 \times 10^3} = 10.42 \text{ A.}$$

The average armature current ( $I_a^B$ ) is

$$I_a^B = \frac{I_a^B}{2} = \frac{10.42}{2} = 5.21 \text{ A.}$$

- (e) **The load on the DC machine gives  $I_a' = 2 \text{ A}$ . Is the converter in discontinuous mode? Note: The duty cycle of the converter is changed.**

If the armature current is 5 A ( $I_a$ ) at 50% duty-cycle ( $D$ ), then the armature current ( $I_a'$ ) is 2 A, the duty-cycle ( $D'$ ) is

$$D' = \frac{I_a' D}{I_a} = \frac{2 \times 0.8}{5} = 0.32.$$

The peak-to-peak armature (inductor) current ripple ( $\Delta I_a'$ ) is

$$\Delta I_a' = \frac{D' (1 - D')}{L f_{sw}} V_d = \frac{0.32 (1 - 0.32)}{200 \times 10^{-6} \times 30 \times 10^3} \times 250 = 9.07 \text{ A}$$

The average armature current  $I_a' = 2 \text{ A}$ . The peak armature current ripple  $\delta I_a'$  is

$$\delta I_a' = \frac{\Delta I_a'}{2} = 4.53 \text{ A}$$

The maximum and minimum values of the armature current ( $I_a'^{\max}$  and  $I_a'^{\min}$ , respectively) are

$$\begin{aligned} I_a'^{\max} &= I_a' + \delta I_a' = 6.53 \text{ A} \\ I_a'^{\min} &= I_a' - \delta I_a' = -2.53 \text{ A} \end{aligned}$$

Since  $I_a'^{\min} < 0$ , the converter is in discontinuous mode.

3. An n-channel power MOSFET, a VMO 400-02F made by IXYS, is to be used in a converter (datasheet is attached). The MOSFET is to conduct a continuous current of 300 A when on and the switching frequency is 10 kHz with a 50% duty cycle. The input voltage is 100 V. The internal junction temperature is not to exceed 100°C and the maximum ambient temperature is 35°C.

- (a) **Calculate the total MOSFET power losses (assume the same time for voltage and current transients, i.e.,  $t_{ri} = t_{fv} = t_r$  and  $t_{fi} = t_{rv} = t_f$ ).**

From the MOSFET datasheets, the on-state resistance of the MOSFET ( $r_{ds(on)}$ ) and the switching transient times are

$$r_{ds(on)} = 4.2 \text{ m}\Omega \quad t_{ri} = t_{fv} = 500 \text{ ns}, \quad t_{rv} = t_{fi} = 350 \text{ ns}.$$

The conduction losses of the MOSFET ( $P_c^l$ ) is

$$P_c^l = D I_{v(\max)}^2 r_{ds(on)} = 0.5 \times 300^2 \times 4.2 \times 10^{-3} = 189 \text{ W}.$$

The switching losses of the MOSFET ( $P_s^l$ ) is

$$\begin{aligned} P_s^l &= \frac{1}{2} V_d I_v t_{sw} f_{sw} = \frac{1}{2} V_d I_v (t_{ri} + t_{fv} + t_{rv} + t_{fi}) f_{sw} \\ &= \frac{1}{2} \times 100 \times 300 \times (2 \times 500 \times 10^{-9} + 2 \times 350 \times 10^{-9}) \times 10 \times 10^3 = 255 \text{ W}. \end{aligned}$$

The total losses in the MOSFET ( $P^l$ ) is

$$P^l = P_c^l + P_s^l = 189 + 255 = 444 \text{ W}.$$

- (b) **Specify the thermal resistance of the required heat sink (Assume that the MOSFET has no heat transfer paste).**

The thermal resistance of the required heat sink is calculated as follows:

$$\begin{aligned} \Delta T_{ja} &= P^l (R_{\theta jc} + R_{\theta ca}) & \implies R_{\theta ca} &= \frac{\Delta T_{ja}}{P^l} - R_{\theta jc} \\ R_{\theta ca} &= \frac{100 - 35}{444} - 0.051 = 0.0954 \text{ K/W}. \end{aligned}$$

- (c) **Determine the peak MOSFET drain-to-source voltage during the switching transient if the blocking voltage (MOSFET drain-to-source voltage when it is completely turned off) is 100 V and the parasitic inductance near the MOSFET drain terminal is 100 nH.**

The voltage across the MOSFET during the turn-off transient is

$$V_{ds}^{\max} = V_d - L \frac{dV_{ds}}{dt} = 100 - 100 \times 10^{-9} \times \frac{0 - 300}{350 \times 10^{-9}} = 185.71 \text{ V}.$$





# MegaMOS™ FET Module

## VMO 400-02F

$V_{DSS} = 200\text{ V}$   
 $I_{D25} = 418\text{ A}$   
 $R_{DS(on)} = 4.2\text{ m}\Omega$

N-Channel Enhancement Mode

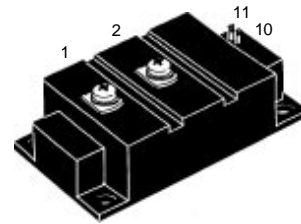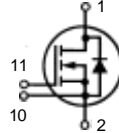

1 = Drain                      2 = Source  
 10 = Kelvin Source        11 = Gate

Symbol	Test Conditions	Maximum Ratings	
$V_{DSS}$	$T_J = 25^\circ\text{C}$ to $150^\circ\text{C}$	200	V
$V_{DGR}$	$T_J = 25^\circ\text{C}$ to $150^\circ\text{C}$ ; $R_{GS} = 10\text{ k}\Omega$	200	V
$V_{GS}$	Continuous	$\pm 20$	V
$V_{GSM}$	Transient	$\pm 30$	V
$I_{D25}$	$T_K = 25^\circ\text{C}$	418	A
$I_{DM}$	$T_K = 25^\circ\text{C}$ , $t_p = 10\ \mu\text{s}$	1672	A
$P_D$	$T_C = 25^\circ\text{C}$	2450	W
	$T_K = 25^\circ\text{C}$	1640	W
$T_J$		-40 ... +150	$^\circ\text{C}$
$T_{JM}$		150	$^\circ\text{C}$
$T_{stg}$		-40 ... +125	$^\circ\text{C}$
$V_{ISOL}$	50/60 Hz $t = 1\text{ min}$	3000	V~
	$I_{ISOL} \leq 1\text{ mA}$ $t = 1\text{ s}$	3600	V~
$M_d$	Mounting torque (M6)	2.25-2.75/20-25	Nm/lb.in.
	Terminal connection torque (M5)	2.5-3.7/22-33	Nm/lb.in.
<b>Weight</b>	typical including screws	250	g

### Features

- International standard package
- Direct Copper Bonded  $\text{Al}_2\text{O}_3$  ceramic base plate
- Isolation voltage 3600 V~
- Low  $R_{DS(on)}$  HDMOS™ process
- Low package inductance for high speed switching
- Kelvin Source contact for easy drive

### Applications

- AC motor speed control for electric vehicles
- DC servo and robot drives
- Switched-mode and resonant-mode power supplies
- DC choppers

### Advantages

- Easy to mount
- Space and weight savings
- High power density
- Low losses


Symbol	Test Conditions	Characteristic Values ( $T_J = 25^\circ\text{C}$ , unless otherwise specified)		
		min.	typ.	max.
$V_{DSS}$	$V_{GS} = 0\text{ V}$ , $I_D = 12\text{ mA}$	200		V
$V_{GS(th)}$	$V_{DS} = 20\text{ V}$ , $I_D = 120\text{ mA}$	3		6 V
$I_{GSS}$	$V_{GS} = \pm 20\text{ V DC}$ , $V_{DS} = 0$			$\pm 500\text{ nA}$
$I_{DSS}$	$V_{DS} = V_{DSS}^*$ , $V_{GS} = 0\text{ V}$ , $T_J = 25^\circ\text{C}$			2.5 mA
	$V_{DS} = 0.8 \cdot V_{DSS}^*$ , $V_{GS} = 0\text{ V}$ , $T_J = 125^\circ\text{C}$			12 mA
$R_{DS(on)}$	$V_{GS} = 10\text{ V}$ , $I_D = 0.5 \cdot I_{D25}$ Pulse test, $t \leq 300\ \mu\text{s}$ , duty cycle $d \leq 2\%$			4.2 m $\Omega$

IXYS reserves the right to change limits, test conditions, and dimensions.

IXYS Corporation  
 3540 Bassett Street, Santa Clara, CA 95054  
 Tel: 408-982-0700 Fax: 408-496-0670

IXYS Semiconductor  
 Edisonstr. 15, D-68623 Lampertheim, Germany  
 Tel: +49-6206-5030 Fax: +49-6206-503629

Symbol	Test Conditions	Characteristic Values ( $T_J = 25^\circ\text{C}$ , unless otherwise specified)		
		min.	typ.	max.
$g_{fs}$	$V_{DS} = 10\text{ V}; I_D = 0.5 \cdot I_{D25}$ pulsed		380	S
$C_{iss}$	$V_{GS} = 0\text{ V}, V_{DS} = 25\text{ V}, f = 1\text{ MHz}$		53	nF
$C_{oss}$			9.6	nF
$C_{rss}$			3.4	nF
$t_{d(on)}$	$V_{GS} = 10\text{ V}, V_{DS} = 0.5 \cdot V_{DSS}, I_D = 0.5 \cdot I_{D25}$ $R_G = 1\ \Omega$ (External)		210	ns
$t_r$			500	ns
$t_{d(off)}$			900	ns
$t_f$			350	ns
$Q_g$	$V_{GS} = 10\text{ V}, V_{DS} = 0.5 \cdot V_{DSS}, I_D = 0.5 \cdot I_{D25}$		2300	nC
$Q_{gs}$			420	nC
$Q_{gd}$			1150	nC
$R_{thJC}$				0.051 K/W
$R_{thJK}$	with 30 $\mu\text{m}$ heat transfer paste			0.076 K/W

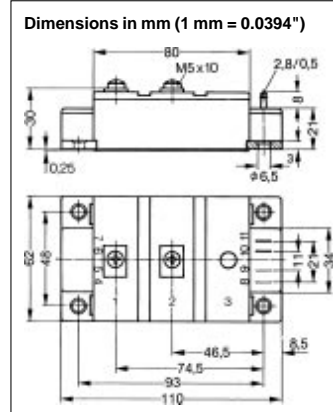

Symbol	Test Conditions	Characteristic Values ( $T_J = 25^\circ\text{C}$ , unless otherwise specified)		
		min.	typ.	max.
$I_S$	$V_{GS} = 0\text{ V}$			418 A
$I_{SM}$	Repetitive; pulse width limited by $T_{JM}$			1672 A
$V_{SD}$	$I_F = I_S; V_{GS} = 0\text{ V}$ , Pulse test, $t \leq 300\ \mu\text{s}$ , duty cycle $d \leq 2\%$		0.9	1.2 V
$t_{rr}$	$I_F = I_S, -di/dt = 1200\text{ A}/\mu\text{s}, V_{DS} = 100\text{ V}$		600	ns

4. The output voltages and current of a single-phase inverter are shown in the figure. Determine the following:

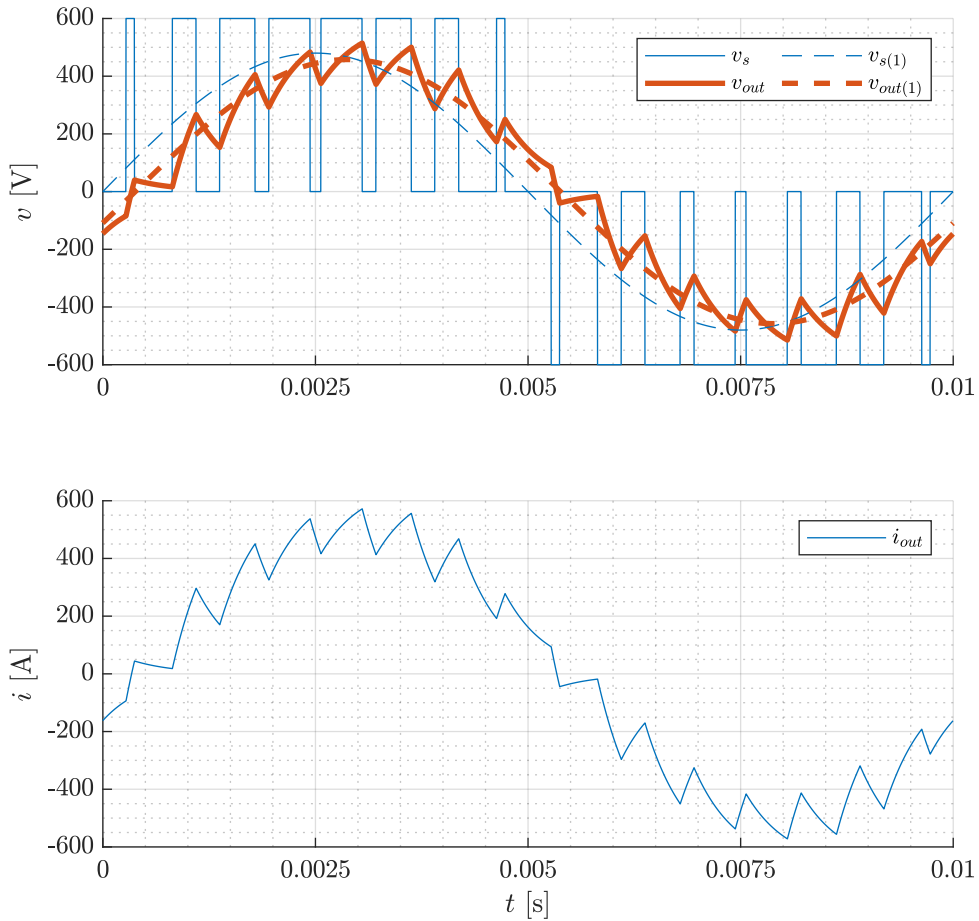


Figure 2: full-bridge inverter output waveforms.

- (a) **Type of modulation (unipolar or bipolar).**

Unipolar modulation.

- (b) **Switching frequency**

Counting the number of positive/negative pulses (or, rising/falling edges) for  $v_s$  in Figure 2, gives  $2 \times m_f$  as

$$2m_f = 16 \quad \Rightarrow \quad m_f = 8.$$

Since  $m_f$  is defined as

$$m_f = \frac{f_{sw}}{f_1} \quad \Rightarrow \quad f_{sw} = m_f f_1,$$

where  $f_1$  is the fundamental frequency, and from Figure 2

$$f_1 = \frac{1}{0.01 \text{ s}} = 100 \text{ Hz}.$$

Therefore,

$$f_{sw} = m_f f_1 = 800 \text{ Hz}.$$

(c) **Inductance.**

From Figure 2, during the time interval  $t \in [0.0025, 0.003]$  s, the  $v_s = 600$  V and for simplicity the voltage after the inductor  $v_{out}$  is about 450 V. Then the voltage drop across the inductor is

$$V_L = (v_{out}(t) - v_s(t)) \Big|_{t \in [0.0025, 0.003]} = L \frac{di(t)}{dt} \Big|_{t \in [0.0025, 0.003]}$$
$$\implies L = \frac{v_{out}(t) - v_s(t)}{\frac{di}{dt}} \Big|_{t \in [0.0025, 0.003]} .$$

$dt = 0.003 \text{ s} - 0.0025 \text{ s}$ , and from Figure 2,  $di = 500 \text{ A} - 400 \text{ A} = 100 \text{ A}$ . Therefore the inductance,  $L$  is

$$L = \frac{600 - 450}{\frac{100}{0.0005}} = 0.5 \text{ mH}.$$

(d) **Peak fundamental current.**

The peak fundamental output current occurs at  $0.0025 \text{ s} \leq t \leq 0.003 \text{ s}$ . The average current in this interval is the peak Fundamental output current ( $\hat{i}_{out(1)}$ )

$$\hat{i}_{out(1)} = \frac{410 + 570}{2} = 490 \text{ A}.$$

(e) **Pole-to-pole DC-link voltage ( $V_d$ ) and modulation index ( $m_a$ ).**

In the full-bridge inverter, the pole-to-pole DC-link voltage ( $V_d$ ) is

$$V_d = \hat{v}_s = 600 \text{ V}.$$

The modulation index ( $m_a$ ) is

$$m_a = \frac{\hat{v}_{s(1)}}{V_d} = \frac{480}{600} = 0.8.$$

(f) **Active power on the load at the fundamental frequency.**

The active power on the load ( $P_{out}$ ) at the fundamental frequency is

$$P_{out} = \frac{\hat{v}_{out(1)} \hat{i}_{out(1)}}{2} = \frac{455 \times 490}{2} = 111.5 \text{ kW}.$$

(g) **Phase angle of the fundamental current with respect to the inverter side voltage.**

At time  $t = 0 \text{ s}$  the reference signal (fundamental converter output voltage) is 0 V thus the converter output voltage ( $v_s$ ) is also assumed to be 0 V. However, the fundamental load current (or voltage) is 0 A (or 0 V) at  $t = 0.0004 \text{ s}$ . The time delay ( $\delta t$ ) is

$$\delta t = 0.0004 \text{ s}.$$

If time  $t = T = 0.01 \text{ s}$  is  $2\pi$ , then time  $t = \delta t$ , i.e., phase angle ( $\phi$ ) is

$$\phi = \frac{\delta t}{T} 2\pi = \frac{0.0004}{0.01} \times 2 \times \pi = 14.4^\circ.$$

(h) **Active and reactive power on the converter at the fundamental frequency.**

The active power ( $P_s$ ) on the converter side is

$$P_s = \frac{\hat{v}_{s(1)} \hat{i}_{out(1)}}{2} \cos(\phi) = \frac{480 \times 490}{2} \cos(14.4^\circ) = 113.91 \text{ kW}.$$

The reactive power ( $Q_s$ ) on the converter side is

$$Q_s = \frac{\hat{v}_{s(1)} \hat{i}_{out(1)}}{2} \sin(\phi) = \frac{480 \times 490}{2} \sin(14.4^\circ) = 29.25 \text{ kVar}.$$



5. The problem with ripple in the output current from a single-phase full bridge converter is to be studied. The first harmonic of the output voltage is given by  $V_{o(1)}$  at  $f_1 = 50$  Hz. The load is given in the figure as  $L = 10$  mH in series with an ideal voltage source  $e_o(t)$ . It is assumed that the converter operates in sinusoidal PWM mode, bipolar modulation.

$$e_o(t) = \sqrt{2} \cdot 220 \sin(2\pi f_1 t)$$

Table 1: Generalized harmonics of a half-bridge inverter output voltage for a large  $m_f$ .

$h \downarrow m_a \rightarrow$	0.2	0.4	0.6	0.8	1
1	0.2	0.4	0.6	0.8	1
Fundamental					
$m_f$	1.242	1.15	1.006	0.818	0.6023
$m_f \pm 2$	0.061	0.061	0.131	0.22	0.318
$m_f \pm 4$					0.018
$2m_f \pm 1$	0.19	0.326	0.37	0.314	0.181
$2m_f \pm 3$		0.024	0.071	0.139	0.212
$2m_f \pm 5$				0.013	0.033
$3m_f$	0.335	0.123	0.083	0.171	0.133
$3m_f \pm 2$	0.044	0.139	0.203	0.176	0.062
$3m_f \pm 4$		0.012	0.047	0.104	0.157
$3m_f \pm 6$				0.016	0.044
$4m_f \pm 1$	0.163	0.157	0.088	0.105	0.068
$4m_f \pm 3$	0.012	0.070	0.132	0.115	0.009
$4m_f \pm 5$			0.034	0.084	0.119
$4m_f \pm 7$				0.017	0.05

Note: output voltage ( $\hat{V}_o$ ) is  $\hat{V}_o = m_a V_d/2$ .

**Note:** Ripple here is referred to as distortion, which is the alteration of the original shape of a signal. Here ripple means the alteration of the waveform from an ideal sinusoidal signal.

- (a) **The frequency of the triangular signal is 1050 Hz. Calculate the frequency modulation ratio (or pulse number),  $m_f$ .**


$$m_f = \frac{f_{sw}}{f_1} = \frac{1050}{50} = 21.$$

- (b) **Find the dc-voltage when the converter fundamental RMS output voltage  $V_{o(1)}$  is 230 V and modulation index,  $m_a = 0.6$ .**

$$V_d = \frac{\hat{V}_{o(1)}}{m_a} = \frac{\sqrt{2} \times 230}{0.6} = 542.12 \text{ V.}$$

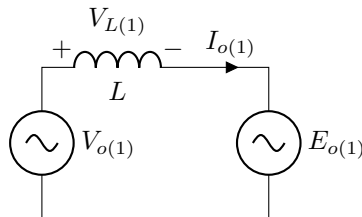- (c) **Determine the RMS fundamental output current (i.e., current through the inductor).**

The equivalent circuit at the fundamental frequency is given as follows



From the figure,

$$E_{o(1)} = V_{L(1)} + V_{o(1)} \implies V_{L(1)} = V_{o(1)} - E_{o(1)} = 230 - 220 = 10 \text{ V}$$

Also,


$$V_{L(1)} = \omega_n L I_{o(n)} = 2\pi n f_1 L I_{o(n)}.$$

Therefore, the average RMS fundamental output current ( $I_{o(1)}$ ), is

$$I_{o(1)} = \frac{V_{L(1)}}{2\pi f_1 L} = \frac{10}{2 \times \pi \times 50 \times 10 \times 10^{-3}} = 3.18 \text{ A}.$$

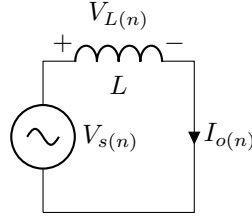- (d) **Determine the RMS and frequency of the highest output ripple current component.**

The equivalent circuit at the  $n^{\text{th}}$  harmonic, where  $n \neq 1$  is given as follows



From the figure,

$$V_{s(n)} = V_{L(n)} = \omega_n L I_{o(n)} = 2\pi n f_1 L I_{o(n)}.$$

or,

$$I_{o(n)} = \frac{V_{s(n)}}{2\pi n f_1 L} = \frac{k V_d}{2\pi n f_1 L}.$$

where  $n$  and its corresponding  $k$  values are taken from Table 1.

The highest ripple component occurs at  $m_f$ , which is 1050 Hz, and the peak value is

$$\hat{I}_{o(m_f)} = \frac{1.006 V_d}{2\pi m_f f_1 L} = \frac{1.006 \times 542.12}{2 \times \pi \times 21 \times 50 \times 10 \times 10^{-3}} = 8.27 \text{ A}.$$

The RMS ripple component is

$$I_{o(m_f)} = \frac{\hat{I}_{o(m_f)}}{\sqrt{2}} = 5.85 \text{ A}.$$

- (e) **If a Unipolar modulation is used, determine the RMS and frequency of the highest output ripple current component.**

In Unipolar modulation, the highest ripple components occur at  $2m_f \pm 1$ , which is 2050 Hz or 2150 Hz, and the peak values are

$$\hat{I}_{o(2m_f+1)} = \frac{0.37 V_d}{2\pi (2m_f - 1) f_1 L} = \frac{0.37 \times 542.12}{2 \times \pi \times (2 \times 21 - 1) \times 50 \times 10 \times 10^{-3}} = 1.56 \text{ A}.$$

$$\hat{I}_{o(2m_f-1)} = \frac{0.37 V_d}{2\pi (2m_f + 1) f_1 L} = \frac{0.37 \times 542.12}{2 \times \pi \times (2 \times 21 + 1) \times 50 \times 10 \times 10^{-3}} = 1.49 \text{ A}.$$

In Unipolar modulation, the highest ripple components occur at  $2m_f - 1$ , i.e., 2050 Hz. the RMS value is

$$I_{o(2m_f-1)} = \frac{\hat{I}_{o(2m_f-1)}}{\sqrt{2}} = 1.1 \text{ A}.$$