

1. You probably figured this one out :)

2. 1 kW, 100 V output step-up converter is to be evaluated. Consider all the components to be ideal. The input voltage is  $V_d = 48$  V, and the switching frequency is  $f_{sw} = 80$  kHz

- (a) **Calculate the output capacitor  $C$  when the output voltage peak-to-peak ripple is 5% of the output voltage  $V_o = 100$  V.**

The duty cycle ( $D$ ) is given by

$$D = 1 - \frac{V_d}{V_o} = 1 - \frac{48}{100} = \mathbf{0.52}.$$

The input current ( $I_d$ ) is

$$I_d = \frac{P}{V_d} = \frac{1000}{48} = \mathbf{20.83 \text{ A}}.$$

Since all the components are assumed to be ideal, the input and output powers are identical. Therefore, the output current ( $I_o$ ) is

$$I_o = \frac{P}{V_o} = \frac{1000}{100} = \mathbf{10 \text{ A}}$$

the output capacitor ( $C$ ) when the output voltage peak-to-peak ripple is 5% of the output voltage  $V_o = 100$  V is

$$C = \frac{I_o D}{\Delta V_o f_{sw}} = \frac{10 \times 0.52}{0.05 \times 100 \times 80 \times 10^3} = \mathbf{13 \mu\text{F}}.$$

- (b) **Consider filter inductance  $L = 40 \mu\text{H}$ , calculate  $I_{L(\text{peak})}$ . Is the converter in continuous conduction mode?**

The peak-to-peak ripple input (or inductor) current is

$$\Delta I_d = \frac{D V_o}{L f_{sw}} (1 - D) = \frac{0.52 \times 100}{40 \times 10^{-6} \times 80 \times 10^3} \times (1 - 0.52) = \mathbf{7.8 \text{ A}}.$$

The maximum and minimum values of the inductor current ( $I_d^{\text{max}}$  and  $I_d^{\text{min}}$ , respectively) are

$$I_d^{\text{max}} = I_d + \frac{\delta I_d}{2} = \mathbf{24.73 \text{ A}}$$

$$I_d^{\text{min}} = I_d - \frac{\delta I_d}{2} = \mathbf{16.93 \text{ A}}$$

Since,  $I_d^{\text{min}} > 0$ , the converter is in continuous conduction mode.

- (c) **Consider filter inductance  $L = 6 \mu\text{H}$ , calculate  $I_{L(\text{peak})}$ . Is the converter in continuous conduction mode?**

The peak-to-peak ripple input (or inductor) current is

$$\Delta I_d = \frac{D V_o}{L f_{sw}} (1 - D) = \frac{0.52 \times 100}{6 \times 10^{-6} \times 80 \times 10^3} \times (1 - 0.52) = \mathbf{52 \text{ A}}.$$

The maximum and minimum values of the inductor current ( $I_d^{\text{max}}$  and  $I_d^{\text{min}}$ , respectively) are

$$I_d^{\text{max}} = I_d + \frac{\delta I_d}{2} = \mathbf{46.83 \text{ A}}$$

$$I_d^{\text{min}} = I_d - \frac{\delta I_d}{2} = \mathbf{-5.17 \text{ A}}$$

Since,  $I_d^{\text{min}} < 0$ , the converter is **not** in continuous conduction mode.

- (d) **Determine the conduction losses of the MOSFET if the on-state resistance of the MOSFET is  $1 \text{ m}\Omega$ .**

The conduction losses of the MOSFET is

$$P_{\text{mos}}^l = D I_d^2 R_{\text{ds(on)}} = 0.52 \times (20.83)^2 \times 1 \times 10^{-3} = \mathbf{0.23 \text{ W}}$$

3. An n-channel power MOSFET, IPD023N04NF2S by Infineon, is to be used in a step-down converter (*datasheet is attached*). The MOSFET conducts an RMS current of 100 A. The switching frequency is 10 kHz, the duty cycle ( $D$ ) is 0.75 and the input voltage of the converter is 20 V.

- (a) **Calculate the total MOSFET power losses (assume the same time for voltage and current transients, i.e.,  $t_{ri} = t_{fv} = t_r$  and  $t_{fi} = t_{rv} = t_f$ ).**

From the MOSFET datasheets, the on-state resistance of the MOSFET ( $r_{ds(on)}$ ) and the switching transient times are

$$r_{ds(on)} = 2.3 \text{ m}\Omega \quad t_{ri} = t_{fv} = 15 \text{ ns}, \quad t_{rv} = t_{fi} = 15 \text{ ns}.$$

The conduction losses of the MOSFET ( $P_c^l$ ) is

$$P_c^l = D I_{\text{mos}}^2 r_{ds(on)} = 0.5 \times 100^2 \times 2.3 \times 10^{-3} = \mathbf{11.5 \text{ W}}.$$

In the DC-DC converter the peak MOSFET current ( $\hat{I}_{\text{mos}}$ ) is

$$\hat{I}_{\text{mos}} = \frac{I_{\text{mos}}}{D} = \frac{100}{0.75} = \mathbf{133.33 \text{ A}}.$$

The switching losses of the MOSFET ( $P_s^l$ ) is

$$\begin{aligned} P_s^l &= \frac{1}{2} V_d \hat{I}_{\text{mos}} t_{\text{sw}} f_{\text{sw}} = \frac{1}{2} V_d \hat{I}_{\text{mos}} (t_{ri} + t_{fv} + t_{rv} + t_{fi}) f_{\text{sw}} \\ &= \frac{1}{2} \times 20 \times 133.33 \times (2 \times 15 \times 10^{-9} + 2 \times 15 \times 10^{-9}) \times 10 \times 10^3 = \mathbf{80 \text{ mW}}. \end{aligned}$$

The total losses in the MOSFET ( $P^l$ ) is

$$P^l = P_c^l + P_s^l = 11.5 + 0.08 = \mathbf{11.58 \text{ W}}.$$

- (b) **If the internal junction temperature is not to exceed 100°C and the maximum ambient temperature is 35°C, specify the thermal resistance of the required heat sink.**

The thermal resistance of the required heat sink is

$$\begin{aligned} \Delta T_{\text{ja}} &= P^l (R_{\theta_{\text{jc}}} + R_{\theta_{\text{ca}}}) \implies R_{\theta_{\text{ca}}} = \frac{\Delta T_{\text{ja}}}{P^l} - R_{\theta_{\text{jc}}} \\ \implies R_{\theta_{\text{ca}}} &= \frac{100 - 35}{11.5} - 1 = \mathbf{4.61 \text{ K/W}}. \end{aligned}$$

- (c) **Determine the peak MOSFET drain-to-source voltage during the turn-off transient if the parasitic inductance between the input voltage source and the MOSFET drain-terminal is 3 nH.**

The voltage across the MOSFET during the turn-off transient is

$$V_{\text{ds}}^{\text{max}} = V_d - L \frac{dV_{\text{ds}}}{dt} = 20 - 3 \times 10^{-9} \times \frac{0 - 100}{15 \times 10^{-9}} = \mathbf{40 \text{ V}}.$$

## 1 Maximum ratings

at  $T_A=25\text{ °C}$ , unless otherwise specified

**Table 2 Maximum ratings**

Parameter	Symbol	Values			Unit	Note / Test Condition
		Min.	Typ.	Max.		
Continuous drain current <sup>1)</sup>	$I_D$	-	-	143 110 27	A	$V_{GS}=10\text{ V}$ , $T_C=25\text{ °C}$ $V_{GS}=10\text{ V}$ , $T_C=100\text{ °C}$ $V_{GS}=10\text{ V}$ , $T_A=25\text{ °C}$ , $R_{THJA}=50\text{ °C/W}^2)$
Pulsed drain current <sup>3)</sup>	$I_{D,pulse}$	-	-	572	A	$T_A=25\text{ °C}$
Avalanche energy, single pulse <sup>4)</sup>	$E_{AS}$	-	-	167	mJ	$I_D=70\text{ A}$ , $R_{GS}=25\text{ }\Omega$
Gate source voltage	$V_{GS}$	-20	-	20	V	-
Power dissipation	$P_{tot}$	-	-	150 3.0	W	$T_C=25\text{ °C}$ $T_A=25\text{ °C}$ , $R_{THJA}=50\text{ °C/W}^2)$
Operating and storage temperature	$T_J$ , $T_{stg}$	-55	-	175	°C	-

## 2 Thermal characteristics

**Table 3 Thermal characteristics**

Parameter	Symbol	Values			Unit	Note / Test Condition
		Min.	Typ.	Max.		
Thermal resistance, junction - case	$R_{thJC}$	-	-	1.0	°C/W	-
Thermal resistance, junction - ambient, 6 cm <sup>2</sup> cooling area <sup>2)</sup>	$R_{thJA}$	-	-	50	°C/W	-
Thermal resistance, junction - ambient, minimal footprint	$R_{thJA}$	-	-	75	°C/W	-

<sup>1)</sup> Rating refers to the product only with datasheet specified absolute maximum values, maintaining case temperature as specified. For other case temperatures please refer to Diagram 2. De-rating will be required based on the actual environmental conditions.

<sup>2)</sup> Device on 40 mm x 40 mm x 1.5 mm epoxy PCB FR4 with 6 cm<sup>2</sup> (one layer, 70 µm thick) copper area for drain connection. PCB is vertical in still air.

<sup>3)</sup> See Diagram 3 for more detailed information

<sup>4)</sup> See Diagram 13 for more detailed information

**3 Electrical characteristics**  
 at  $T_j=25\text{ °C}$ , unless otherwise specified

**Table 4 Static characteristics**

Parameter	Symbol	Values			Unit	Note / Test Condition
		Min.	Typ.	Max.		
Drain-source breakdown voltage	$V_{(BR)DSS}$	40	-	-	V	$V_{GS}=0\text{ V}$ , $I_D=1\text{ mA}$
Gate threshold voltage	$V_{GS(th)}$	2.2	2.8	3.4	V	$V_{DS}=V_{GS}$ , $I_D=81\text{ }\mu\text{A}$
Zero gate voltage drain current	$I_{DSS}$	-	0.1 10	1 100	$\mu\text{A}$	$V_{DS}=40\text{ V}$ , $V_{GS}=0\text{ V}$ , $T_j=25\text{ °C}$ $V_{DS}=40\text{ V}$ , $V_{GS}=0\text{ V}$ , $T_j=125\text{ °C}$
Gate-source leakage current	$I_{GSS}$	-	10	100	nA	$V_{GS}=20\text{ V}$ , $V_{DS}=0\text{ V}$
Drain-source on-state resistance	$R_{DS(on)}$	-	1.9 2.2	2.3 3.1	$\text{m}\Omega$	$V_{GS}=10\text{ V}$ , $I_D=70\text{ A}$ $V_{GS}=6\text{ V}$ , $I_D=35\text{ A}$
Gate resistance	$R_G$	-	3.0	-	$\Omega$	-
Transconductance <sup>1)</sup>	$g_{fs}$	125	-	-	S	$ V_{DS} \geq 2 I_D R_{DS(on)max}$ , $I_D=70\text{ A}$

**Table 5 Dynamic characteristics**

Parameter	Symbol	Values			Unit	Note / Test Condition
		Min.	Typ.	Max.		
Input capacitance	$C_{iss}$	-	4800	-	pF	$V_{GS}=0\text{ V}$ , $V_{DS}=20\text{ V}$ , $f=1\text{ MHz}$
Output capacitance	$C_{oss}$	-	1800	-	pF	$V_{GS}=0\text{ V}$ , $V_{DS}=20\text{ V}$ , $f=1\text{ MHz}$
Reverse transfer capacitance	$C_{rss}$	-	98	-	pF	$V_{GS}=0\text{ V}$ , $V_{DS}=20\text{ V}$ , $f=1\text{ MHz}$
Turn-on delay time	$t_{d(on)}$	-	16	-	ns	$V_{DD}=20\text{ V}$ , $V_{GS}=10\text{ V}$ , $I_D=70\text{ A}$ , $R_{G,ext}=1.6\text{ }\Omega$
Rise time	$t_r$	-	15	-	ns	$V_{DD}=20\text{ V}$ , $V_{GS}=10\text{ V}$ , $I_D=70\text{ A}$ , $R_{G,ext}=1.6\text{ }\Omega$
Turn-off delay time	$t_{d(off)}$	-	35	-	ns	$V_{DD}=20\text{ V}$ , $V_{GS}=10\text{ V}$ , $I_D=70\text{ A}$ , $R_{G,ext}=1.6\text{ }\Omega$
Fall time	$t_f$	-	15	-	ns	$V_{DD}=20\text{ V}$ , $V_{GS}=10\text{ V}$ , $I_D=70\text{ A}$ , $R_{G,ext}=1.6\text{ }\Omega$

**Table 6 Gate charge characteristics<sup>2)</sup>**

Parameter	Symbol	Values			Unit	Note / Test Condition
		Min.	Typ.	Max.		
Gate to source charge	$Q_{gs}$	-	21	-	nC	$V_{DD}=20\text{ V}$ , $I_D=70\text{ A}$ , $V_{GS}=0\text{ to }10\text{ V}$
Gate charge at threshold	$Q_{g(th)}$	-	13.5	-	nC	$V_{DD}=20\text{ V}$ , $I_D=70\text{ A}$ , $V_{GS}=0\text{ to }10\text{ V}$
Gate to drain charge	$Q_{gd}$	-	13	-	nC	$V_{DD}=20\text{ V}$ , $I_D=70\text{ A}$ , $V_{GS}=0\text{ to }10\text{ V}$
Switching charge	$Q_{sw}$	-	20	-	nC	$V_{DD}=20\text{ V}$ , $I_D=70\text{ A}$ , $V_{GS}=0\text{ to }10\text{ V}$
Gate charge total <sup>1)</sup>	$Q_g$	-	68	102	nC	$V_{DD}=20\text{ V}$ , $I_D=70\text{ A}$ , $V_{GS}=0\text{ to }10\text{ V}$
Gate plateau voltage	$V_{plateau}$	-	4.3	-	V	$V_{DD}=20\text{ V}$ , $I_D=70\text{ A}$ , $V_{GS}=0\text{ to }10\text{ V}$
Gate charge total, sync. FET	$Q_{g(sync)}$	-	61	-	nC	$V_{DS}=0.1\text{ V}$ , $V_{GS}=0\text{ to }10\text{ V}$
Output charge	$Q_{oss}$	-	76	-	nC	$V_{DS}=20\text{ V}$ , $V_{GS}=0\text{ V}$

<sup>1)</sup> Defined by design. Not subject to production test.

<sup>2)</sup> See "Gate charge waveforms" for parameter definition

4. The output voltages and current of a single-phase full-bridge inverter are shown in Figure 1.

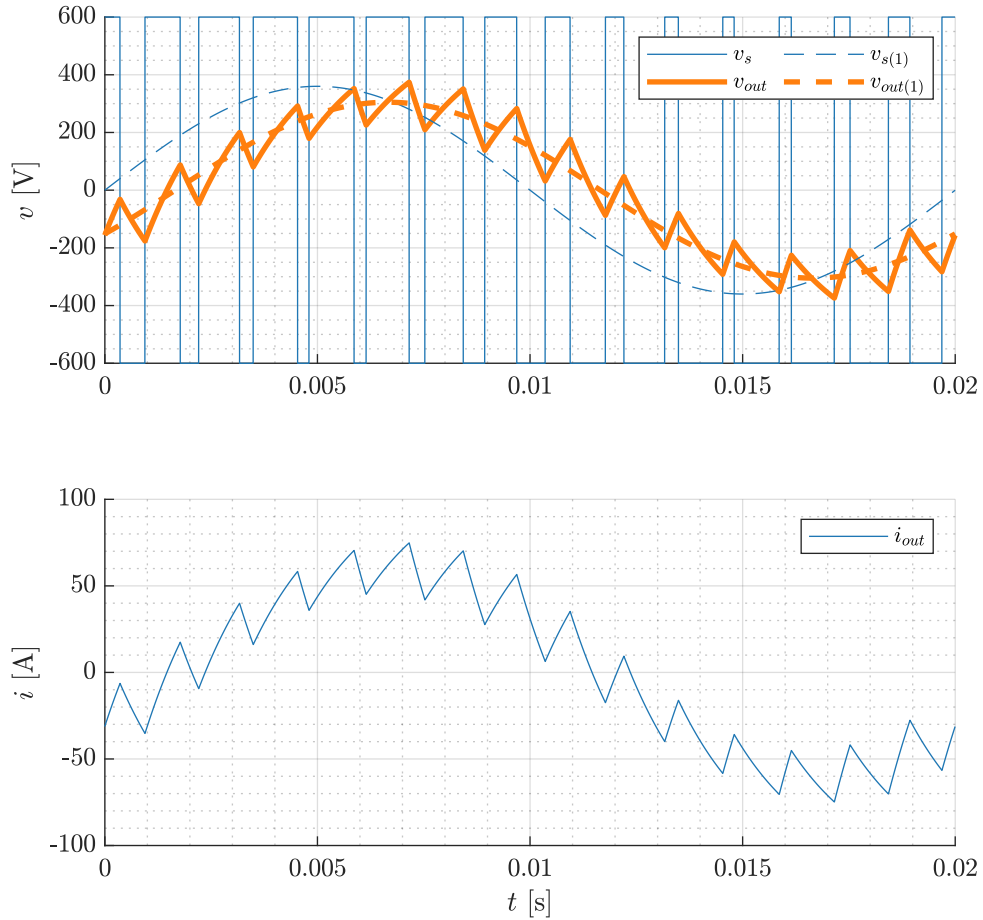


Figure 1: full-bridge inverter output waveforms.

(a) **Type of modulation (unipolar or bipolar).**

Bipolar modulation.

(b) **Switching frequency**

Counting the number of positive/negative pulses (or, rising/falling edges) for  $v_s$  in Figure 1, gives

$$m_f = 15.$$

Since  $m_f$  is defined as

$$m_f = \frac{f_{sw}}{f_1} \quad \Rightarrow \quad f_{sw} = m_f f_1,$$

where  $f_1$  is the fundamental frequency, and from Figure 1

$$f_1 = \frac{1}{0.02 \text{ s}} = 50 \text{ Hz}.$$

Therefore,

$$f_{sw} = m_f f_1 = 15 \times 50 = \mathbf{750 \text{ Hz}}.$$

(c) **Inductance.**

From Figure 1, during the time interval  $t \in [0.005, 0.006]$  s, the  $v_s = 600$  V and for simplicity the voltage after the inductor  $v_{out}$  is about 275 V. Then the voltage drop across the inductor is

$$V_L = (v_{out}(t) - v_s(t)) \Big|_{t \in [0.005, 0.006]} = L \frac{di(t)}{dt} \Big|_{t \in [0.005, 0.006]}$$
$$\implies L = \frac{v_{out}(t) - v_s(t)}{\frac{di}{dt}} \Big|_{t \in [0.005, 0.006]}.$$

$dt = 0.006 \text{ s} - 0.005 \text{ s}$ , and from Figure 1,  $di = 70 \text{ A} - 38 \text{ A} = 32 \text{ A}$ . Therefore the inductance,  $L$  is

$$L = \frac{600 - 275}{\frac{32}{0.001}} = \mathbf{10.2 \text{ mH}}.$$

(d) **Peak fundamental current.**

The peak fundamental output current occurs at  $0.006 \text{ s} \leq t \leq 0.007 \text{ s}$ . The average current in this interval is the peak Fundamental output current ( $\hat{i}_{out(1)}$ )

$$\hat{i}_{out(1)} = \frac{45 + 75}{2} = \mathbf{60 \text{ A}}.$$

(e) **Pole-to-pole DC-link voltage ( $V_d$ ) and modulation index ( $m_a$ ).**

In the full-bridge inverter, the pole-to-pole DC-link voltage ( $V_d$ ) is

$$V_d = \hat{v}_s = 600 \text{ V}.$$

The modulation index ( $m_a$ ) is

$$m_a = \frac{\hat{v}_{s(1)}}{V_d} = \frac{360}{600} = \mathbf{0.6}.$$

(f) **Active power on the load at the fundamental frequency.**

The active power on the load ( $P_{out}$ ) at the fundamental frequency is

$$P_{out} = \frac{\hat{v}_{out(1)} \hat{i}_{out(1)}}{2} = \frac{300 \times 60}{2} = \mathbf{9 \text{ kW}}.$$

(g) **Phase angle of the fundamental current with respect to the inverter side voltage.**

At time  $t = 0 \text{ s}$  the reference signal (fundamental converter output voltage) is 0 V thus the converter output voltage ( $v_s$ ) is also assumed to be 0 V. However, the fundamental load current (or voltage) is 0 A (or 0 V) at  $t = 0.0017 \text{ s}$ . The time delay ( $\delta t$ ) is

$$\delta t = 0.0017 \text{ s}.$$

If time  $t = T = 0.02 \text{ s}$  is  $2\pi$ , then at time  $t = \delta t$ , the phase angle ( $\phi$ ) is

$$\phi = \frac{\delta t}{T} 2\pi = \frac{0.0017}{0.02} \times 2 \times \pi = \mathbf{30.6^\circ}.$$

(h) **Active and reactive power on the converter at the fundamental frequency.**

The active power ( $P_s$ ) on the converter side is

$$P_s = \frac{\hat{v}_{s(1)} \hat{i}_{out(1)}}{2} \cos(\phi) = \frac{360 \times 60}{2} \cos(30.6^\circ) = \mathbf{9.3 \text{ kW}}.$$

The reactive power ( $Q_s$ ) on the converter side is

$$Q_s = \frac{\hat{v}_{s(1)} \hat{i}_{out(1)}}{2} \sin(\phi) = \frac{360 \times 60}{2} \sin(30.6^\circ) = \mathbf{5.5 \text{ kVar}}.$$

5. For a full-bridge inverter with unipolar modulation, the RMS fundamental (at 150 Hz) output voltage and current are 1 kV and 180 A respectively. The inverter incorporates a filter inductor with inductance  $100 \mu\text{H}$  and it operates with a modulation index of 0.8 with a switching frequency of 10 kHz.

Table 1: Generalized harmonics of a half-bridge inverter output voltage for a large  $m_f$ .


$h \downarrow$ $m_a \rightarrow$	0.2	0.4	0.6	0.8	1
1	0.2	0.4	0.6	0.8	1
Fundamental					
$m_f$	1.242	1.15	1.006	0.818	0.6023
$m_f \pm 2$	0.061	0.061	0.131	0.22	0.318
$m_f \pm 4$					0.018
$2m_f \pm 1$	0.19	0.326	0.37	0.314	0.181
$2m_f \pm 3$		0.024	0.071	0.139	0.212
$2m_f \pm 5$				0.013	0.033
$3m_f$	0.335	0.123	0.083	0.171	0.133
$3m_f \pm 2$	0.044	0.139	0.203	0.176	0.062
$3m_f \pm 4$		0.012	0.047	0.104	0.157
$3m_f \pm 6$				0.016	0.044
$4m_f \pm 1$	0.163	0.157	0.088	0.105	0.068
$4m_f \pm 3$	0.012	0.070	0.132	0.115	0.009
$4m_f \pm 5$			0.034	0.084	0.119
$4m_f \pm 7$				0.017	0.05

Note: output voltage ( $\hat{V}_o$ ) is  $\hat{V}_o = m_a V_d/2$ .

**Note:** Ripple here is referred to as distortion, which is the alteration of the original shape of a signal. Here ripple means the alteration of the waveform from an ideal sinusoidal signal.

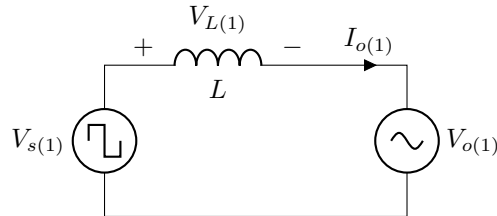(a) **Determine the dc-link voltage of the inverter**

The equivalent circuit at the fundamental frequency is given as



The peak fundamental converter voltage ( $V_{s(1)}$ ) is determined using KVL, i.e.,

$$V_{s(1)} = V_{o(1)} + I_{o(1)} \omega_1 L = 1000 - 180 \times 2 \times \pi \times 150 \times 100 \times -6 = \mathbf{1094.2 \text{ V}}$$

The peak fundamental converter output voltage ( $\hat{V}_{s(1)}$ ) is

$$\hat{V}_{s(1)} = \sqrt{2} V_{s(1)} = \sqrt{2} \times 1094.2 = \mathbf{1547.4 \text{ V}}.$$


The DC-link voltage is calculated as

$$V_d = \frac{\hat{V}_{s(1)}}{m_a} = \frac{1547.5}{0.8} = \mathbf{1934.4 \text{ V}}.$$



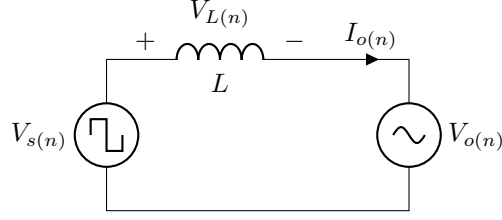- (b) Calculate the magnitude (in RMS) and frequency of the largest component of the output current for a modulation index of 0.8. Assume that the magnitude of all the other components of the output voltage is zero.

The equivalent circuit at the  $n^{\text{th}}$  harmonic, where  $n \neq 1$  is



The RMS output voltage at the  $n^{\text{th}}$  harmonic ( $V_{o(n)}$ ) is

$$V_{o(n)} = V_{s(n)} - I \omega_n L. \quad (1)$$

From Table 1, the highest harmonic component for uni-polar modulation is at  $2m_f \pm 1$ , i.e.,

$$V_{s(2m_f \pm 1)} = 0.314 \frac{V_d}{\sqrt{2}} = 0.314 \times \frac{1934.4}{\sqrt{2}} = \mathbf{429.5 \text{ V}},$$

and

$$m_f = \frac{f_{\text{sw}}}{f_1} = \frac{10 \times 10^3}{150} = \mathbf{66.67}.$$

The output current at the  $n^{\text{th}}$  harmonic ( $I_{o(n)}$ ), from (1) is

$$I_{o(n)} = \frac{V_{s(n)} - V_{o(n)}}{\omega_n L} = \frac{429.5 - 0}{2\pi \times (n) \times 150 \times 1 \times 100^{-6}}$$

. Substituting,  $n = 2m_f \pm 1$ ,

$$I_{o(2m_f+1)} = \mathbf{33.92 \text{ A}}, \quad \text{and, } I_{o(2m_f-1)} = \mathbf{34.44 \text{ A}}.$$

The highest harmonic component of the output current occurs at  $2m_f - 1$ , i.e., at **19.85 kHz** with a magnitude of **34.44 A**.