

Calculation of on-state and switching losses in a PWM DC/AC or DC/DC converter

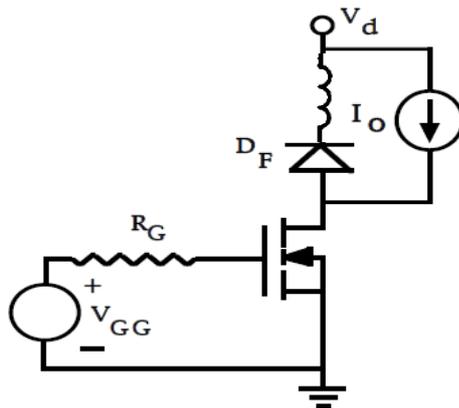


Figure 1 Equivalent switching circuit for a MOSFET/diode pair

The circuit above is considered when calculating losses in one switching device, e.g. MOSFET. Switching in most basic voltage source converters involves commutation of current between a diode and a MOSFET (or other switching devices). The waveform for a typical switching sequence is shown in Figure 2.

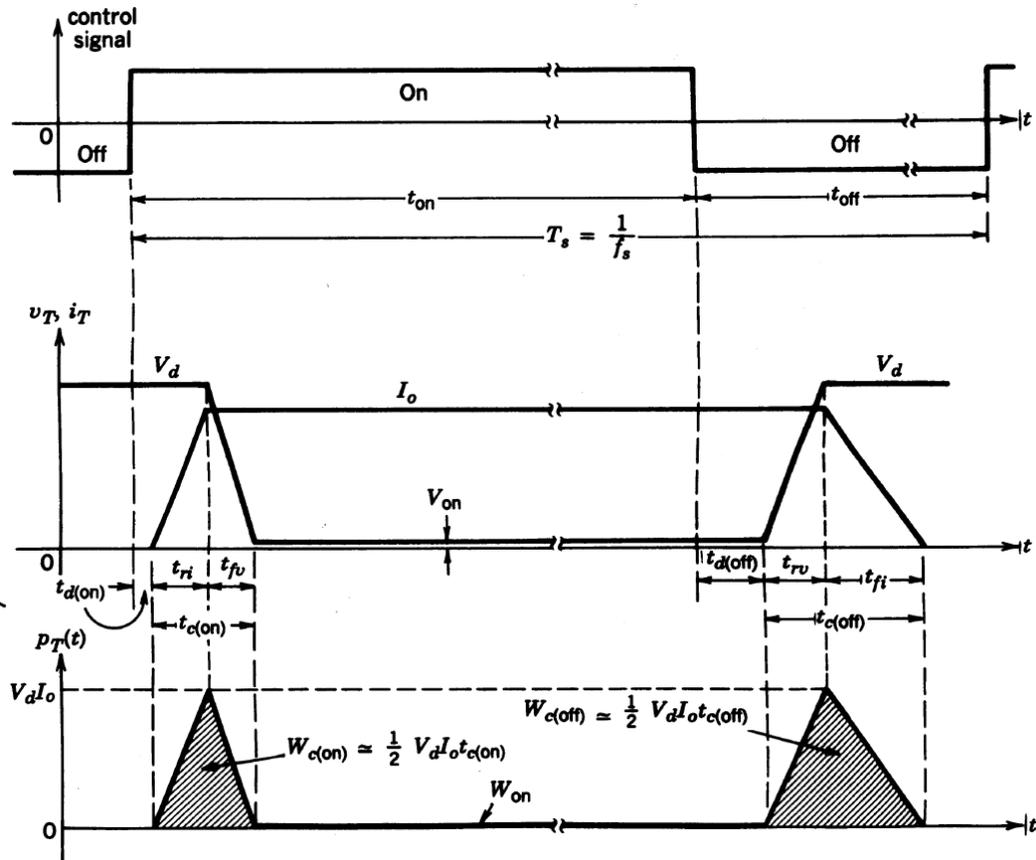


Figure 2 Switching sequence

The power loss during on-state is calculated as:

$$P_{on} = V_{on} I_o \frac{t_{on}}{T_s} = r_{on} I_o^2 \frac{t_{on}}{T_s}$$

Equation 1

Here I_o is the actual current during the conduction interval. For a simplified calculation I_o can be considered as the total rms current (I_v) through the inductance L . The factor $\frac{t_{on}}{T_s}$ equals the duty cycle D of a DC/DC converter.

$$P_{on(\frac{DC}{DC})} = r_{on} I_{v,rms}^2 D$$

Equation 2

For a DC/AC converter the duty cycle is varying between a small and a large value when the control signal is in the positive or negative half cycle, as shown in Figure 3(b).

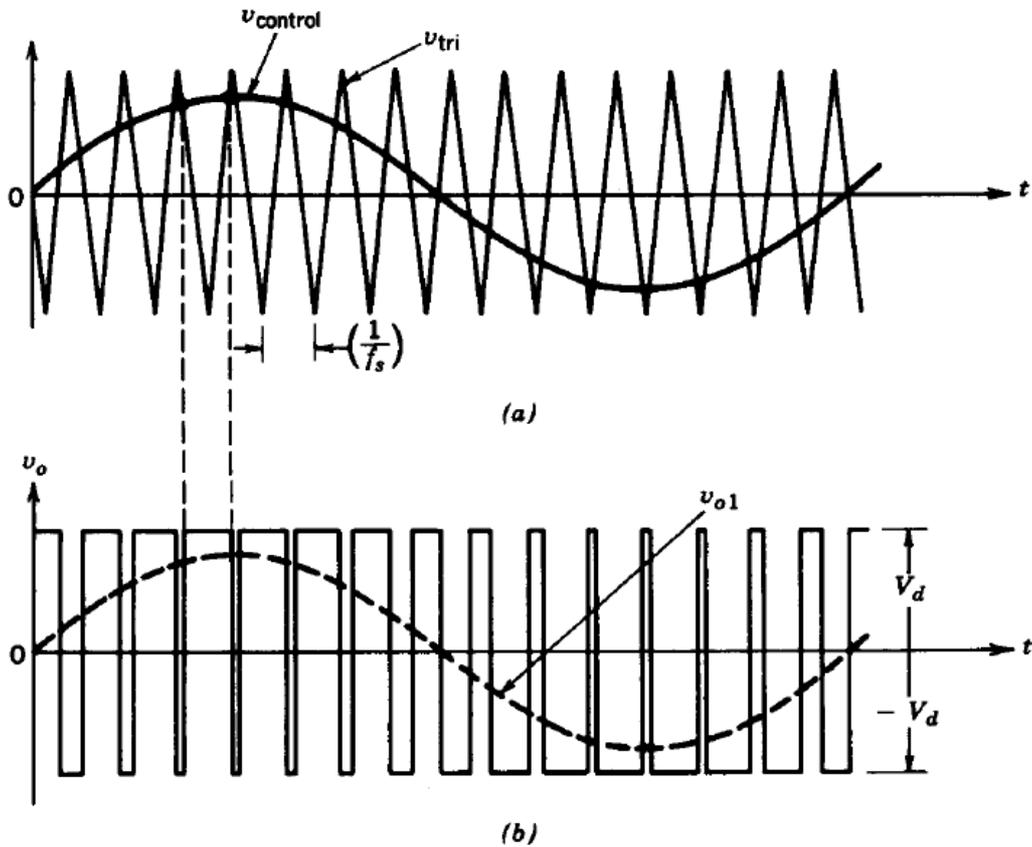


Figure 3 DC/AC converter PWM

Defining the amplitude ratio, m_a , between amplitudes of the control signal and PWM triangular wave defined as:

$$m_a = \frac{\hat{V}_{control}}{\hat{V}_{tri}}$$

The max and min duty cycle can be defined as:

$$D_{max} = 0.5 + \frac{m_a}{2}, D_{min} = 0.5 - \frac{m_a}{2}$$

Consequently, on average, the duty cycle in an DC/AC converter can be considered as 0.5.

$$P_{on(\frac{DC}{AC})} = \frac{1}{2} r_{on} I_{v,rms}^2$$

Equation 3

Switching losses

The power losses during switching is defined as:

$$P_s = \frac{1}{2} V_d I_o f_s (t_{c(on)} + t_{c(off)})$$

Equation 4

The time delays for turn-on and turn-off can be estimated using the capacitor equivalent of the MOSFET and a gate drive represented as a voltage source V_{GG} in series with a resistance R_G .

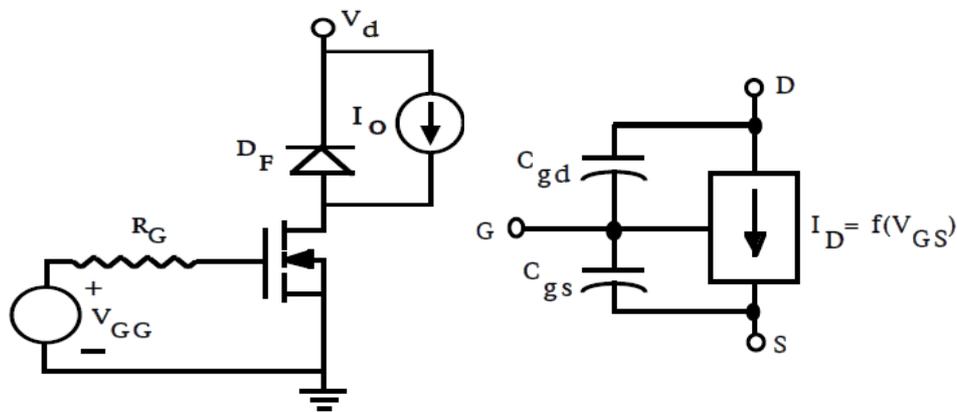


Figure 4

Four time delays are used to define the wave forms of current and voltage during switching:

Turn-on:

t_{ri} : Rise time of current

t_{fv} : Fall time of voltage

Turn-off

t_{rv} : Rise time of voltage

t_{fi} : Fall time of current

Based on the definition of time delays for MOSFET turn-on and turn-off from [1] per Figure 5 below, the four time delays above can be determined.

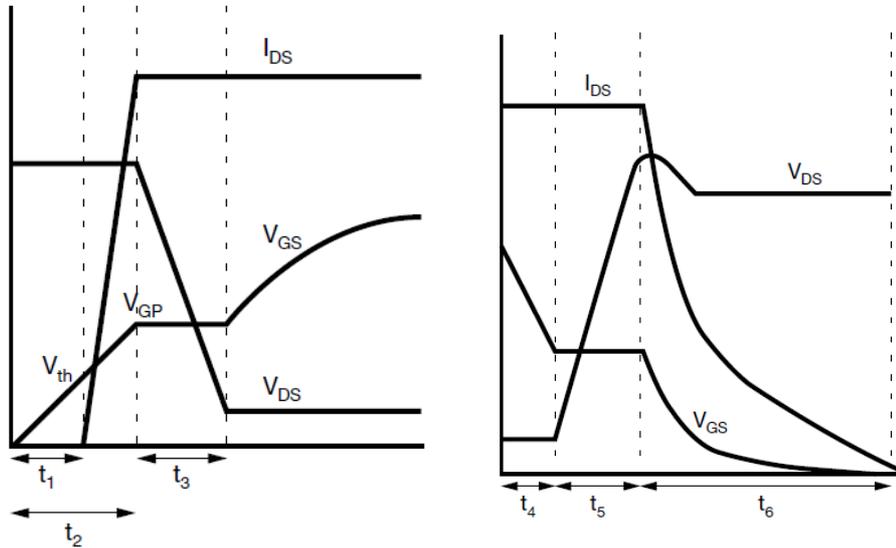


Figure 5 MOSFET turn-on and turn-off waveforms

$$t_{ri} = t_2 - t_1$$

$$t_{fv} = t_3$$

$$t_{rv} = t_5$$

$$t_{fi} = t_6$$

For the MOSFET based converter used in Lab 3 the following parameters are used:

$$R_{gon} = 1000 \text{ ohm}$$

$$R_{goff} = 10 \text{ ohm}$$

$$V_{GG(on)} = 15\text{V}$$

$$V_{GG(off)} = 1.2\text{V (incl schottky diode voltage and output voltage of driver)}$$

$$V_{gs(th-on)} = 4\text{V (MOSFET gate threshold at turn-on)}$$

$$V_{gs(th-off)} = 2\text{V (MOSFET gate threshold at turn-off)}$$

$$V_{GP} = 4.2 \text{ V (Miller plateau voltage of } V_{gs})$$

$$C_{iss} = 1700 \text{ pF @ } V_{ds}=25\text{V}$$

$$C_{iss} = 2500 \text{ pF @ } V_{ds}=0\text{V}$$

$$C_{rss} = 200 \text{ pF @ } V_{ds}=10\text{V}$$

$$C_{rss} = 500 \text{ pF @ } V_{ds}=2.5\text{V}$$

$$t_1 = R_{gon}(C_{gs} + C_{gd}) \ln \left(\frac{1}{1 - \frac{V_{gs(th-on)}}{V_{GG(on)}}} \right); C_{gs} + C_{gd} = C_{iss} @ V_{ds} = 25V$$

$$t_2 = R_{gon}(C_{gs} + C_{gd}) \ln \left(\frac{1}{1 - \frac{V_{GP}}{V_{GG(on)}}} \right); C_{gs} + C_{gd} = C_{iss} @ V_{ds} = 25V$$

$$t_3 = R_{gon} C_{gd} \frac{V_{ds}}{V_{GG(on)} - V_{GP}}; C_{gd} = C_{rss} @ V_{ds} = 2.5V$$

$$t_5 = R_{goff} C_{gd} \frac{V_{ds}}{V_{GP}}; C_{gd} = C_{rss} @ V_{ds} = 2.5V$$

$$t_6 = R_{goff}(C_{gs} + C_{gd}) \ln \left(\frac{V_{GP}}{V_{gs(th-off)}} \right); C_{gs} + C_{gd} = C_{iss} @ V_{ds} = 0V$$

The MOSFET time delays are calculated as:

$$t_1 = 527 \text{ ns}$$

$$t_2 = 565 \text{ ns}$$

$$t_3 = 690 \text{ ns}$$

$$t_5 = 24 \text{ ns}$$

$$t_6 = 32 \text{ ns}$$

This gives the following values of the time delays:

$$t_{ri} = \mathbf{38 \text{ ns}}$$

$$t_{fv} = \mathbf{690 \text{ ns}}$$

$$t_{rv} = \mathbf{24 \text{ ns}}$$

$$t_{fi} = \mathbf{32 \text{ ns}}$$

Consequently, the total switching losses can be calculated as:

$$P_s = \frac{1}{2} V_d I_o f_s (t_{ri} + t_{fv} + t_{rv} + t_{fi}) = V_d I_o f_s 0.39 \mu W$$

Where I_o should be the MOSFET current at the actual switching for detailed result.

To simplify calculations the average MOSFET current can be used instead.

$$I_{o(\frac{DC}{DC})} = I_{v,av}$$

For a DC/AC converter the average of a sinusoidal current can be used as:

$$I_{o(\frac{DC}{AC})} = \frac{2\sqrt{2}}{\pi} I_{v,rms}$$

References

- [1] Application Note 608, Power MOSFET Basics: Understanding Gate Charge and Using it to Assess Switching Performance, VISHAY Siliconix